
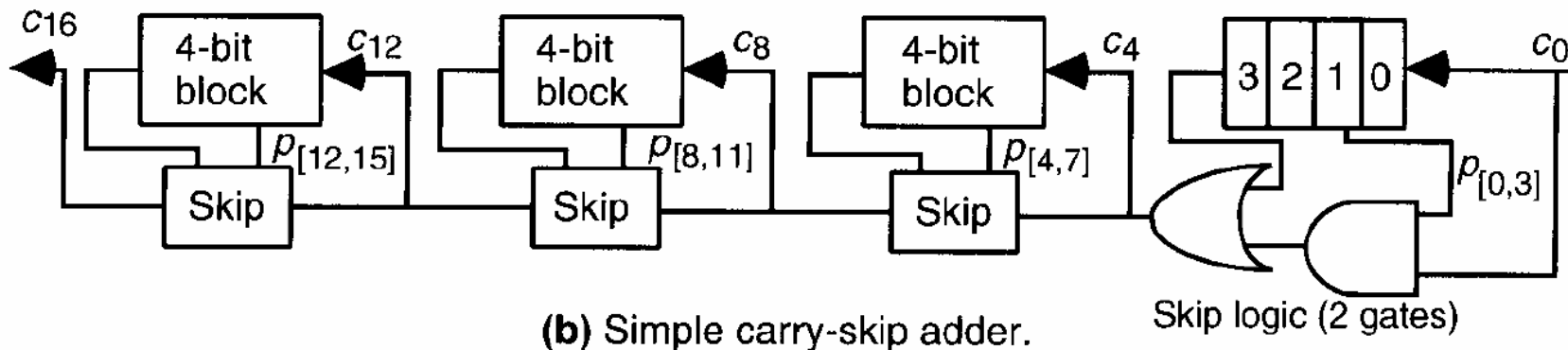



Chapter 7 **Variations in Fast Adders**

- ❑ Simple Carry-Skip Adders
- ❑ Multilevel Carry-Skip Adders
- ❑ Carry-Select Adders
- ❑ Conditional-Sum Adder
- ❑ Hybrid Adder Designs
- ❑ Optimizations in Fast Adders

Simple Carry-Skip Adders

 


Skip Logic in Carry-Skip Adders

 

carry = 1
if (a carry is generated) or
($C_0 == 1$ and Propagation == 1)

Worst Case Delay

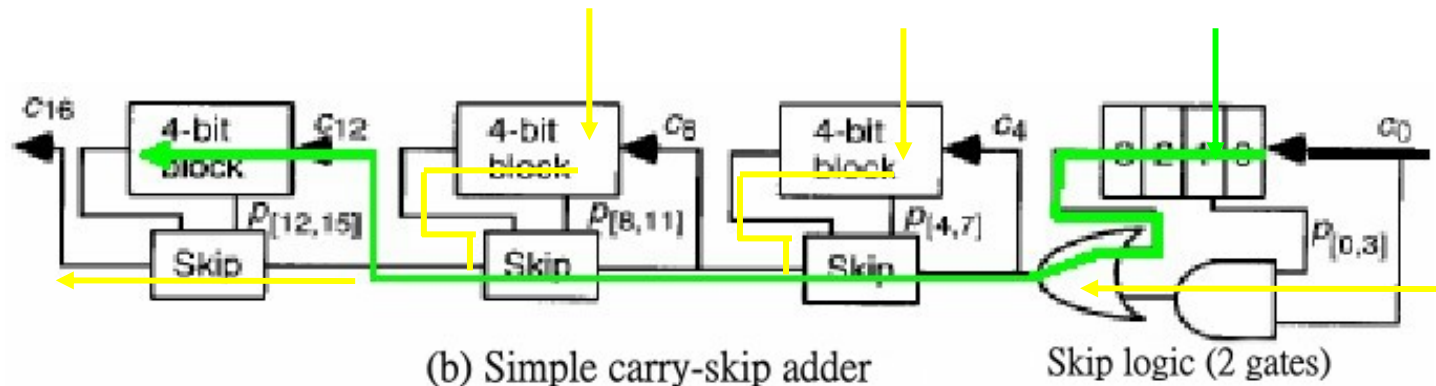

b = fixed block width (ex : 4)

k = number of bits (ex : 16)

$$T_{\text{delay}} = \underbrace{(b-1)}_{\text{block0}} + \underbrace{(0.5)}_{\text{OR-gate}} + \underbrace{(k/b - 2)}_{\text{skips}} + \underbrace{(b-1)}_{\text{block}(k-1)}$$

$$\approx 2b + k/b - 3.5 \text{ stages (ex : 12.5)}$$

- The worst-case delay in stage 0-3: a carry generated in stage 0 and propagated through 1-3.
 - It is $b-1$

What is the optimal block size?

1. set $\frac{dT}{db} = 0$

2. solve for $b = b_{opt}$


$$b_{opt} = \sqrt{\frac{k}{2}}$$

$$t = \text{number of blocks} = k/b$$

$$t_{opt} = \sqrt{2k}$$

$$T_{opt} = 2\sqrt{2k} - 3.5$$

Can we do better?

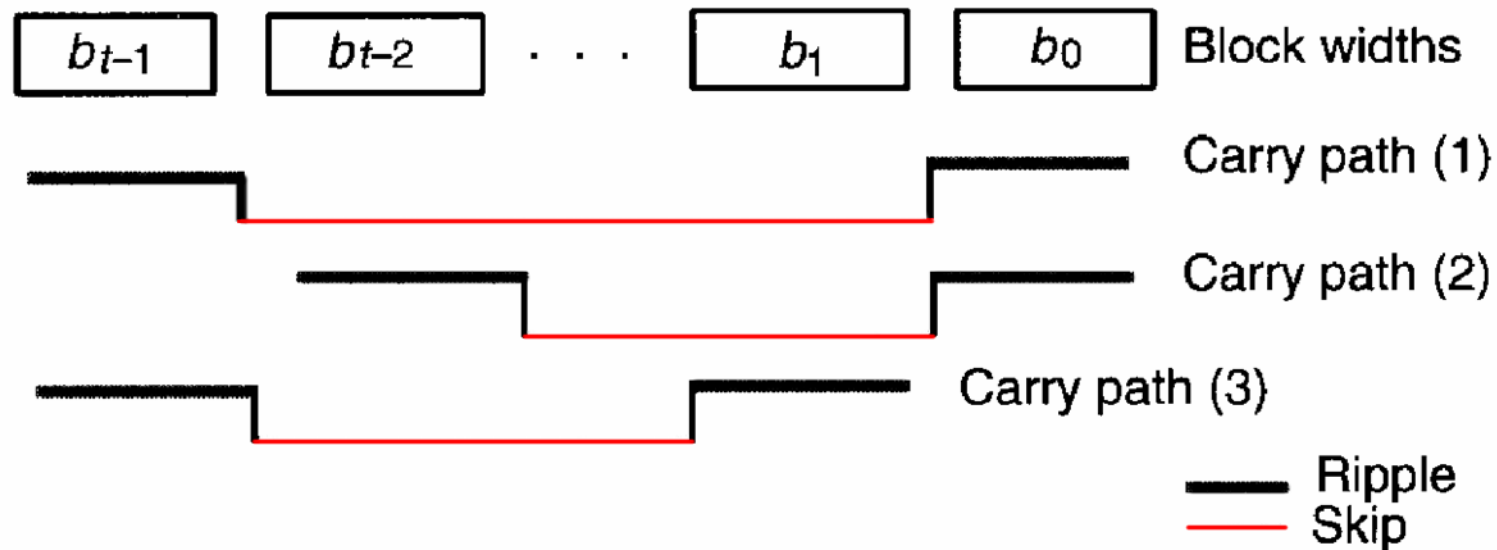


Path (1) is one delay longer than Path (2) \rightarrow
 block $t-2$ can be one bit wider than block $t-1$.

Path (1) is one delay longer than Path (3) \rightarrow
 block 1 can be one bit wider than block 0 .

Variable Block-Width Carry-Skip Adders

Optimal Block Widths :

 

$$b + (b+1) + \dots + (b + \frac{t}{2} - 1) + (b + \frac{t}{2} - 1) + \dots + (b+1) + b = k$$

$$\rightarrow b = (k/t) - (t/4) + 1/2$$

Optimal number of blocks

$$T_{delay} = \underbrace{2(b-1)}_{\text{first + last stage}} + \underbrace{(0.5)}_{\text{OR gate}} + \underbrace{(t-2)}_{\text{Skip stages}} = \frac{2k}{t} + \frac{t}{2} - 2.5$$

$$1. \text{ set } \frac{dT}{dt} = 0$$

$$2. \text{ solve for } t = t_{opt}$$

$$t_{opt} = 2\sqrt{k}$$

$$b_{opt} = \lceil 1/2 \rceil = 1 \quad (\text{stage } 0, t-1; \text{ goes up to } t_{opt}/2 = \sqrt{k})$$

$$T_{opt} = 2\sqrt{k} - 2.5$$


Comparison

	Fixed-width Carry-Skip	Variable-width Carry-Skip
t_{opt}	$\sqrt{2k}/2$	$2\sqrt{k}$
b_{opt}	$\sqrt{k}/2$	$1 \cdots \sqrt{k} \quad \sqrt{k} \cdots 1$
T_{opt}	$2\sqrt{2k} - 3.5$	$2\sqrt{k} - 2.5$


Conclusion: Variable-width is about 40% faster.

Multilevel Carry-Skip Adders



❑ One-level carry-skip adder

 

❑ Two-level carry-skip adder

 

Multilevel Carry-Skip Adders

  


Multilevel Carry-Skip Adders


- ❑ Allow carry to skip over several level-1 skip blocks at once.
- ❑ Level-2 propagate is AND of level-1 propagates.
- ❑ Assumptions:
 - OR gate is no delay (insignificant delay)
 - Basic delay = Skip delay = Ripple delay
= Propagate Computation = Sum Computation

Simplifying the Circuit

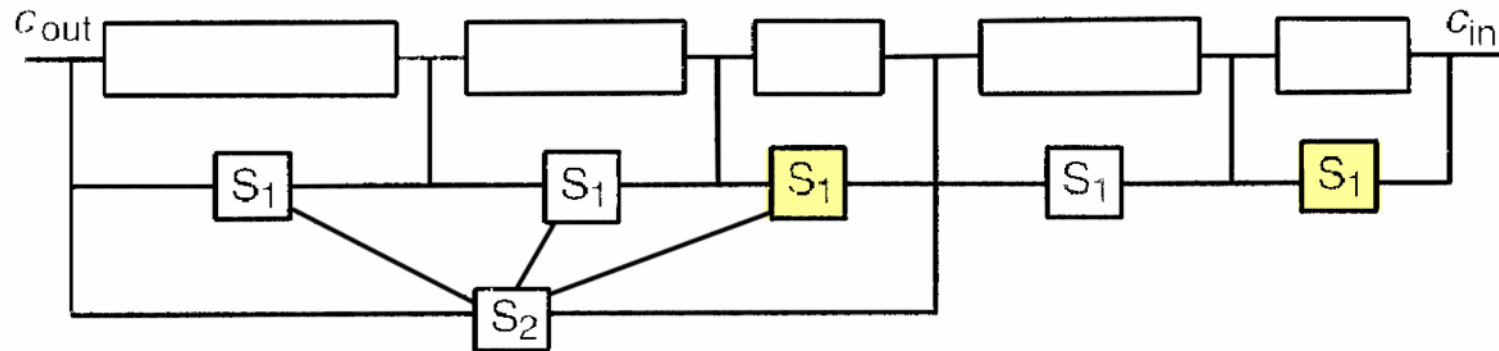
It doesn't save any time to skip short carry-chains (1-2 cells long)



optimized

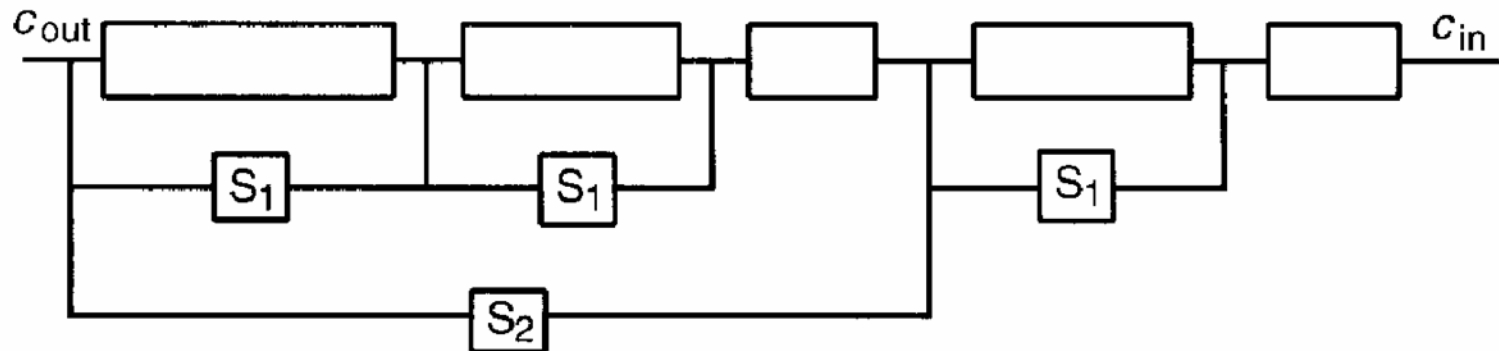

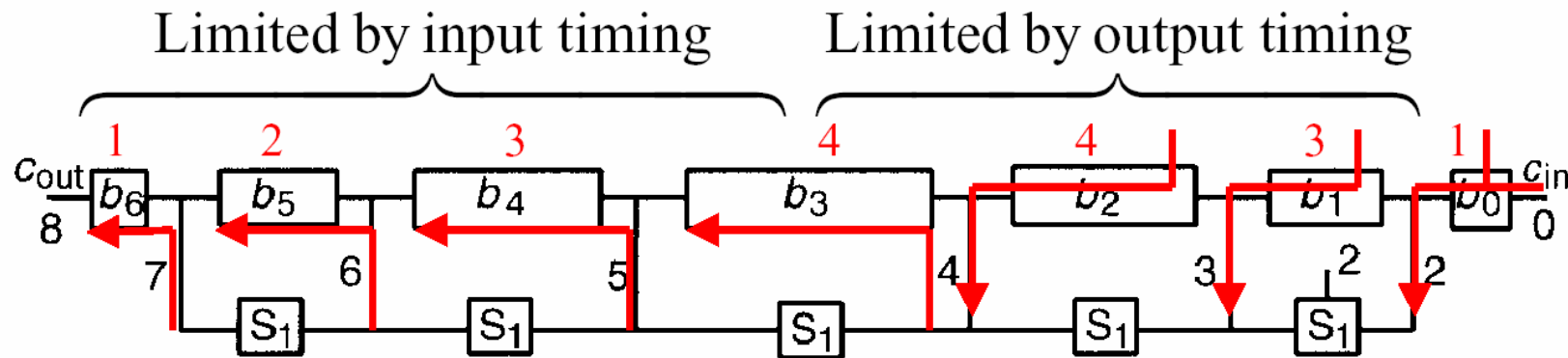
Build the Widest Single-Level Carry-Skip Adder with 8 delays max



$$Width = 1 + 3 + 4 + 4 + 3 + 2 + 1 = 18 \text{ bits}$$


Build the Widest Two-Level Carry-Skip Adder with 8 delays max

First, we need a new notation:

 

8-delay, 2-level, continued

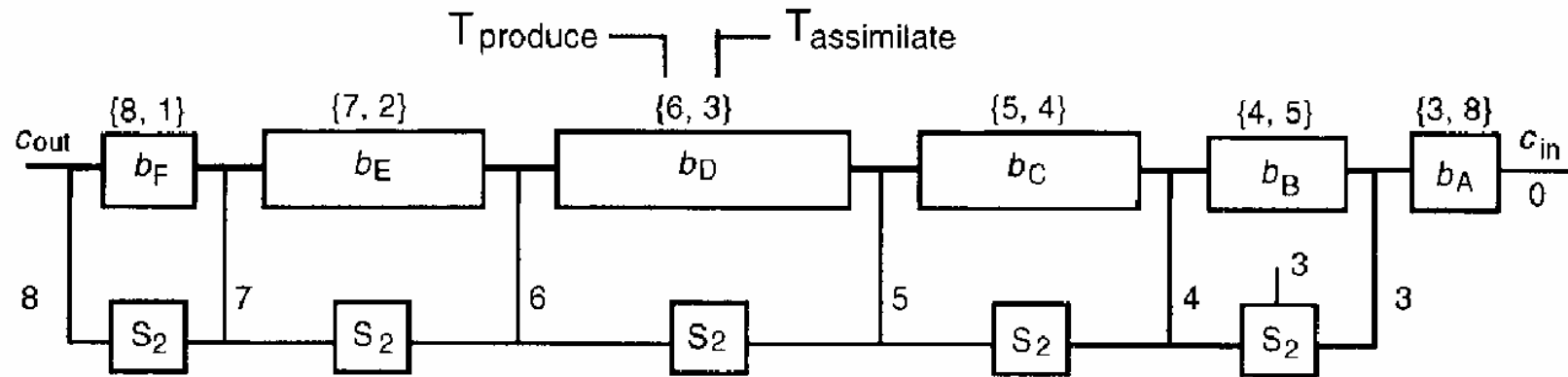
1. Find $\{\beta, \alpha\}$ for level two



Initial Timing Constraint, Level 2

8-delay, 2-level, continued

 
2. Given $\{\beta, \alpha\}$ for level two, derive level one



Block	T_{produce}	$T_{\text{assimilate}}$	Number of subblocks	Subblock widths (bits)	Block Width (bits)
A	3	8	2	1, 3	4
B	4	5	3	2, 3, 3	8
C	5	4	4	2, 3, 2, 1	8
D	6	3	3	3, 2, 1	6
E	7	2	2	2, 1	3
F	8	1	1	1	1


Generalization

 - ❑ • Chan et al. [1992] relax assumptions to include general worst-case delays:
 - $I(b)$ Internal carry-propagate delay for the block.
 - $G(b)$ Carry-generate delay for the block.
 - $A(b)$ Carry-assimilate delay for the block.



- ❑ Used dynamic programming to obtain optimal configuration.

Carry-Select Adders

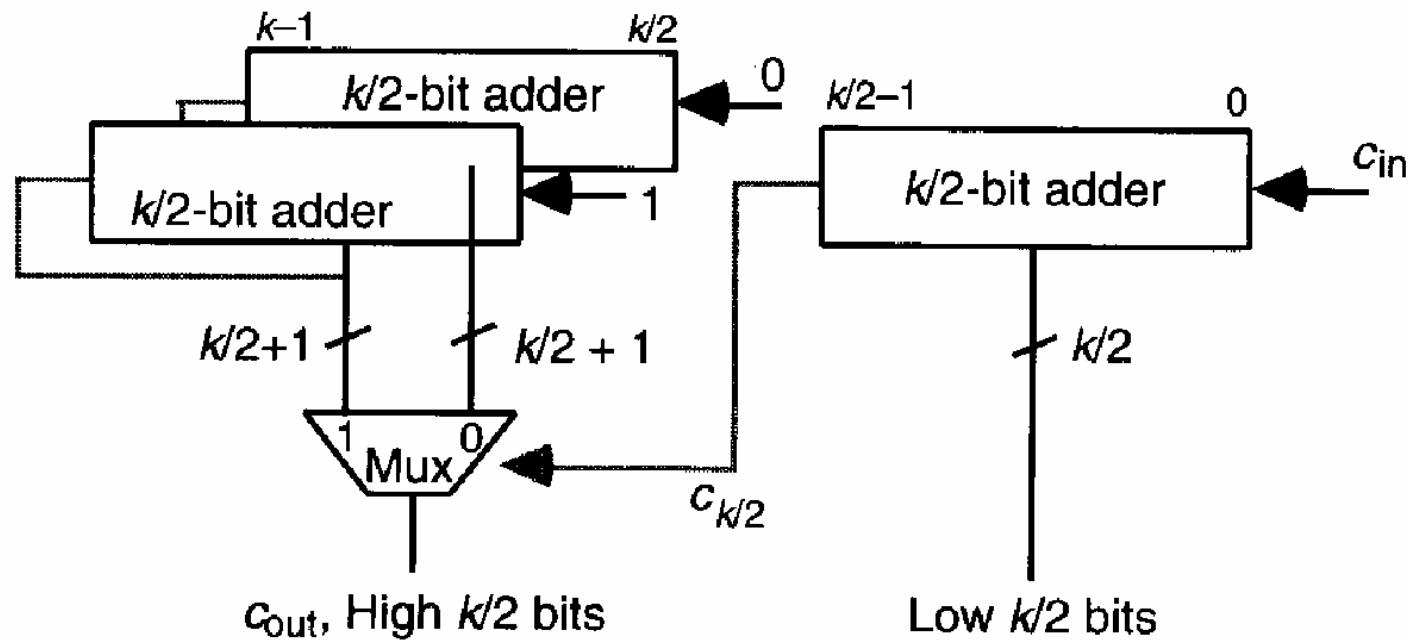


$$C_{\text{select-add}}(k) = 3C_{\text{add}}(k/2) + k/2 + 1$$


$$T_{\text{select-add}}(k) = T_{\text{add}}(k/2) + 1$$

Carry-select: Carried one step further

Two-Level Carry-Select Adder

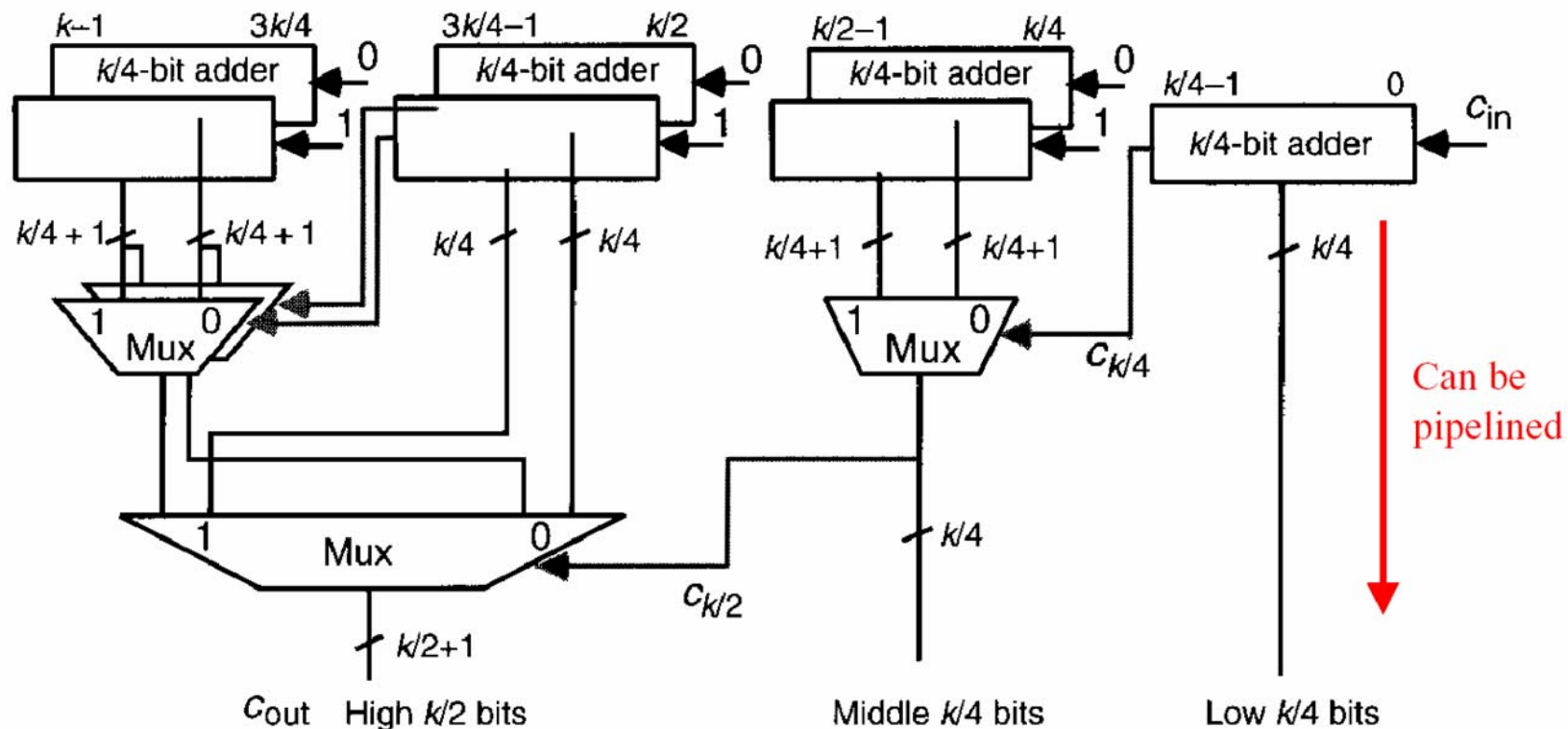

Compare to Two-Level G-P Adder

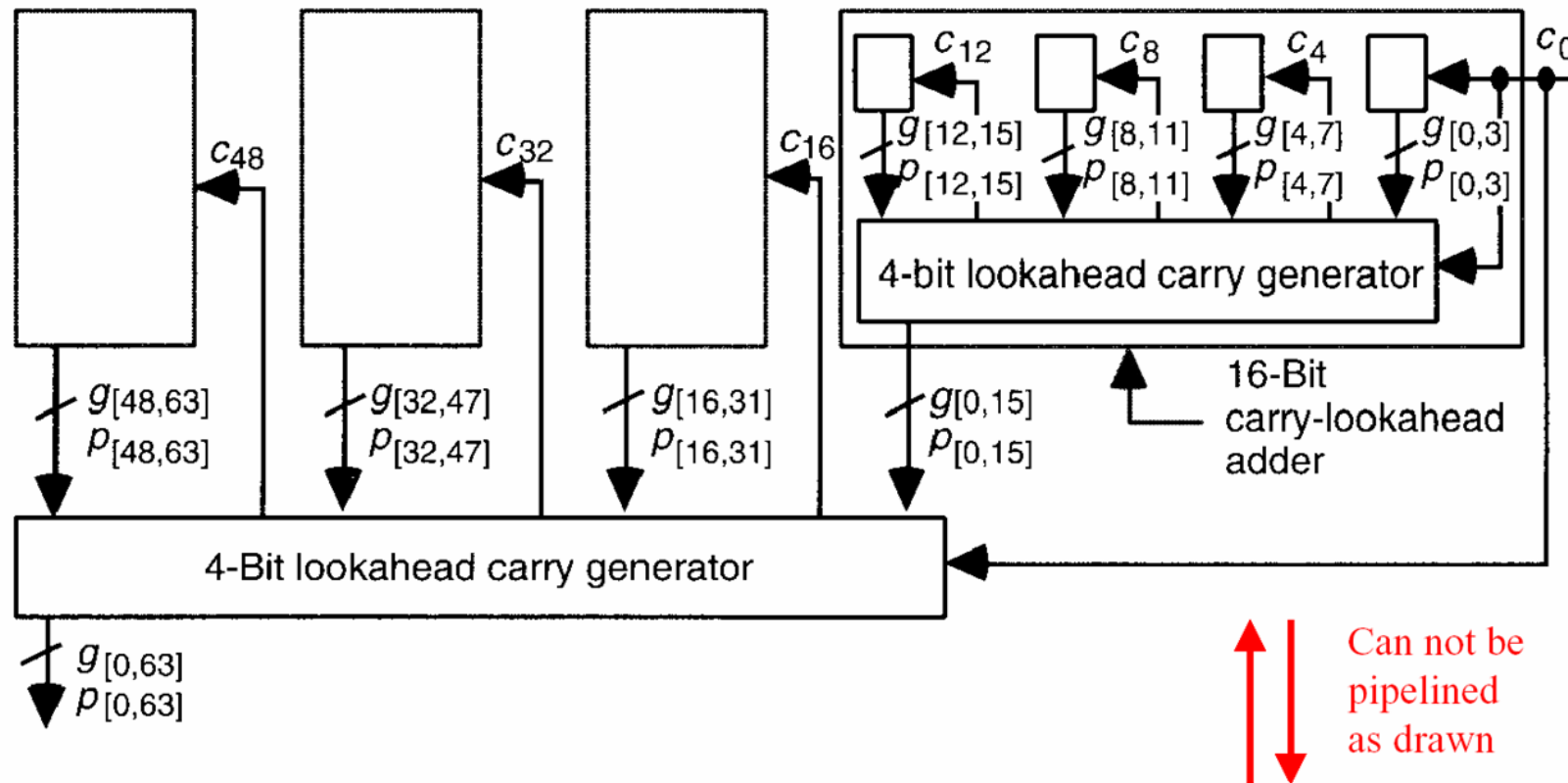

Conditional Sum Adder


- ❑ The process that led to the two-level carry select adder can be continued . . .
- ❑ A logarithmic time *conditional-sum adder* results if we proceed to the extreme:
 - single bit adders at the top.
- ❑ A conditional-sum adder is actually a $(\log_2 k)$ -level carry-select adder.

Cost and Delay of a Conditional-Sum Adder

$$C(k) \approx 2C(k/2) + k + 2 \approx k(\log_2 k + 2) + kC(1)$$

$$T(k) = T(k/2) + 1 = \log_2 k + T(1)$$

 More exact analysis gives actual cost = $(k - 1)(\log_2 k + 1) + kC(1)$



Top-level block for one bit position of a conditional-sum adder

$C(1)$ and $T(1)$ are the cost and time delay of this circuit.

Conditional-Sum Example

		x	0	0	1	0	0	1	1	0	1	1	1	0	1	0	1	0	1	0
		y	0	1	0	0	1	0	1	1	0	1	1	0	1	1	1	1	0	1
Block width	Block carry-in	Block sum and block carry-out																		C_{in}
		15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0			
1	0	s	0	1	1	0	1	1	0	1	1	0	1	1	0	1	0	1	1	1
	c	0	0	0	0	0	0	1	0	0	0	1	0	0	1	0	0	1	0	0
1	1	s	1	0	0	1	0	0	1	0	0	1	0	0	1	0	0	1	0	
	c	0	1	1	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	
2	0	s	0	1	1	0	1	1	0	1	0	0	1	1	0	1	1	1	1	
	c	0		0		0		1		1		0		0		1		0		
1	1	s	1	0	1	1	0	0	1	0	0	1	0	0	1	0	0	1	0	
	c	0		0		0		1		1		0		1		1		0		
4	0	s	0	1	1	0	0	0	0	1	0	0	1	1	0	1	1	1	1	
	c	0				1					1				1			1		
1	1	s	0	1	1	1	0	0	1	0	0	1	0	0						
	c	0				1					1				1					
8	0	s	0	1	1	1	0	0	0	1	0	1	0	0	0	1	1	1	1	
	c	0									1					1				
1	1	s	0	1	1	1	0	0	1	0										
	c	0																		
16	0	s	0	1	1	1	0	0	1	0	0	1	0	0	0	1	1	1	1	
	c	0																		
1	1	s																		
	c																			
			C_{out}																	

Hybrid Adder Designed

- ❑ Hybrids are obtained by combining elements of:
 - Ripple-carry adders.
 - Carry-lookahead (generate-propagate) adders.
 - Carry-skip adders.
 - Carry-select adders.
 - Conditional-sum adders.
- ❑ You can obtain adders with
 - higher performance.
 - greater cost-effectiveness.
 - lower power consumption.


Example 1

Carry-Select / Carry-Lookahead

- ❑ One- and Two-level carry select adders are essentially hybrids, since the top level $k/2$ - or $k/4$ -bit adders can be of any type.
- ❑ Often combined with carry-lookahead adders.


Example 2

Carry-Lookahead/Carry-Select

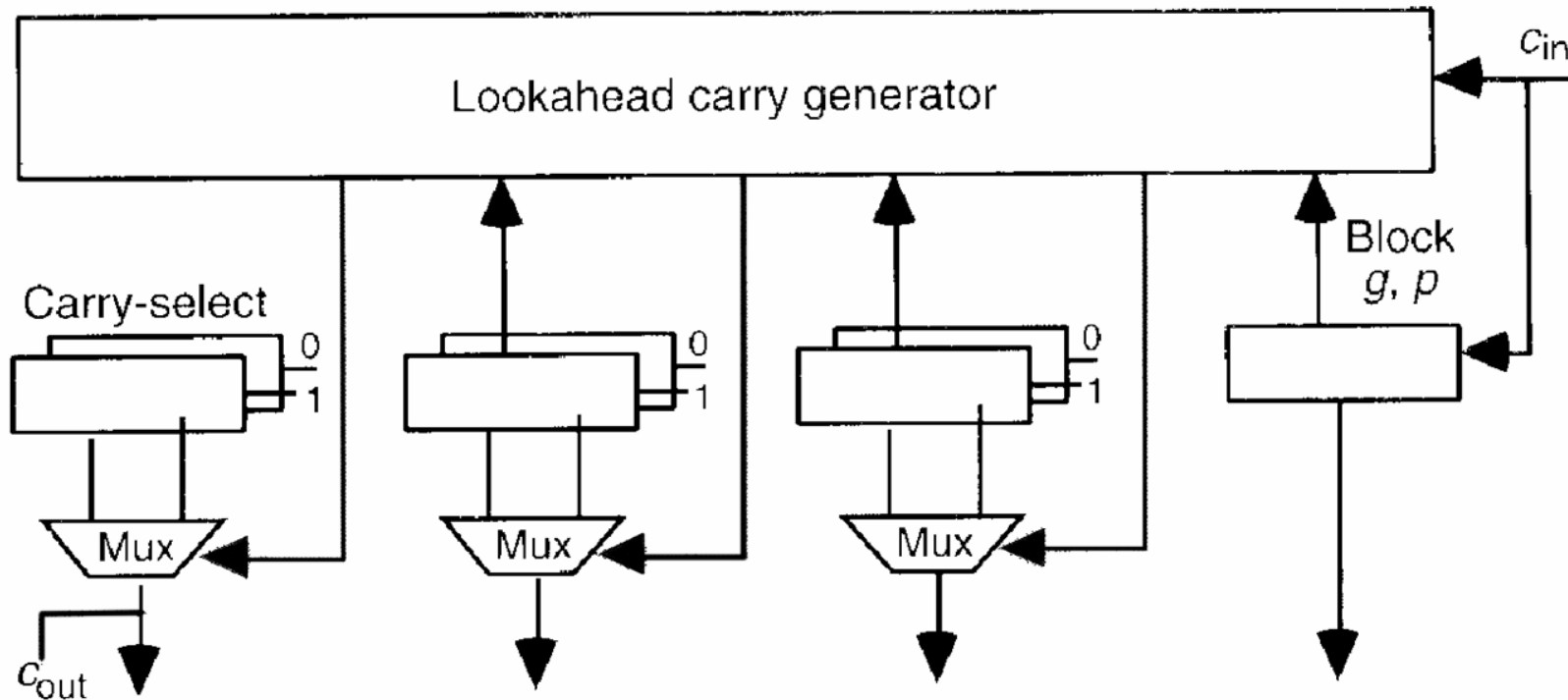


Example 3

Multilevel Carry-Lookahead/Carry-Select

 

Example 4

Ripple-Carry/Carry-Lookahead

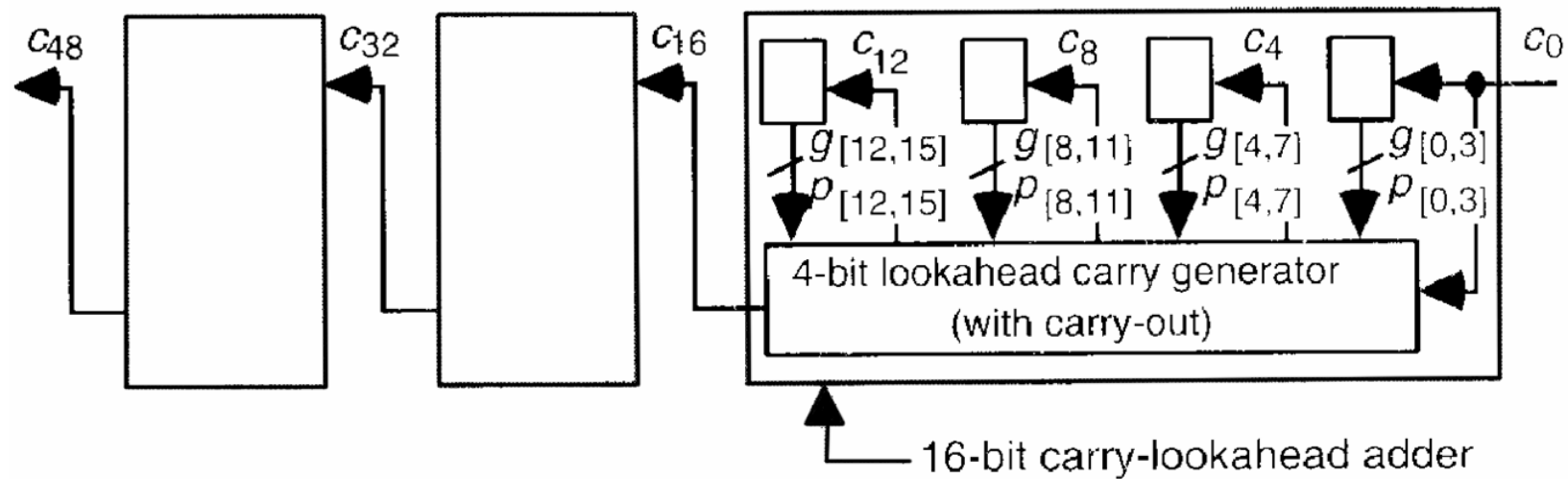

Simple and modular

Example 5

Carry Lookahead/Conditional-Sum

- ❑ Reduces fan-out required to control the muxes at the lower level (a draw-back of wide conditional sum adders).
- ❑ Use carry conditional-sum addition in smaller blocks, but form inter-block carries using carry-lookahead.

Open Questions

- ❑ Application requirements may shift the balance in favor of a particular hybrid design.
- ❑ What combinations are useful for:
 - low power addition.
 - addition on an FPGA.

Optimizations in Fast Adders

- ❑ It is often possible to reduce the delay of adders (including hybrids) by optimizing block widths.
- ❑ The exact optimal configuration is highly technology dependent.
- ❑ Designs that minimize or regularize the interconnect may actually be more cost effective than a design with low gate count.

Other Optimizations

- ❑ Assumption: all inputs are available at time zero.
- ❑ But, sometimes that is not true:
 - I/O arrive/depart serially, or
 - Different arrival times are associated with input digits, or
 - Different production times are associated with output digits.
- ❑ Example: Addition of partial products in a multiplier.