

Read/Write Memory Architectures

Dr. Shubhajit Roy Chowdhury,

Centre for VLSI and Embedded Systems Technology,

IIT Hyderabad, India

Email: src.vlsi@iiit.ac.in




Dr. Shubhajit Roy Chowdhury

CVES, IIT HYDERABAD



Registers

 - Used for storing data
- Structure
 - N-bit wide
 - Parallel/serial read/write
 - Clocked
 - Static/dynamic implementation
- Register files
 - Multiple read/write ports possible
 - Example: 32-bit wide by 16-bit deep, dual-port parallel read, single port parallel write register file




Implementing Registers in CMOS

  - Direct gate implementation too costly
 - A master-slave JK flip-flop uses 38 CMOS transistors
- Directly implement in transistors
 - Example: clocked SR FF



Implementing Registers in CMOS (cont.)

 - Another example: D latch (register)
 - Uses transmission gate
 - When “WR” asserted, “write” operation will take place
 - Stack D latch structures to get n-bit register



Memory (Array) Design

- Array of bits
- Area very important
 - Memory takes considerable area in processor chips
 - Compaction results in fewer memory chip modules, more on-chip cache
- Timing and power consumption of memory blocks have significant impact on the system
- Different types
 - RAM (SRAM, DRAM, CAM)
 - ROM (PROM, EEPROM, FLASH)





Memory Design (cont.)

- Static vs. dynamic RAM
 - Dynamic needs refreshing
 - Refreshing: read, then write back to restore charge
 - Either periodically or after each read
- Static (SRAM)
 - Data stored as long as supply voltage is applied
 - Large (6 transistors/cell)
 - Fast
- Dynamic (DRAM)
 - Periodic refresh required
 - Small (1-3 transistors/cell)
 - Slower
 - Special fabrication process




Memory Architecture: the Big Picture

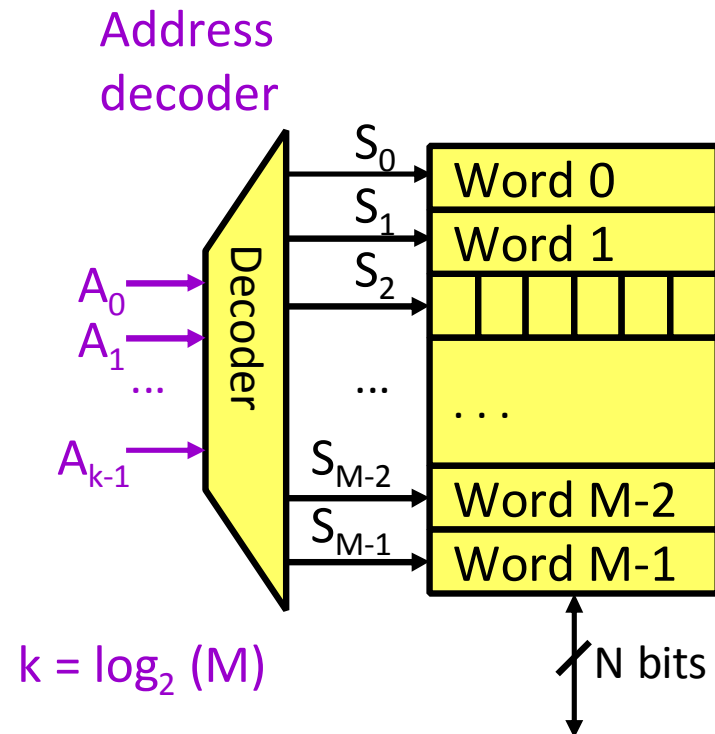 - Address: which one of the M words to access
- Data: the N bits of the word are read/written





Memory Access Timing: the Big Picture

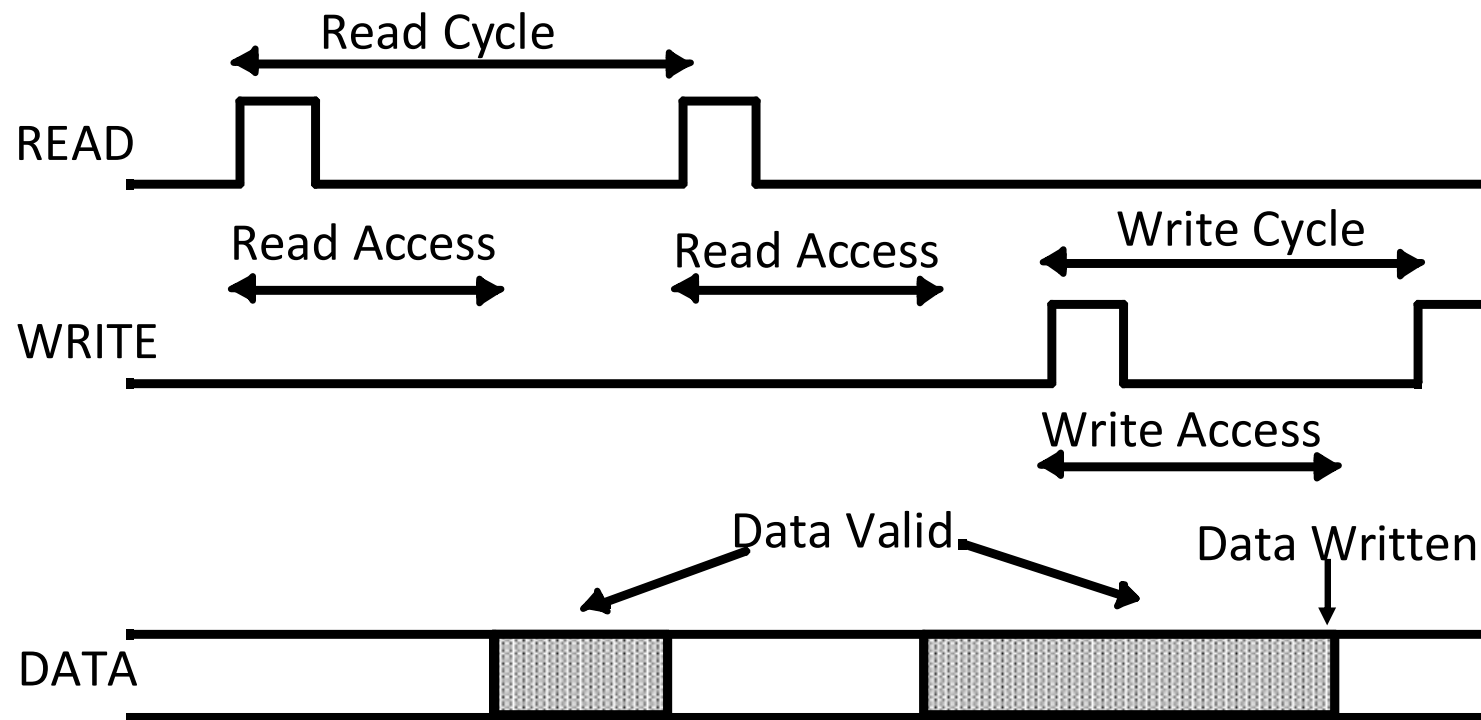- Timing:
 - Send address on the address lines, wait for the word line to become stable
 - Read/write data on the data lines




6-Transistor SRAM Cell: Layout

  - WL is word line (select line S_j)
- BL is bit line (bit_i)





SRAM Read

 - Precharge both bitlines high
- Then turn on wordline
- One of the two bitlines will be pulled down by the cell
- Ex: $A = 0$, $A_b = 1$
 - bit discharges, bit_b stays high
 - But A bumps up slightly
- *Read stability*
 - A must not flip




SRAM Write

  - Drive one bitline high, the other low
- Then turn on wordline
- Bitlines overpower cell with new value
- Ex: $A = 0$, $A_b = 1$, $\text{bit} = 1$, $\text{bit}_b = 0$
 - Force A_b low, then A rises high
- *Writability*
 - Must overpower feedback inverter
 - $N2 \gg P1$




SRAM sizing

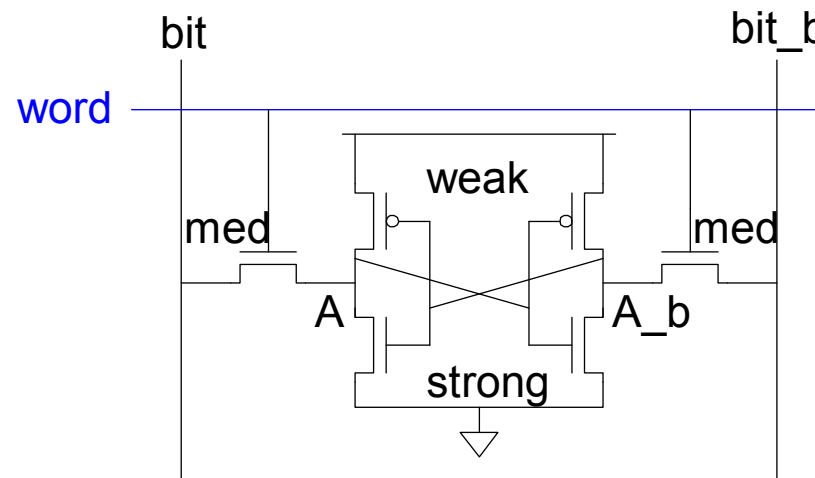- High bitlines must not overpower inverters during reads
- But low bitlines must write new value into cell



6-Transistor Memory Array

 
- 8 words deep RAM, 2 bits wide words
- To write to word j :
 - Set $S_j=1$, all other S lines to 0
 - Send data on the global $\text{bit}_0, \text{bit}_0', \text{bit}_1, \text{bit}_1'$
- To read word k :
 - Set $S_k=1$, all other S lines to 0
 - Sense data on bit_0 and bit_1 .




Decoders

- $n:2^n$ decoder consists of 2^n n -input AND gates
 - One needed for each row of memory
 - Build AND from NAND or NOR gates

Static CMOS

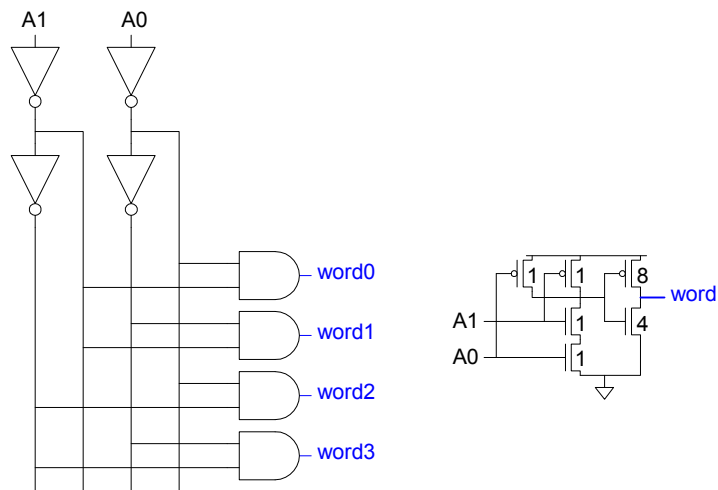


Pseudo-nMOS

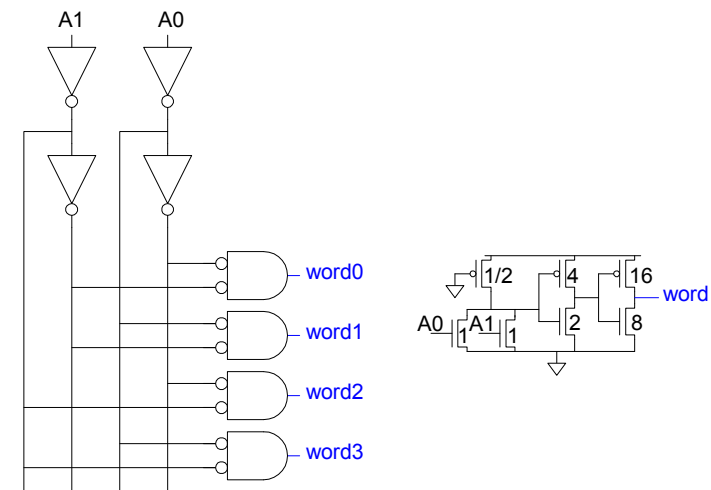


Large Decoders

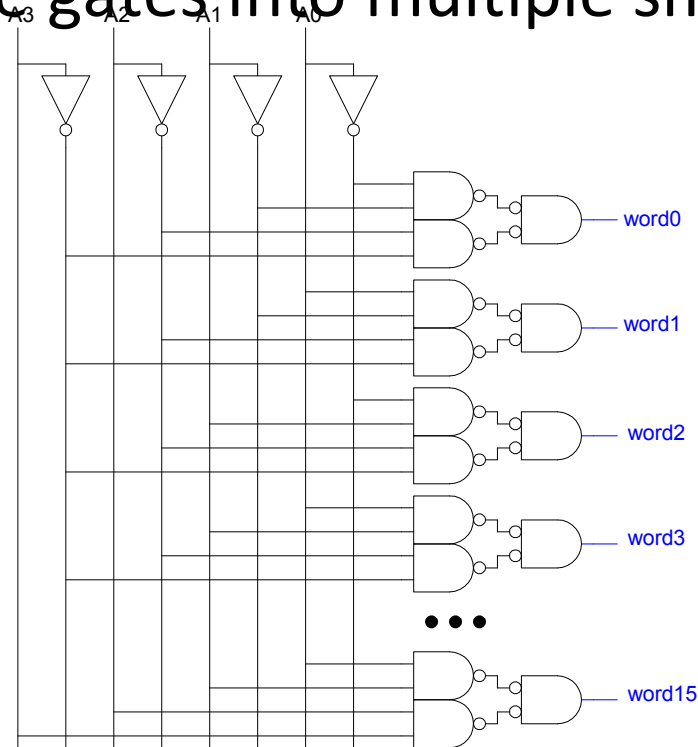- For $n \geq 4$, NAND gates become slow
 - Break large gates into multiple smaller gates



Predecoding

 - Many of these gates are redundant
 - Factor out common gates into predecoder
 - Saves area
 - Same path effort




Column Circuitry

- Some circuitry is required for each column
 - Bitline conditioning
 - Sense amplifiers
 - Column multiplexing




Bitline Conditioning

- Precharge bitlines high before reads

 

 - Equalize bitlines to minimize voltage difference when using sense amplifiers




Sense Amplifiers

- Bitlines have many cells attached
 - Ex: 32-kbit SRAM has 256 rows x 128 cols
 - 128 cells on each bitline
- $t_{pd} \propto (C/I) \Delta V$
 - Even with shared diffusion contacts, 64C of diffusion capacitance (big C)
 - Discharged slowly through small transistors (small I)
- *Sense amplifiers* are triggered on small voltage swing (reduce ΔV)




Differential Pair Amp

 - Differential pair requires no clock
- But always dissipates static power




Clocked Sense Amp

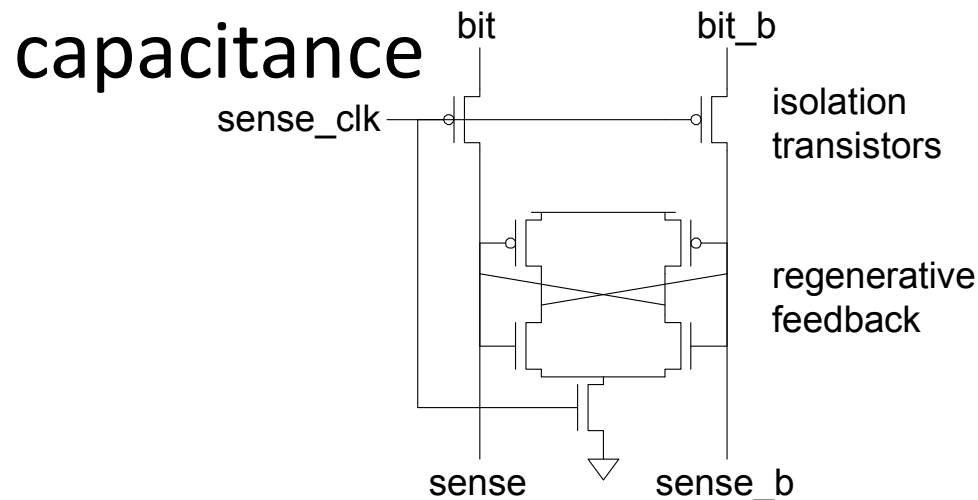- Clocked sense amp saves power
- Requires sense_clk after enough bitline swing
- Isolation transistors cut off large bitline capacitance



Twisted Bitlines

 - Sense amplifiers also amplify noise
 - Coupling noise is severe in modern processes
 - Try to couple equally onto bit and bit_b
 - Done by *twisting* bitlines




Column Multiplexing

- Recall that array may be folded for good aspect ratio
- Ex: 2 kword x 16 folded into 256 rows x 128 columns
 - Must select 16 output bits from the 128 columns
 - Requires 16 8:1 column multiplexers




Tree Decoder Mux

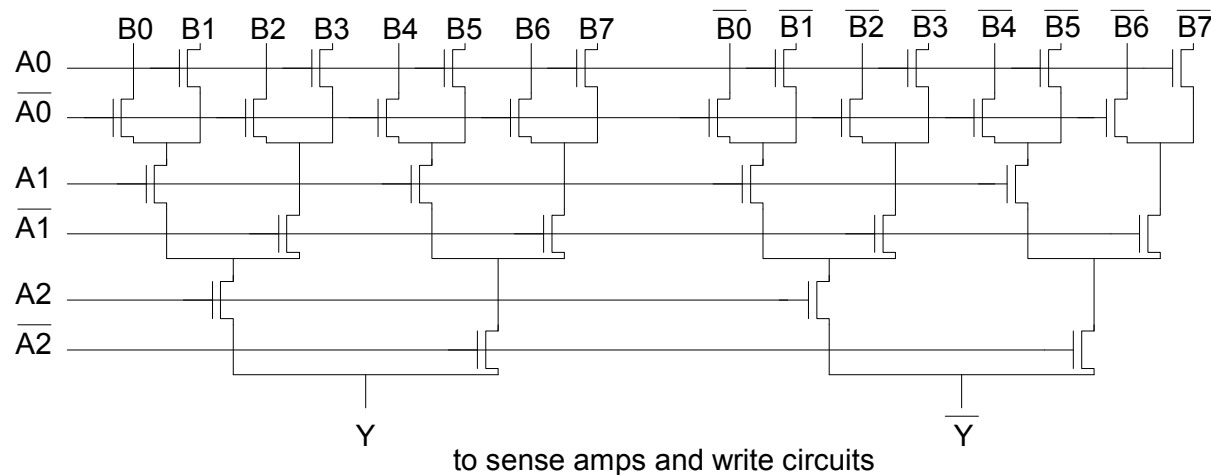- Column mux can use pass transistors
 - Use nMOS only, precharge outputs
- One design is to use k series transistors for $2^k:1$ mux
 - No external decoder logic needed



Single Pass-Gate Mux

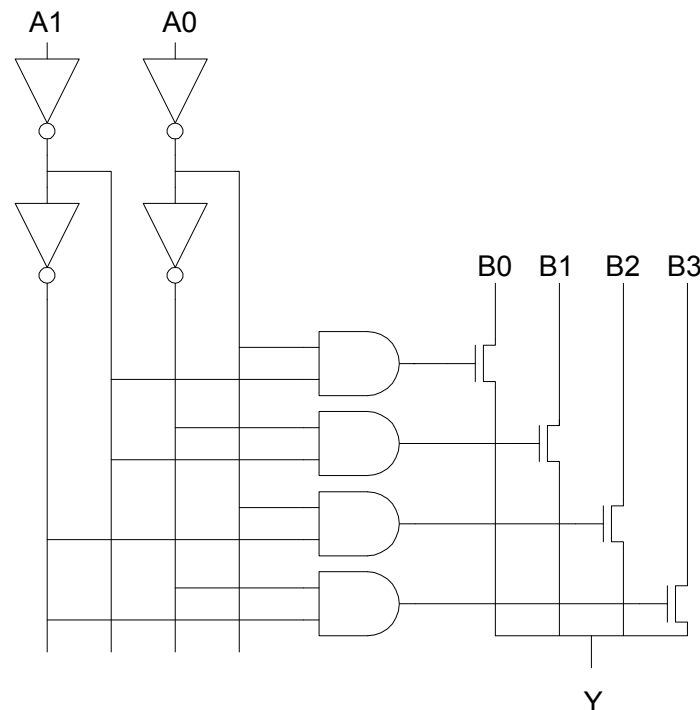- Or eliminate series transistors with separate decoder




Multiple Ports

- We have considered single-ported SRAM
 - One read or one write on each cycle
- *Multiported* SRAM are needed for register files
- Examples:
 - Multicycle MIPS must read two sources or write a result on some cycles
 - Pipelined MIPS must read two sources and write a third result each cycle
 - Superscalar MIPS must read and write many sources and results each cycle



Multi-Port SRAM Cells

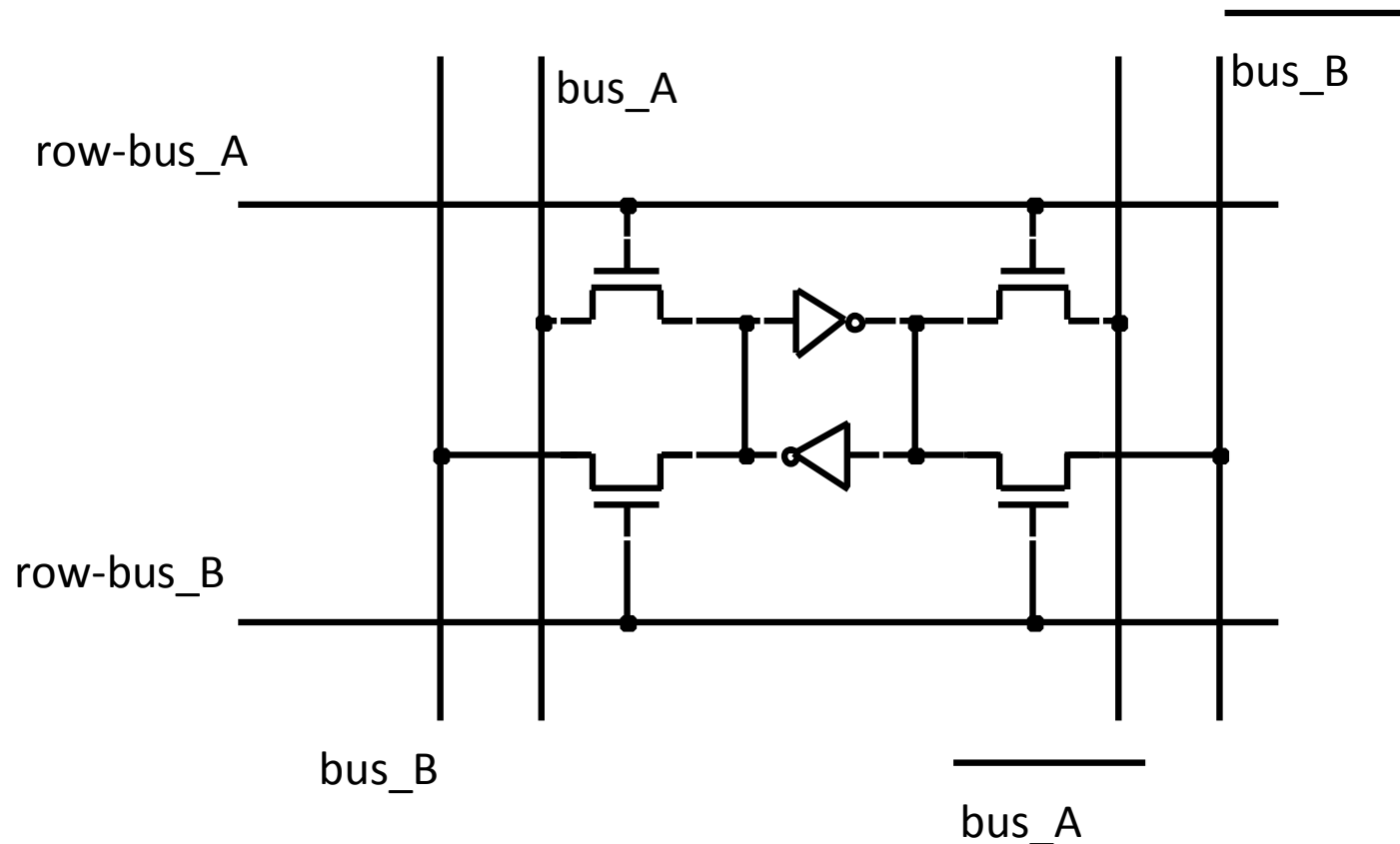


- Idea: add more input and output transistors
- Can be applied to all variants
 - Usually not done for 1T cells




Multi-Port SRAM Cells Array

 - 7 words deep, 2 wide words, dual port mem
- To read from word j and write " d_1d_0 " to word k simultaneously:
 - Set $SA_j=1$, and all other SA 's=0
 - Set $SB_k=1$, and all other SB 's=0
 - Sense the values on bus_A0 and bus_A1
 - Write d_1d_0 to bus_B0 and bus_B1





Dynamic RAM 1-Transistor Cell

 - 1-transistor cell
 - Storage capacitor is source of cell transistor
 - Special processing steps to make the storage capacitor large
 - Charge sharing with bus capacitance ($C_{\text{cell}} \ll C_{\text{bus}}$)
 - Extra demand on sense amplifier to detect small changes
 - Destructive read (must write immediately)



Dynamic RAM 1-Transistor Cell: Timing

 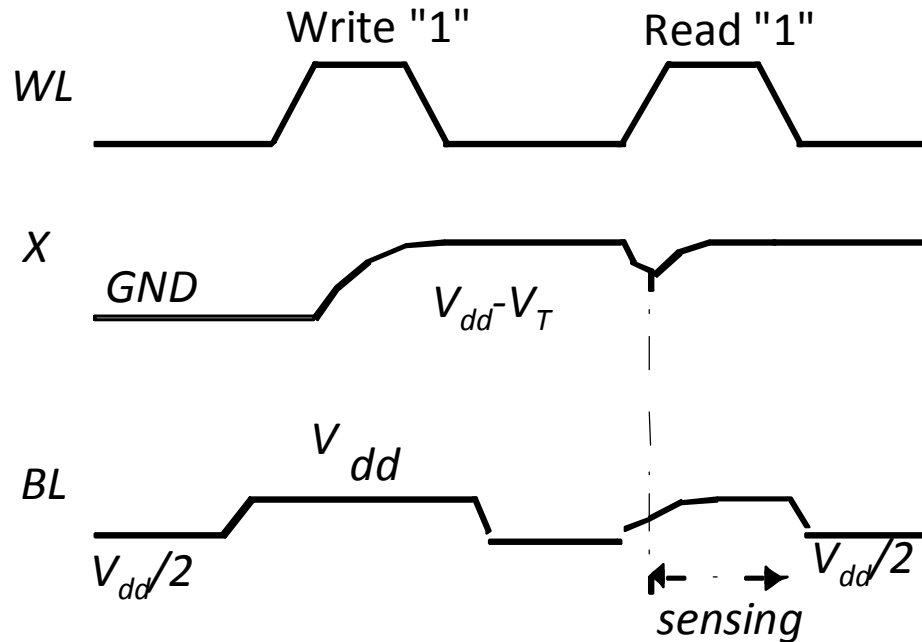

- Write: C_s is charged/discharged
- Read
 - Voltage swing is small (~ 250 mV)
 - $$\Delta V = V_{BL} - V_{PRE} = (V_X - V_{PRE}) \cdot C_s / (C_s + C_{BL})$$




Dynamic RAM 1-Transistor Cell: Observations

- DRAM memory cell is single-ended
- Read operation is destructive
- 1T cell requires presence of an extra capacitance that must be explicitly included in the design
 - Polysilicon-diffusion plate capacitor
- When writing a “1” into a DRAM cell, a threshold voltage is lost
 - Set WL to a higher value than V_{dd}



Dynamic RAM 1-Transistor Cell: Layout

 


Used Polysilicon-Diffusion Capacitance




Expensive in Area



Dynamic RAM 1-Transistor Cell: Layout

 

Dynamic RAM 1-Transistor Cell: Layout

   

RAM Cells: Summary

- Static
 - Fastest (no refresh)
 - Simple design
 - Right solution for small memory arrays such as register files
- Dynamic
 - Densest: 1T is best and is the way to go for large memory arrays
 - Built-in circuitry to step through cells and refresh (can do more than one word at a time)
 - Sense amplifier needed for fast read operation



THANK YOU



Dr. Shubhajit Roy Chowdhury

CVES^T, IIIT HYDERABAD