

Arithmetic Circuits

Dr. Shubhajit Roy Chowdhury,

Centre for VLSI and Embedded Systems Technology,
IIIT Hyderabad, India

Email: src.vlsi@iiit.ac.in




Dr. Shubhajit Roy Chowdhury

CVEST, IIIT HYDERABAD

Subtractors

 - Two's complement subtraction is easy:
 - Invert the second number and add




Comparators

- ❑ 0's detector: $A = 00\dots000$
- ❑ 1's detector: $A = 11\dots111$
- ❑ Equality comparator: $A = B, A \neq B$
- ❑ Magnitude comparator: $A < B$, etc.




1's and 0's Detector

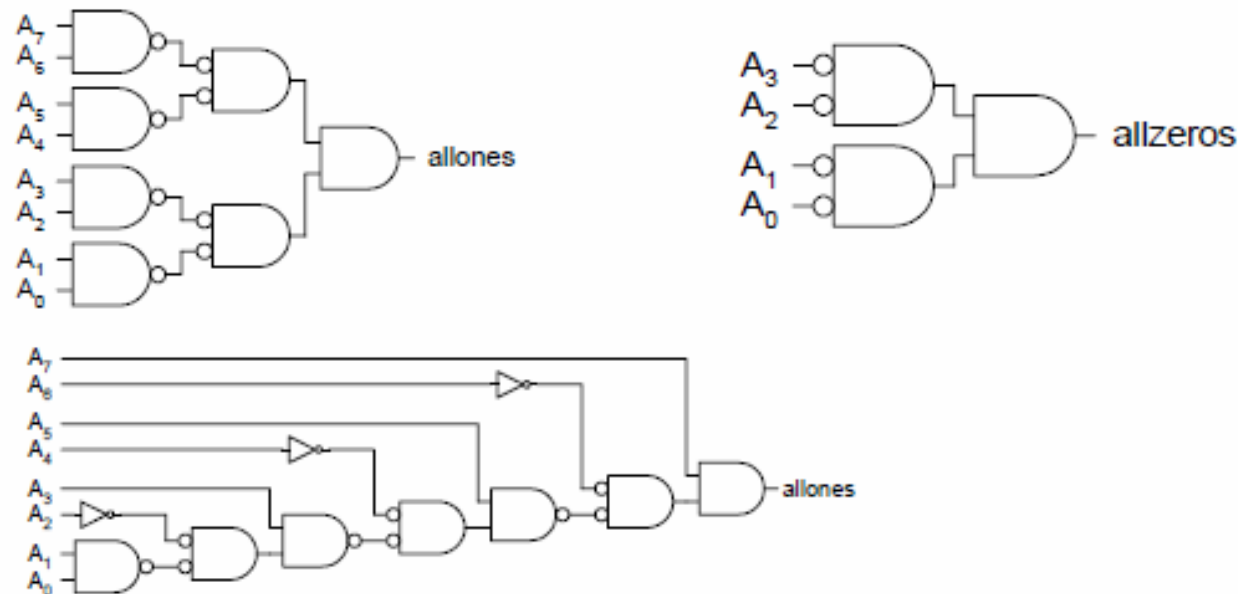- ❑ 1's detector: N-input AND gate
- ❑ 0's detector: NOTs + 1's detector (N-input NOR)




Equality detector

 - ❑ Check if each bit is equal (XNOR, aka equality gate)
- ❑ 1's detect on bitwise equality



Magnitude Comparator

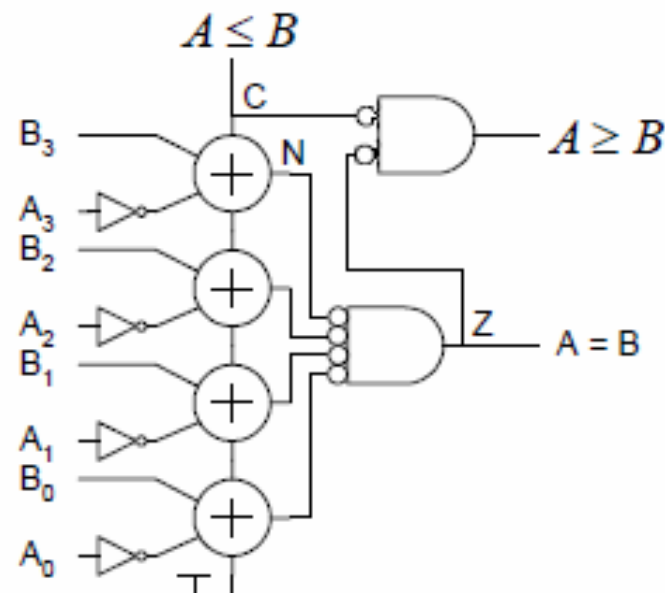- ❑ Compute $B-A$ and look at sign
- ❑ $B-A = B + \sim A + 1$
- ❑ For unsigned numbers, carry out is sign bit



A+B=K Comparison

- ❑ Determining if $A + B = K$ is easier than adding!
- ❑ Knowing bits, determine what carry in would be necessary if the sum is correct

A_i	B_i	K_i	c_{i-1} (required)	c_i (produced)
0	0	0	0	0
0	0	1	1	0
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	1
1	1	1	1	1




A+B=K Comparator Circuit

- Check if actual and required carries are equal

$$c_{i-1}(\text{required}) = A_i \oplus B_i \oplus K_i$$
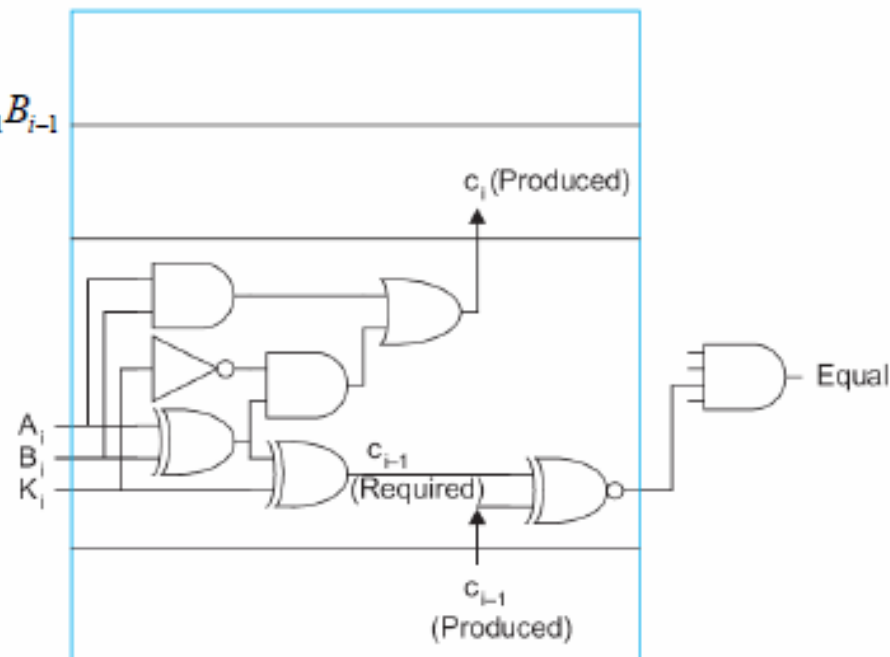
$$c_{i-1}(\text{actual}) = (A_{i-1} \oplus B_{i-1}) \bar{K}_{i-1} + A_{i-1} B_{i-1}$$




Multi-input Adders

- Suppose we want to add k N-bit words
 - Ex: $0001 + 0111 + 1101 + 0010 = \underline{\hspace{2cm}}$




Multi-Input Adders

 - ❑ Suppose we want to add k N -bit words
 - Ex: $0001 + 0111 + 1101 + 0010 = 10111$
- ❑ Straightforward solution: $k-1$ N -input CPAs
 - Large and slow




Carry Save Adders

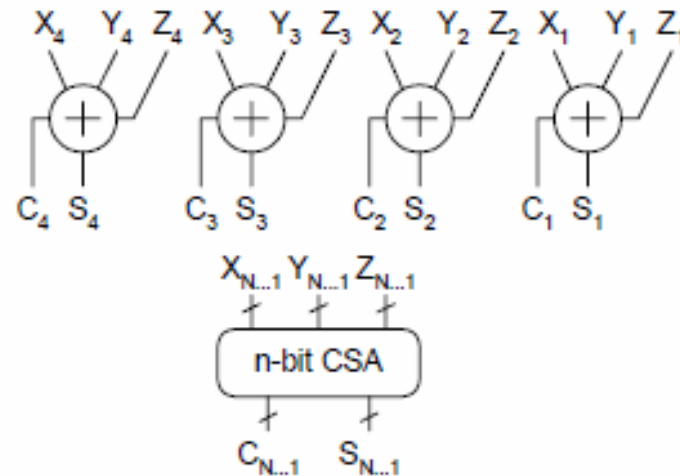- ❑ A full adder sums 3 inputs and produces 2 outputs
 - Carry output has twice *weight* of sum output
- ❑ N full adders in parallel are called *carry save adder*
 - Produce N sums and N carry outs



Carry Save Adders

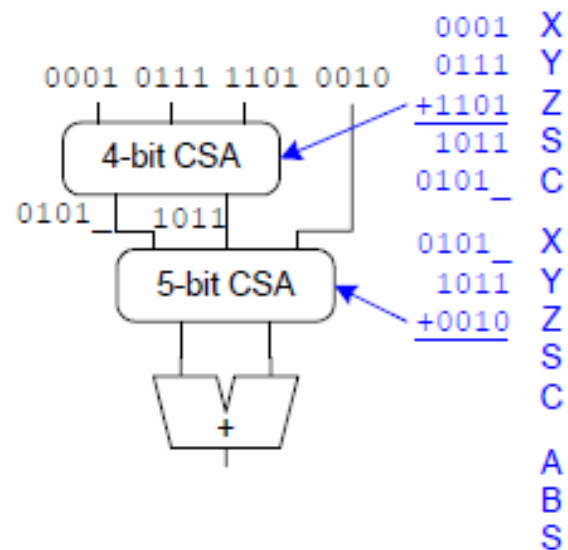- ❑ Use k-2 stages of CSAs
 - Keep result in carry-save redundant form
- ❑ Final CPA computes actual result



Multiplication

□ Example:

$$\begin{array}{rcl} 1100 & : & 12_{10} \\ \underline{0101} & : & 5_{10} \end{array}$$



General Form of Multiplication

❑ **Multiplicand:** $Y = (y_{M-1}, y_{M-2}, \dots, y_1, y_0)$

❑ Multiplier: $X = (x_{N-1}, x_{N-2}, \dots, x_1, x_0)$


Product:
$$P = \left(\sum_{j=0}^{M-1} y_j 2^j \right) \left(\sum_{i=0}^{N-1} x_i 2^i \right) = \sum_{i=0}^{N-1} \sum_{j=0}^{M-1} x_i y_j 2^{i+j}$$

							y_5	y_4	y_3	y_2	y_1	y_0	multiplicand multiplier
							x_5	x_4	x_3	x_2	x_1	x_0	
							x_0y_5	x_0y_4	x_0y_3	x_0y_2	x_0y_1	x_0y_0	partial products
					x_1y_5	x_1y_4	x_1y_3	x_1y_2	x_1y_1	x_1y_0			
			x_2y_5	x_2y_4	x_2y_3	x_2y_2	x_2y_1	x_2y_0					
		x_3y_5	x_3y_4	x_3y_3	x_3y_2	x_3y_1	x_3y_0						
	x_4y_5	x_4y_4	x_4y_3	x_4y_2	x_4y_1	x_4y_0							
x_5y_5	x_5y_4	x_5y_3	x_5y_2	x_5y_1	x_5y_0								product
p_{11}	p_{10}	p_9	p_8	p_7	p_6	p_5	p_4	p_3	p_2	p_1	p_0		




Dot diagram

□ Each dot represents a bit

 


Array Multiplier

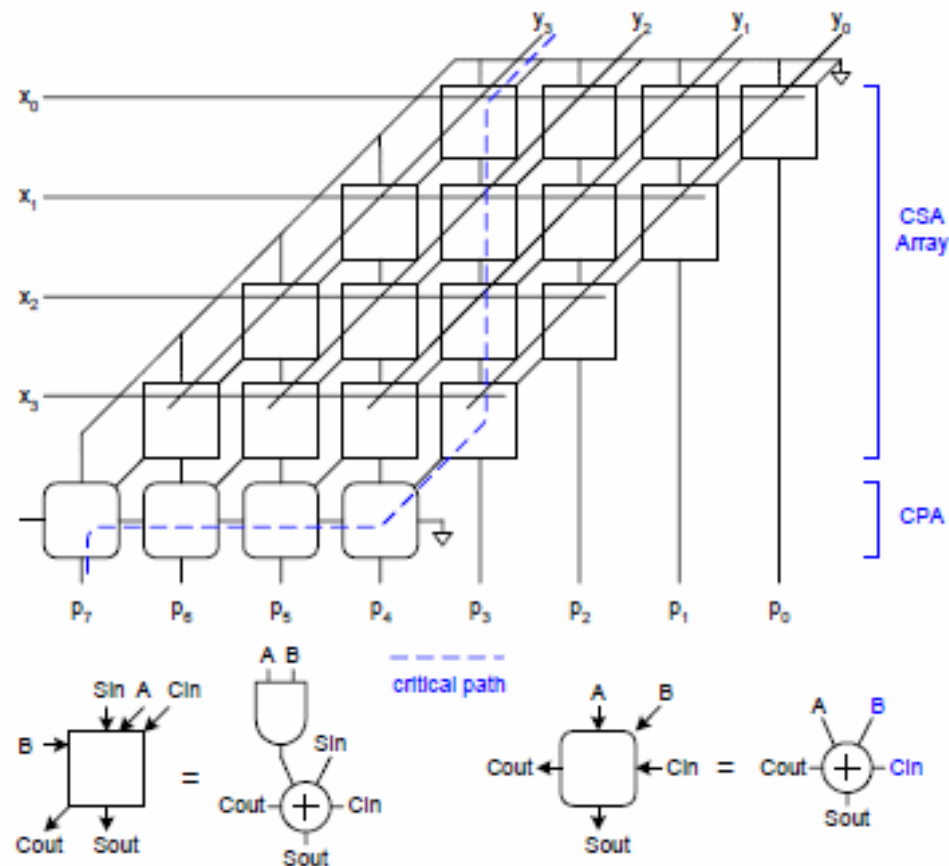

Rectangular Array

 - ❑ Squash array to fit rectangular floorplan



Fewer Partial Products

- ❑ Array multiplier requires N partial products
- ❑ If we looked at groups of r bits, we could form N/r partial products.
 - Faster and smaller?
 - Called radix- 2^r encoding
- ❑ Ex: $r = 2$: look at pairs of bits
 - Form partial products of $0, Y, 2Y, 3Y$
 - First three are easy, but $3Y$ requires adder ☹



Booth Encoding


- ❑ Instead of $3Y$, try $-Y$, then increment next partial product to add $4Y$
- ❑ Similarly, for $2Y$, try $-2Y + 4Y$ in next partial product

Inputs			Partial Product	Booth Selects		
X_{2i+1}	X_{2i}	X_{2i-1}	PP_i	X_i	$2X_i$	M_i
0	0	0	0	0	0	0
0	0	1	Y	1	0	0
0	1	0	Y	1	0	0'
0	1	1	$2Y$	0	1	0
1	0	0	$-2Y$	0	1	1
1	0	1	$-Y$	1	0	1
1	1	0	$-Y$	1	0	1
1	1	1	-0	0	0	1




Booth Hardware

 - Booth encoder generates control lines for each PP
 - Booth selectors choose PP bits




Booth Example

□ 011001 x 100111

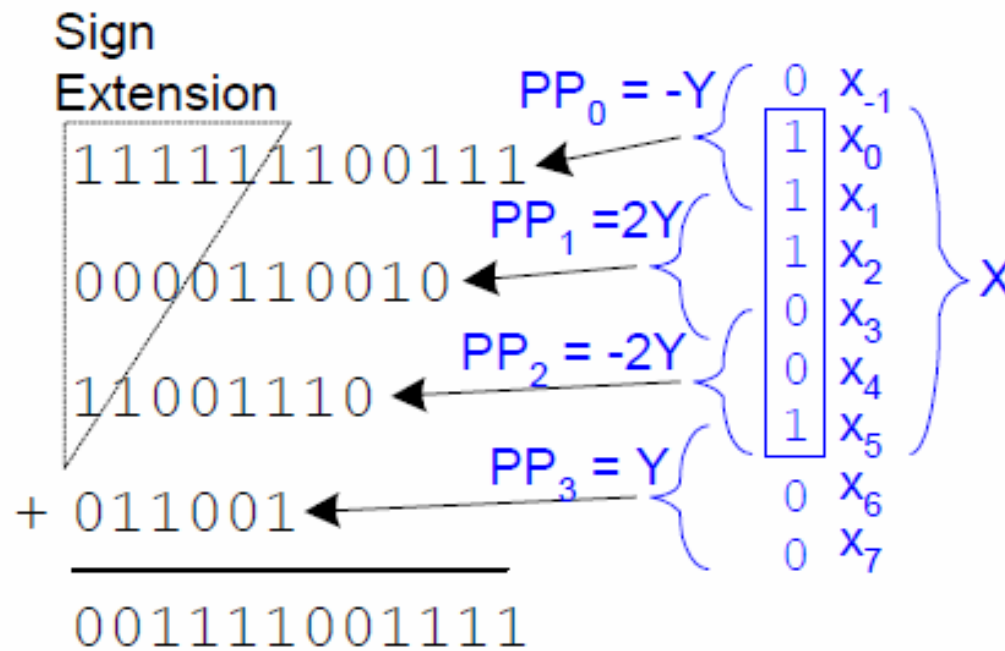


Sign Extension

 - Partial products can be negative
 - Require sign extension, which is cumbersome
 - High fanout on most significant bit




Simplified Sign Extension

 - Sign bits are either all 0's or all 1's
 - Note that all 0's is all 1's + 1 in proper column
 - Use this to reduce loading on MSB



Even simpler sign extension

 - ❑ No need to add all the 1's in hardware
 - Precompute the answer!



Higher Radix Booth Encoding

- Booth-8 reduces partial products by factor of 3
 - Requires +/- 3Y multiples which need a CPA

x_{i+2}	x_{i+1}	x_i	x_{i-1}	Partial Product
0	0	0	0	0
0	0	0	1	Y
0	0	1	0	Y
0	0	1	1	2Y
0	1	0	0	2Y
0	1	0	1	3Y
0	1	1	0	3Y
0	1	1	1	4Y
1	0	0	0	-4Y
1	0	0	1	-3Y
1	0	1	0	-3Y
1	0	1	1	-2Y
1	1	0	0	-2Y
1	1	0	1	-Y
1	1	1	0	-Y
1	1	1	1	-0



Column Addition


- ❑ Add up all the dots in a column in carry-save form
- ❑ Then use CPA to convert to nonredundant binary
- ❑ CSAs act as “1’s counters”

A	B	C	Carry	Sum	Number of 1's
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	0	1	1
0	1	1	1	0	2
1	0	0	0	1	1
1	0	1	1	0	2
1	1	0	1	0	2
1	1	1	1	1	3




Array multiplier CSAs

 - N-2 CSAs to sum N partial products
 - Ex: 16 x 16 Booth-4 multiplier with 9 PPs
 - Remember carries actually cross columns




Wallace Tree

 - ❑ Reduce number of levels using a tree
 - $\log_{3/2} N$ levels



 
4:2 Compressor

- ❑ Wallace tree routing is irregular and long
 - Use 4:2 compressors instead




Compressor Design

 - ❑ 3:2 CSA
 - 2 XOR delays
 - X is fast input
 - C is fast output




- ❑ 4:2 Compressor
 - 2 3:2 CSAs
 - Note horizontal carry t

 


Improved 4:2 Compressor

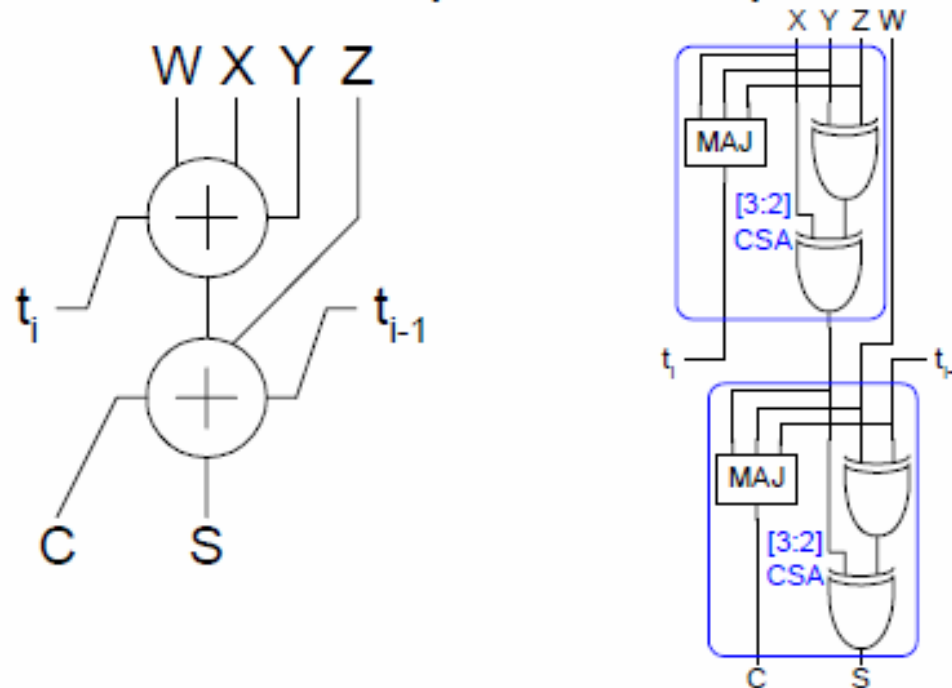- ❑ Arrange inputs carefully for only 3 XOR delays
 - Connect slow output to fast input




5:3 Compressor

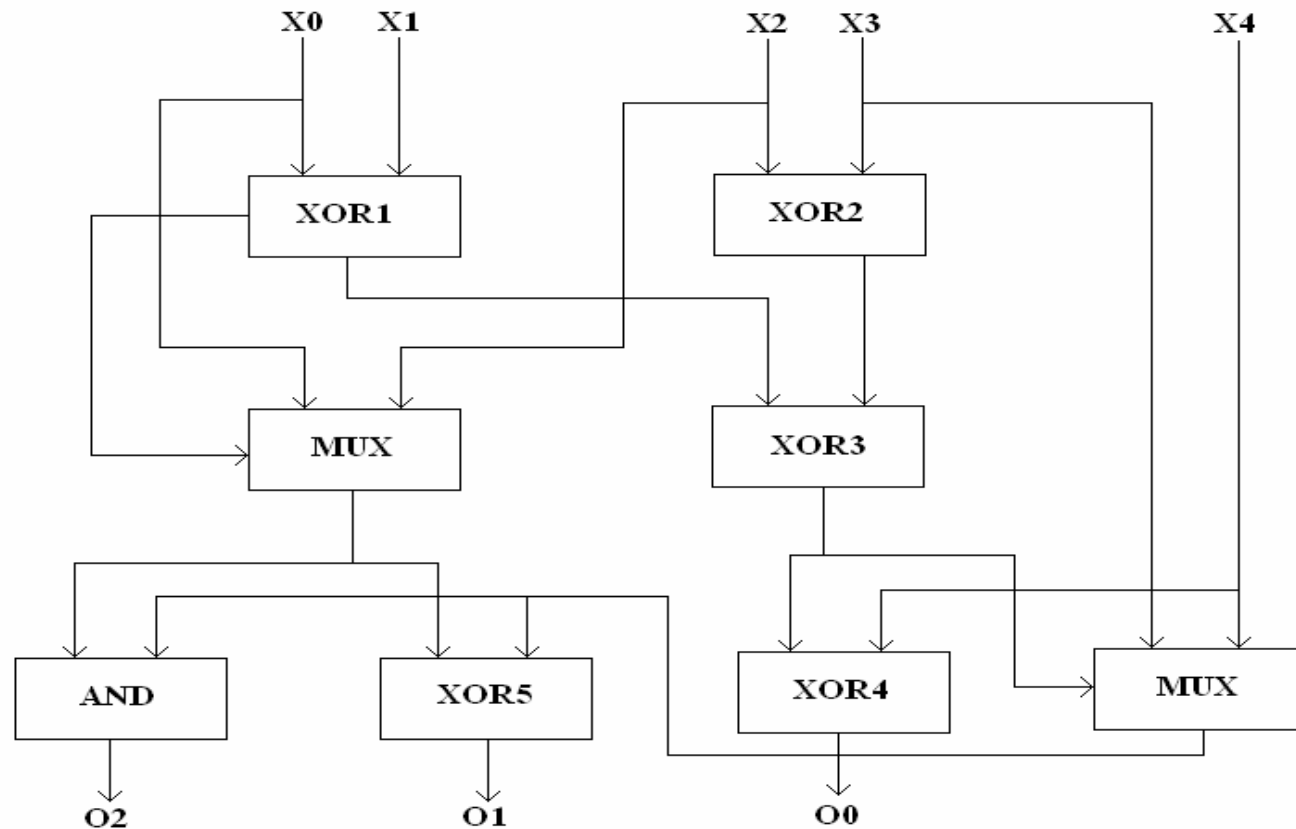

S. Roy Chowdhury, A. Banerjee, A. Roy, H. Saha, IEEE VDAT 2008




15:4 Compressor

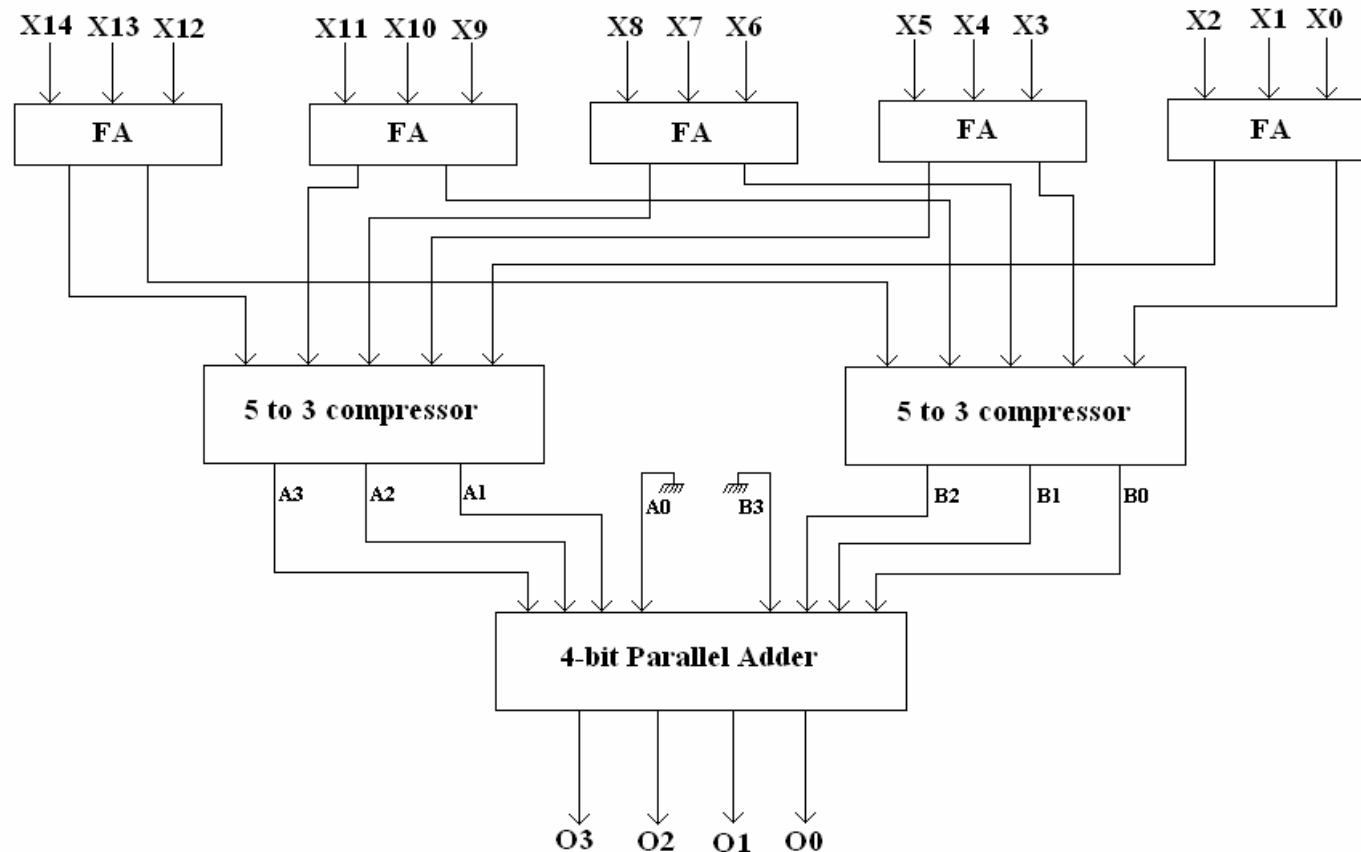

S. Roy Chowdhury, A. Banerjee, A. Roy, H. Saha, IEEE VDAT 2008



Multiplier Floorplans

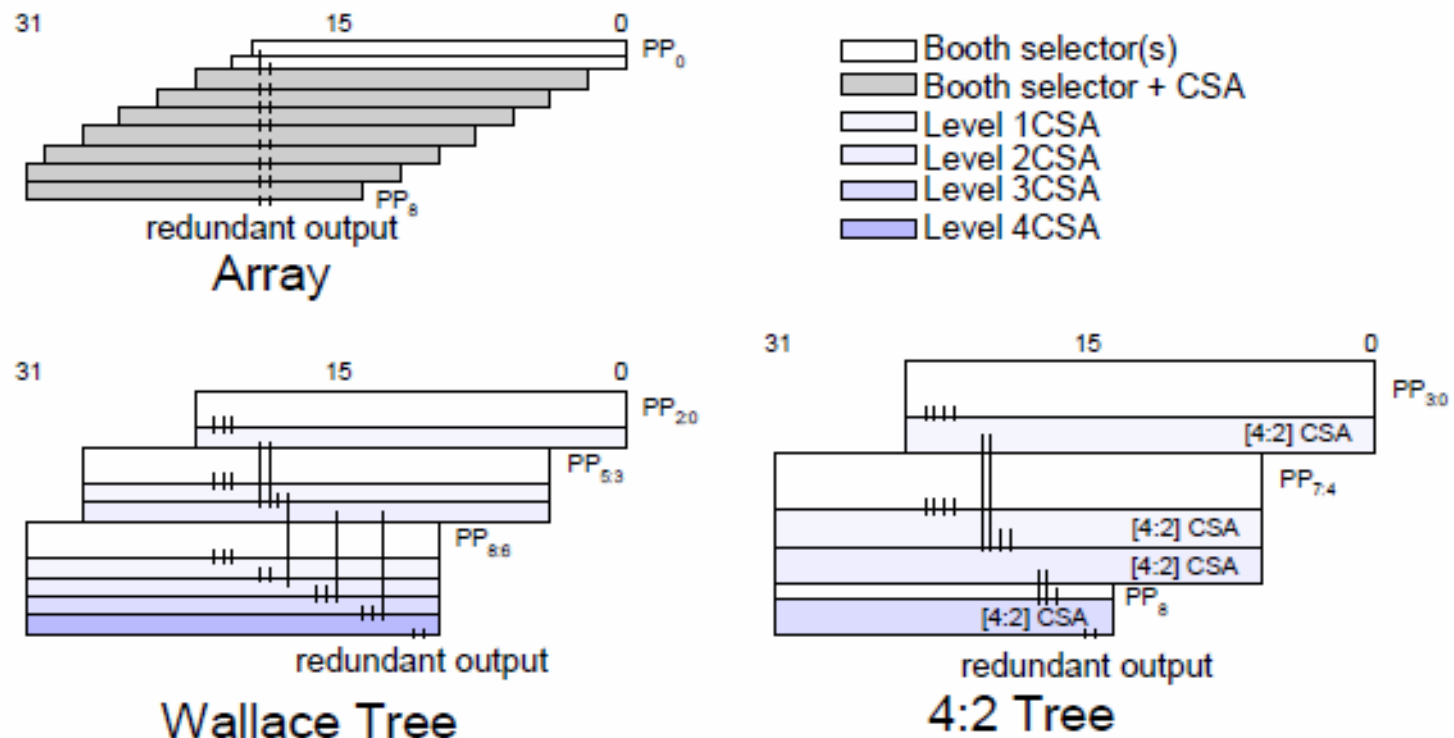


Comparison of different multiplier architectures

- ❑ Arrays
 - + shortest wiring
 - + most compact layout
 - Most levels of CSAs
- ❑ Wallace tree
 - + fewest levels of CSAs
 - not fewest levels of XORs
 - long, irregular wiring
- ❑ 4:2 Trees
 - + nearly minimal levels of XORs
 - + few irregular wires




Final Addition

 - Take advantage of irregular arrival times
 - First and last columns have fewer PPs
 - Reduce power of noncritical early inputs



Serial Multiplication

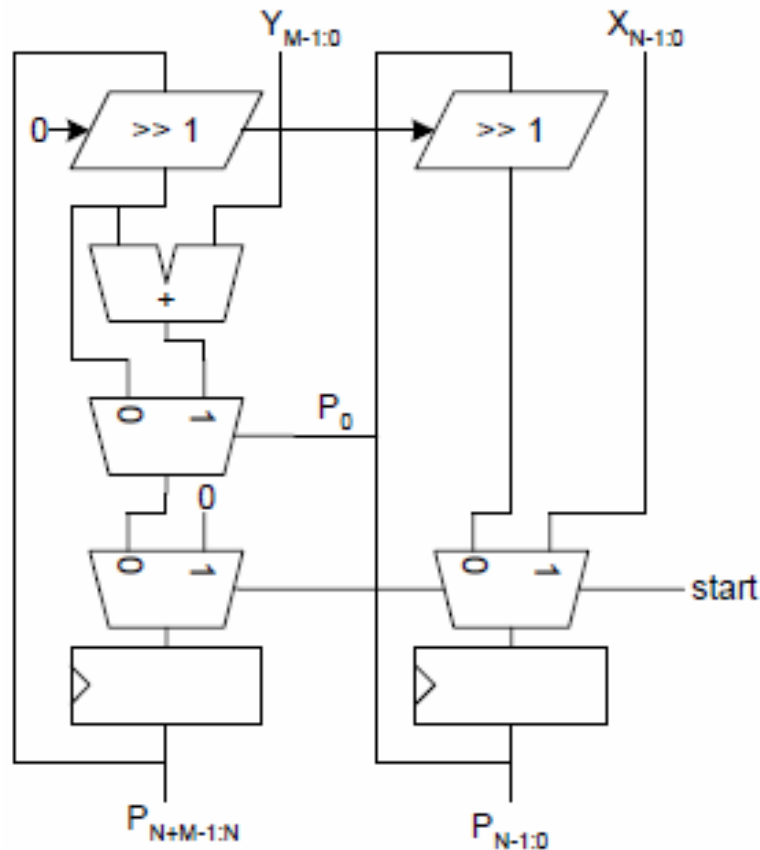

Step	Shift Reg	Notes
	0000 0101	initialize
0a	1100 0101	add 1*Y
0b	01100 010	shift right
1a	01100 010	add 0*Y
1b	001100 01	shift right
2a	111100 01	add 1*Y
2b	0111100 0	shift right
3a	0111100 0	add 0*Y
3b	00111100	shift right



Division

- ❑ Compute $X/Y = Q, R$
 - Where $X = QY + R$
 - $|R| < |Y|$
- ❑ X: Dividend (M+N bits in range $[0, 2^NY-1]$)
- ❑ Y: Divisor (M bits)
- ❑ Q: Quotient (N bits)
- ❑ R: Remainder (M bits)



Division Example

quotient remainder

0110 r 1011

1101 $\overline{) 01011001}$ ← dividend

 -0000

 1011001

 -1101

 100101

 -1101

 01011

 -0000

 1011 ← remainder

divisor

partial remainders

remainder



Division Algorithm

```
PR[0] = X
for i = 0 to N-1
    D[i] = 2PR[i] - (Y << N)
    if D[i] < 0 then QN-i-1 = 0, PR[i+1] = 2PR[i]
    else
        QN-i-1 = 1, PR[i+1] = D[i]
R = PR[N] >> N
```




Division Example

Iteration	$PR[i]$	$Q[i]$	Q_i
0	01011001	$\begin{array}{r} 010110010 \\ -1101 \\ \hline 101100010 \end{array}$	0
1	10110010	$\begin{array}{r} 101100100 \\ -1101 \\ \hline 010010100 \end{array}$	1
2	10010100	$\begin{array}{r} 100101000 \\ -1101 \\ \hline 001011000 \end{array}$	1
3	01011000	$\begin{array}{r} 010110000 \\ -1101 \\ \hline 111100000 \end{array}$	0
4	10110000		



Iterative Approximation

 - ❑ Make initial guess, then iteratively improve
- ❑ Common method: Newton-Raphson
 - Method of finding root of $f(z)$



$$z_{i+1} = z_i - \frac{f(z_i)}{f'(z_i)}$$



Signed Division

- ❑ Magnitude of Q and R are independent of signs
- ❑ Quotient is negative if X and Y have different signs
- ❑ Remainder satisfies $X = QY + R$
 - Hence, sign of remainder matches sign of X
- ❑ Examples:
 - $89 / 13 = 6$ remainder 11
 - $89 / -13 = -6$ remainder 11
 - $-89 / 13 = -6$ remainder -11
 - $-89 / -13 = 6$ remainder -11
- ❑ Convert to unsigned division, correct signs at end



Thank You