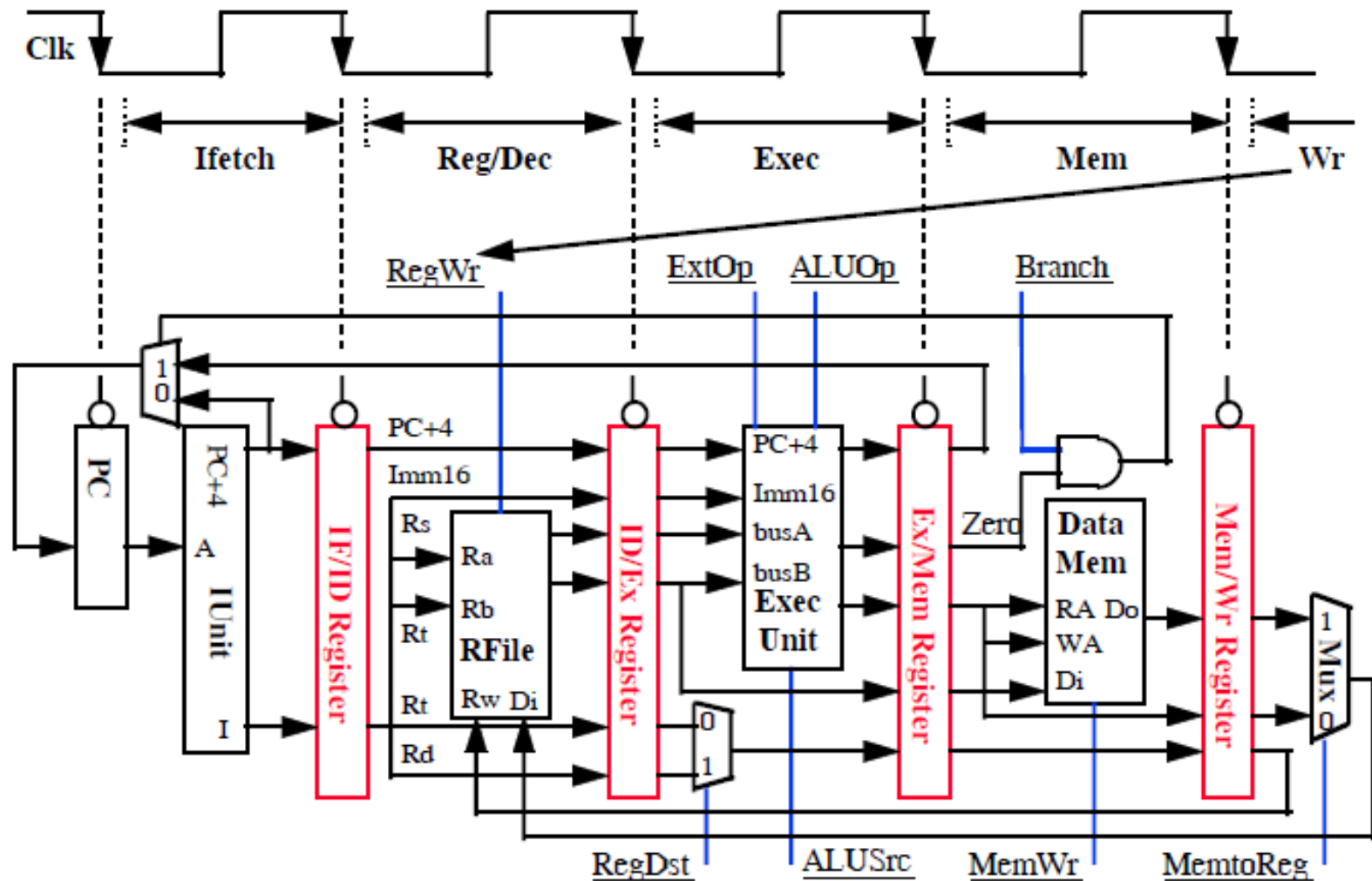


**Acknowledgment:** Almost all of these slides are based on Dave Patterson's CS152 Lecture Slides at UC, Berkeley.

## COMPUTER SYSTEMS ORGANIZATION

Pipelined CPU Design -- Spring 2010 -- IIIT-H -- Suresh Purini

## A Pipelined Datapath




# Basic Pipelining Principle

- 5 TAs
- 200 papers to grade
- Each paper has 5 answers scripts
- Each answer takes half an hour to grade.

Can you suggest grading strategies?

## The Five Stages of Load

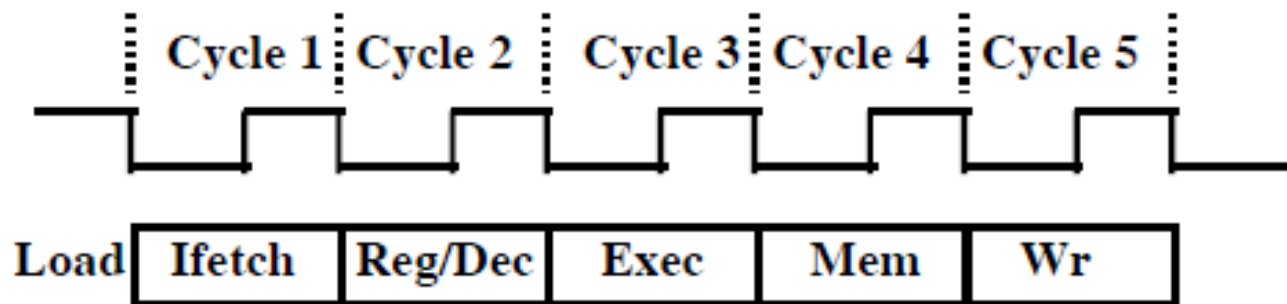


- **Ifetch: Instruction Fetch**
  - Fetch the instruction from the Instruction Memory
- **Reg/Dec: Registers Fetch and Instruction Decode**
- **Exec: Calculate the memory address**
- **Mem: Read the data from the Data Memory**
- **Wr: Write the data back to the register file**

# Key Ideas Behind Pipelining


- ❑ The load instruction has 5 stages:
  - ❑ Five independent functional units to work on each stage
  - ❑ Each functional unit is used only once
- ❑ The 2nd load can start as soon as the 1st finishes its **lfetch** stage
- ❑ Each load still takes five cycles to complete
- ❑ The throughput, however, is much higher

# Pipelining the Load Instruction

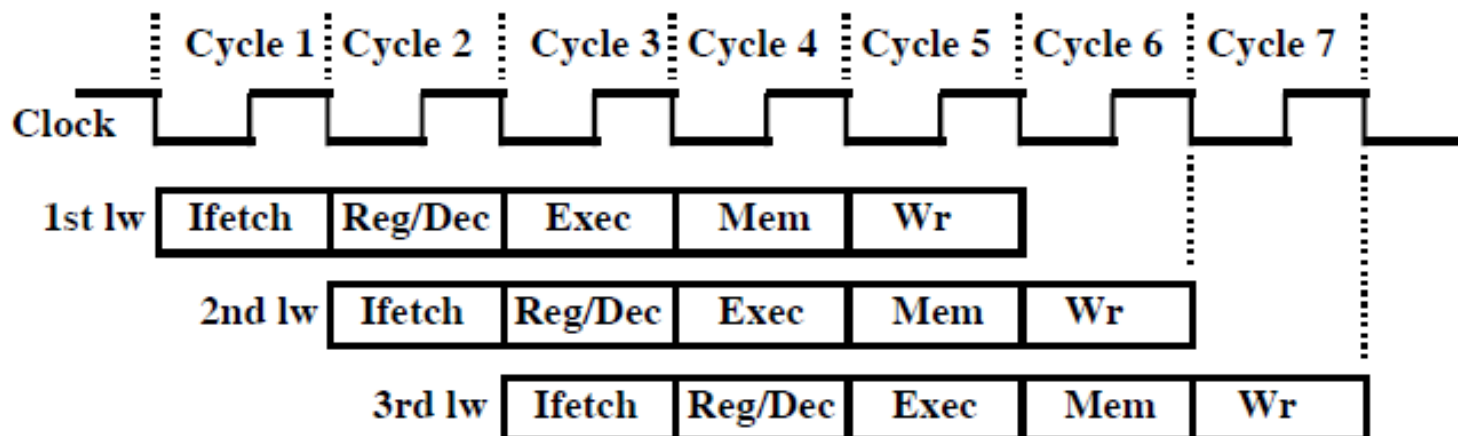


- The five independent functional units in the pipeline datapath are:
  - Instruction Memory for the Ifetch stage
  - Register File's Read ports (bus A and busB) for the Reg/Dec stage
  - ALU for the Exec stage
  - Data Memory for the Mem stage
  - Register File's Write port (bus W) for the Wr stage
- One instruction enters the pipeline every cycle
  - One instruction comes out of the pipeline (complete) every cycle
  - The "Effective" Cycles per Instruction (CPI) is 1

# The Four Stages of R-type

 

- **Ifetch: Instruction Fetch**
  - Fetch the instruction from the Instruction Memory
- **Reg/Dec: Registers Fetch and Instruction Decode**
- **Exec: ALU operates on the two register operands**
- **Wr: Write the ALU output back to the register file**
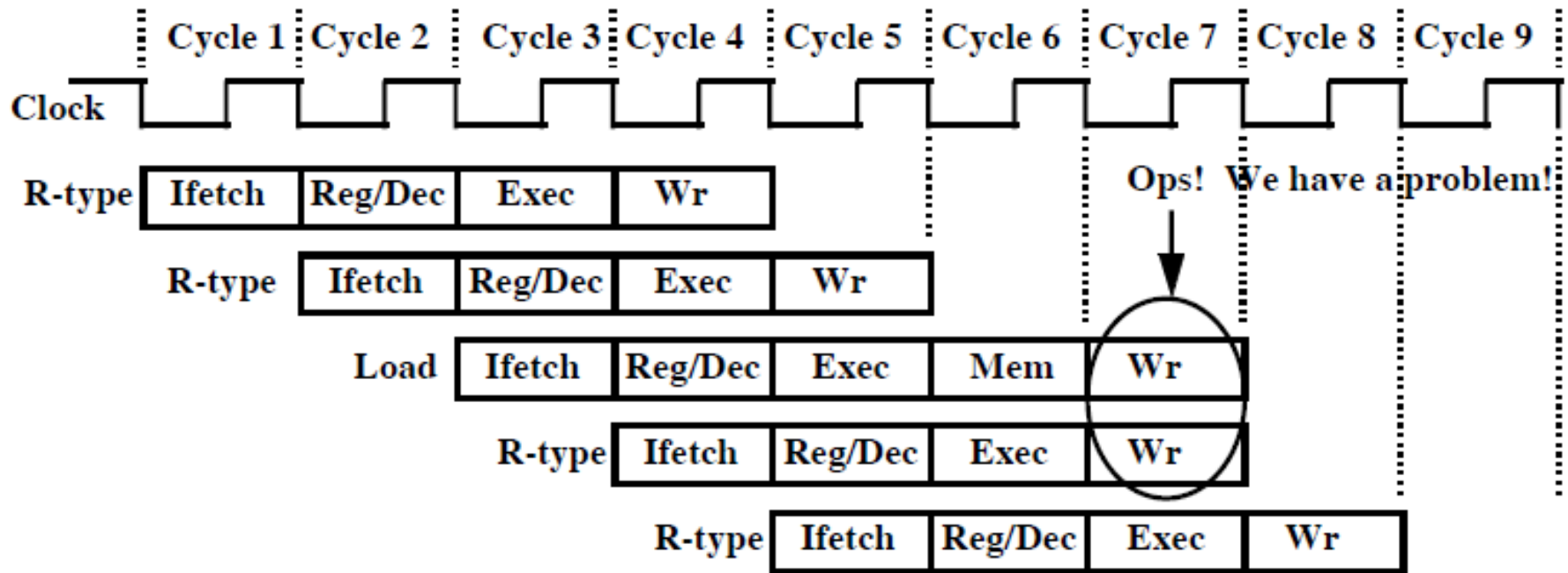
# Pipelining the R-type and Load Instruction



◦ We have a problem:


- Two instructions try to write to the register file at the same time!

**Structural Hazard:** Two instructions require access to the same functional unit.



 
## Important Observation


- Each functional unit can only be used once per instruction
- Each functional unit must be used at the same stage for all instructions:
  - Load uses Register File's Write Port during its 5th stage



 - R-type uses Register File's Write Port during its 4th stage



 
## Solution 1: Insert “Bubble” into the Pipeline




- Insert a “bubble” into the pipeline to prevent 2 writes at the same cycle
  - The control logic can be complex
- No instruction is completed during Cycle 5:
  - The “Effective” CPI for load is 2
 
## Solution 2: Delay R-type's Write by One Cycle

- Delay R-type's register write by one cycle:
  - Now R-type instructions also use Reg File's write port at Stage 5
  - Mem stage is a NOOP stage: nothing is being done




# The Four Stages of Store

 

- **Ifetch: Instruction Fetch**
  - **Fetch the instruction from the Instruction Memory**
- **Reg/Dec: Registers Fetch and Instruction Decode**
- **Exec: Calculate the memory address**
- **Mem: Write the data into the Data Memory**


# The Four Stages of Beq

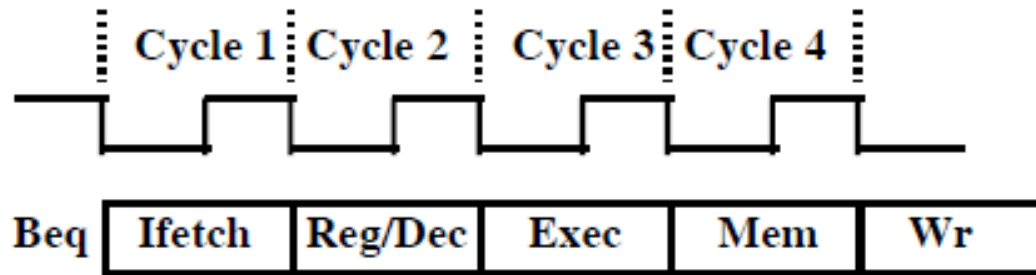

- **Ifetch: Instruction Fetch**
  - Fetch the instruction from the Instruction Memory
- **Reg/Dec: Registers Fetch and Instruction Decode**
- **Exec: ALU compares the two register operands**
  - Adder calculates the branch target address
- **Mem: If the registers we compared in the Exec stage are the same,**
  - Write the branch target address into the PC

Hey, this happens in second cycle in our Multi-Cycle CPU Design

# A Pipelined Datapath

 


## Fields of IF/ID Register:

1. 32-bits to store instruction
2. 32-bits to store PC+4

 
## The Instruction Fetch Stage

◦ Location 10: `lw $1, 0x100($2)`      $\$1 \leftarrow \text{Mem}[(\$2) + 0x100]$



# A Detail View of the Instruction Unit


- Location 10: lw \$1, 0x100(\$2)

 


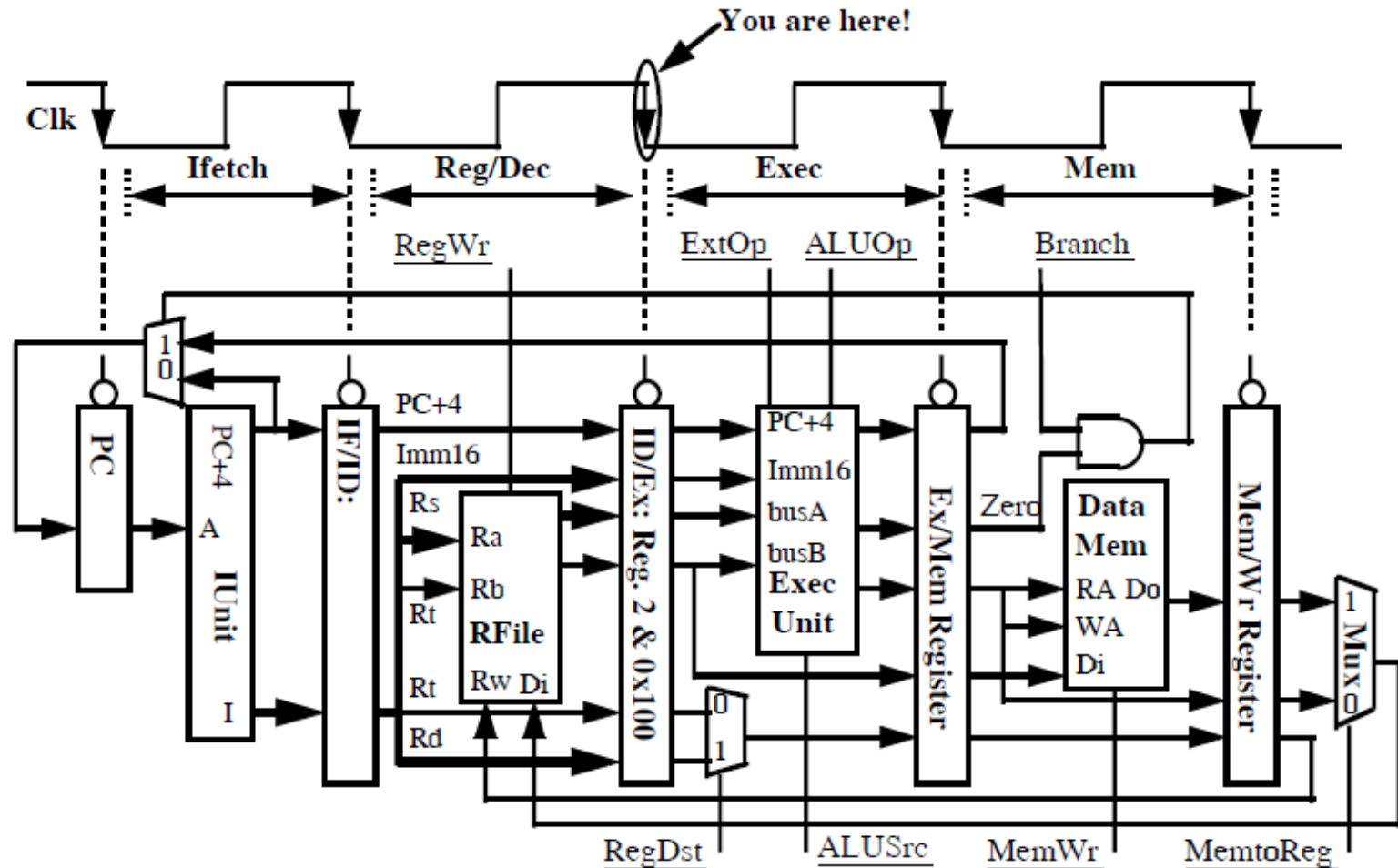
# The Decode / Register Fetch Stage

◦ Location 10: lw \$1, 0x100(\$2)     \$1 ← Mem[(\$2) + 0x100]



## Fields of ID/Ex Register:


1. 32-bits for PC+4
2. 16-bits for Imm16
3. 32-bits for M[Rs]

## Fields of ID/Ex Register (continued):

4. 32-bits for M[Rt]
5. 5-bits for Rt
6. 5-bits for Rd
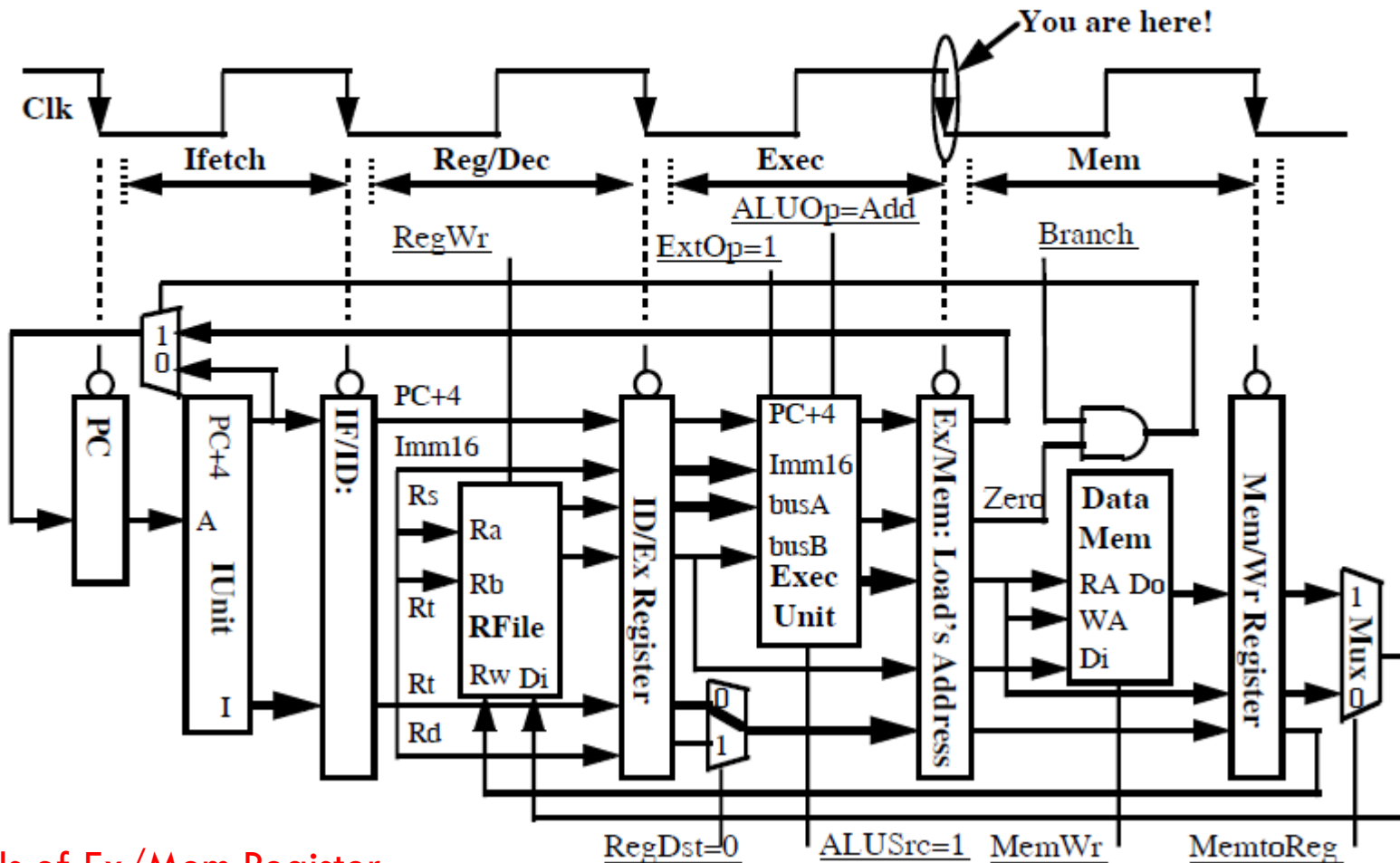
# Load's Address Calculation Stage


◦ Location 10: lw \$1, 0x100(\$2)     \$1 ← Mem[(\$2) + 0x100]



## Fields of Ex/Mem Register:

1. 32-bits for Branch Target Address
2. 32-bits for ALUout
3. 1-bit for Zero Flag
4. 32-bits for Mem[Rt]
5. 5-bits for RegDest: Rt or Rd


## A Detail View of the Execution Unit

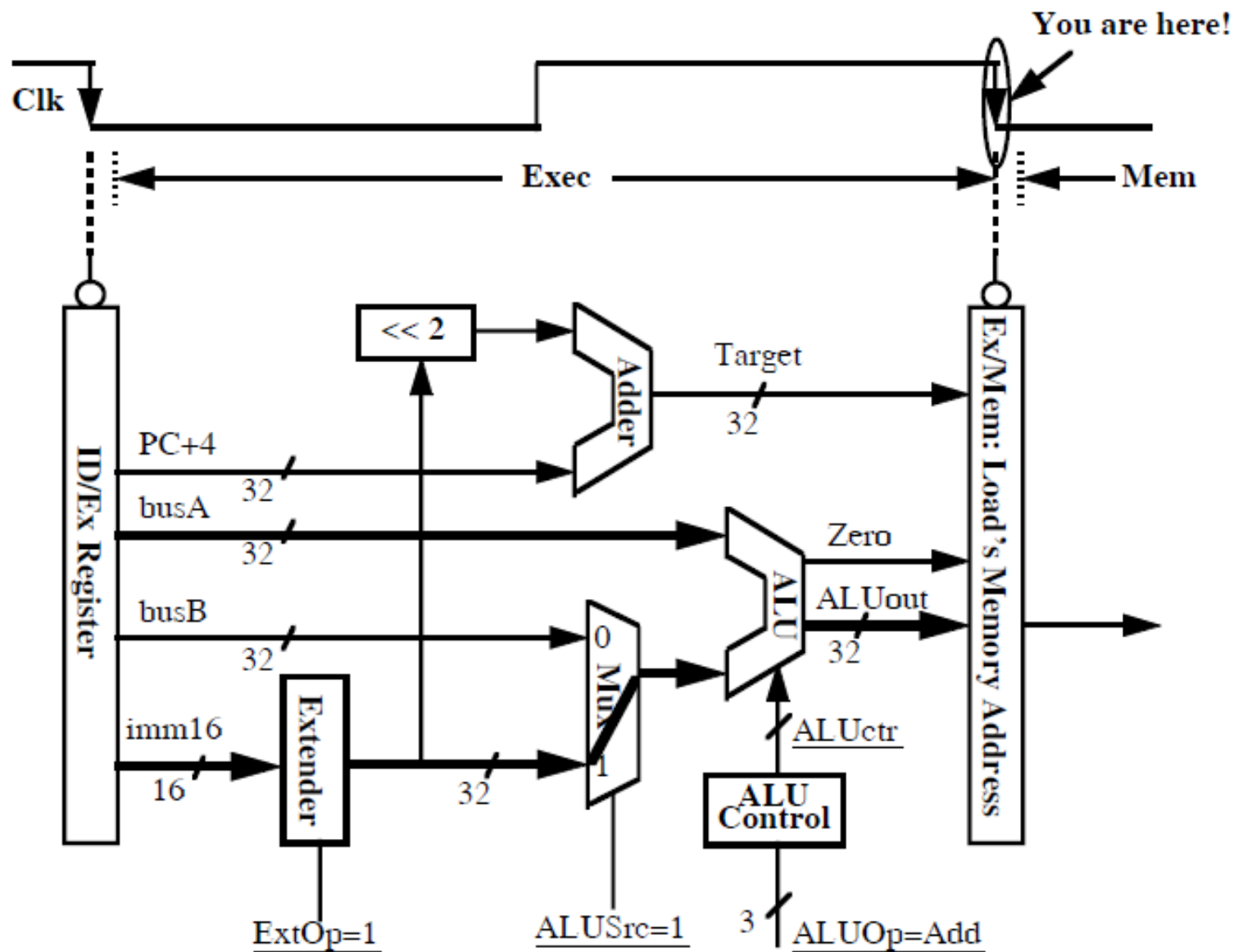

# Load's Memory Access Stage

◦ Location 10: lw \$1, 0x100(\$2)     \$1 <- Mem[(\$2) + 0x100]

You are here! →

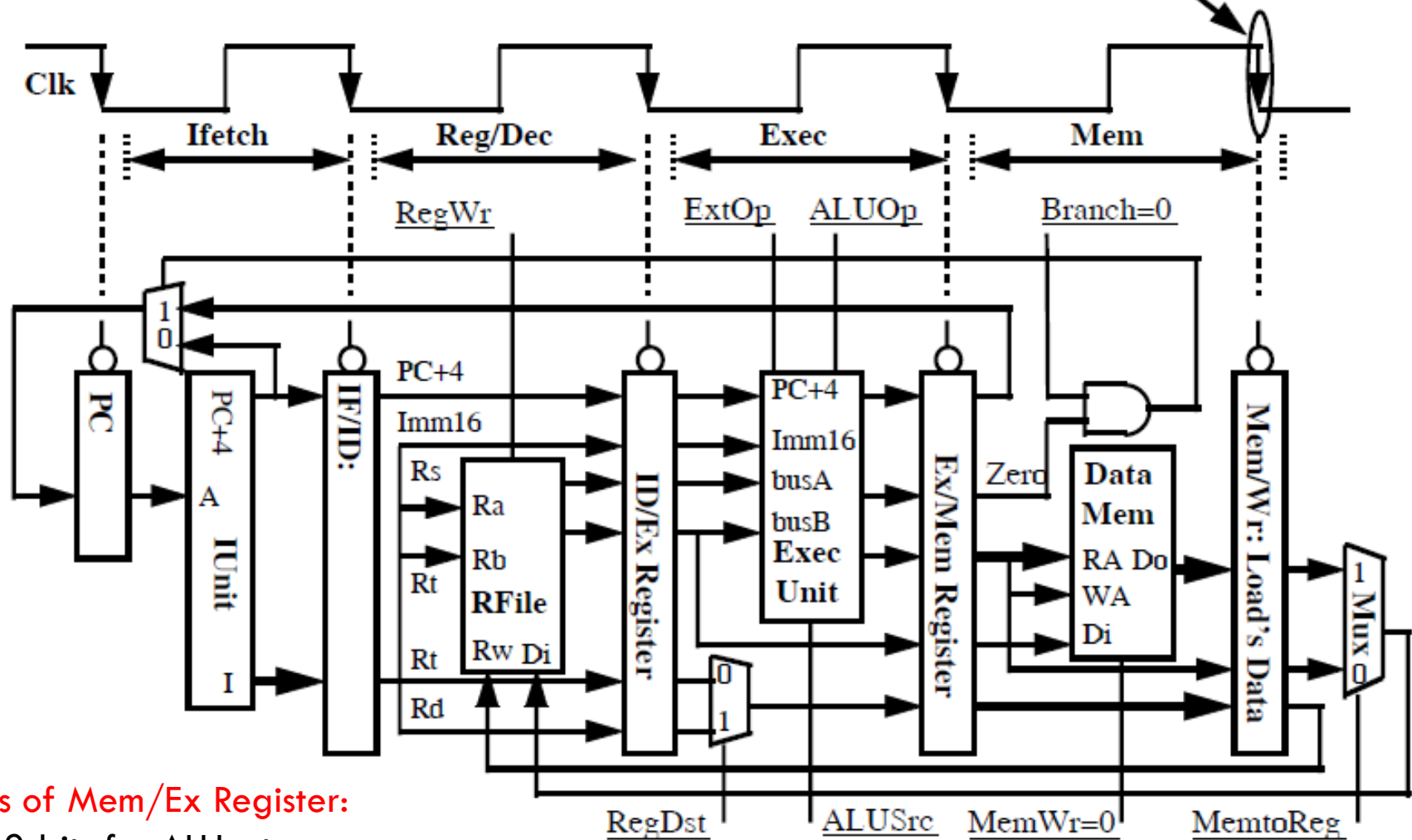


Fields of Mem/Ex Register:

1. 32-bits for ALUOut
2. 32-bits for Data Memory
3. 5-bits for RegDest: Rt or Rd

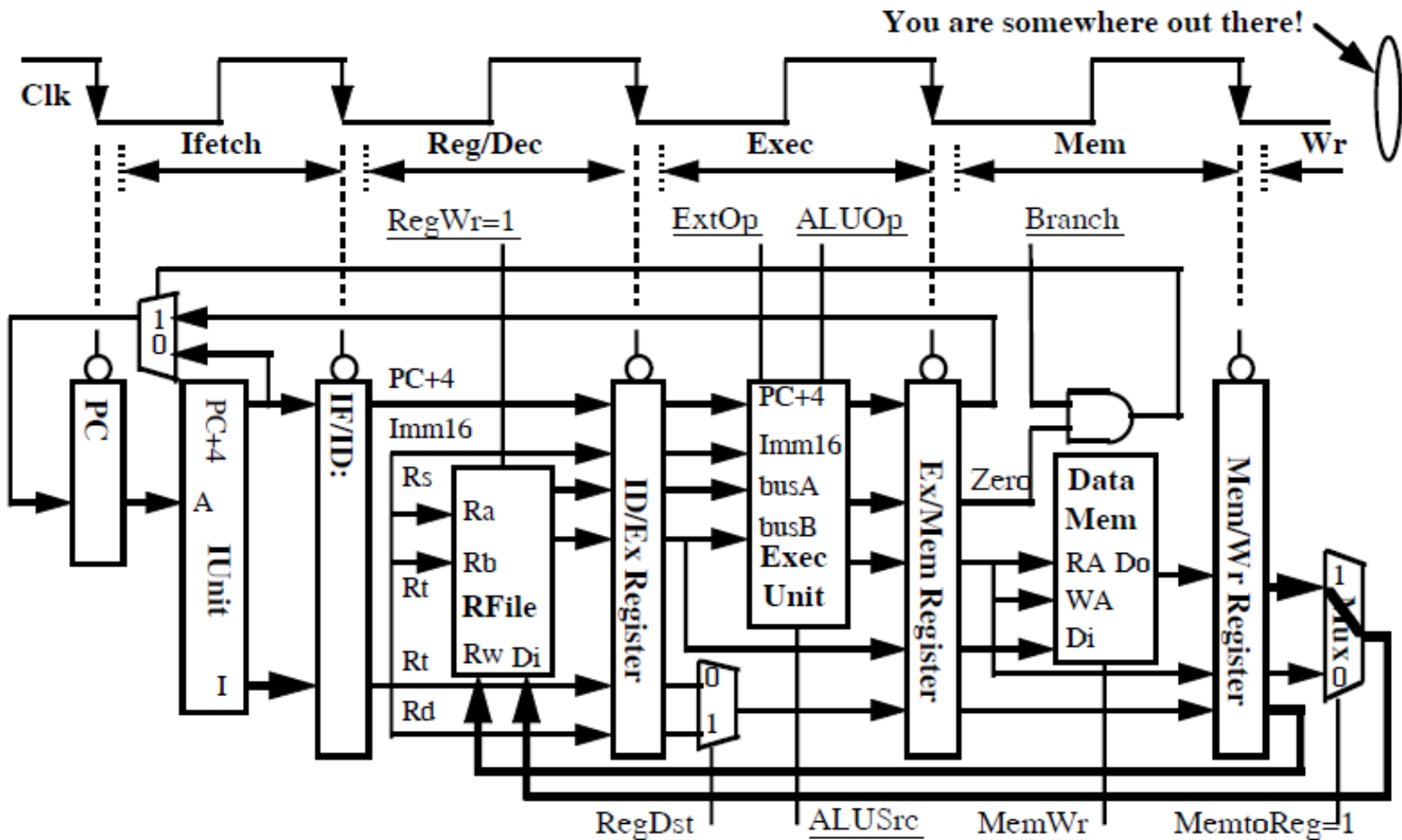
## Load's Write Back Stage

◦ Location 10: `lw $1, 0x100($2)`      $\$1 \leftarrow \text{Mem}[(\$2) + 0x100]$



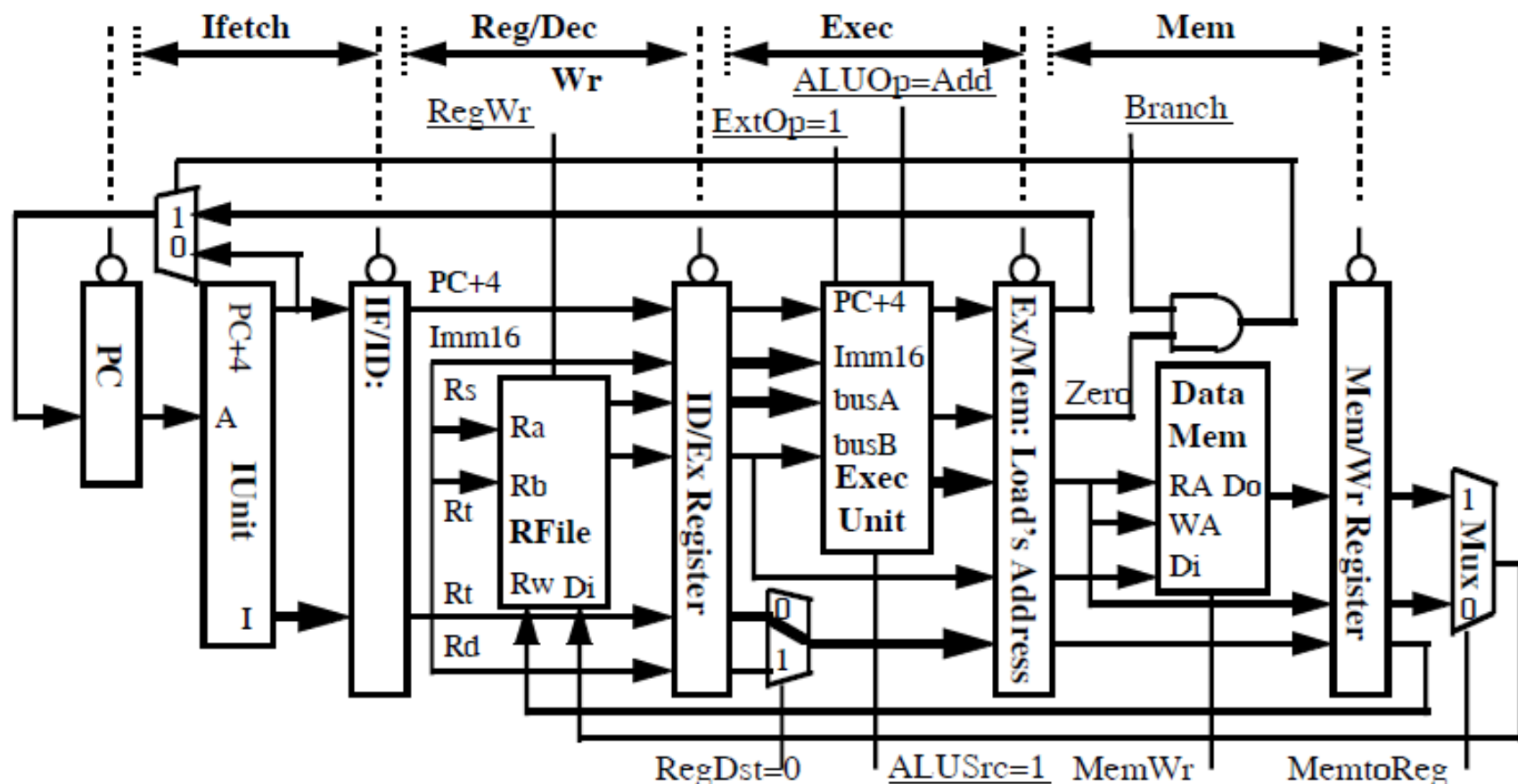
## How About Control Signals?

- Key Observation: Control Signals at Stage N = Func (Instr. at Stage N)
  - N = Exec, Mem, or Wr
- Example: Controls Signals at Exec Stage = Func(Load's Exec)




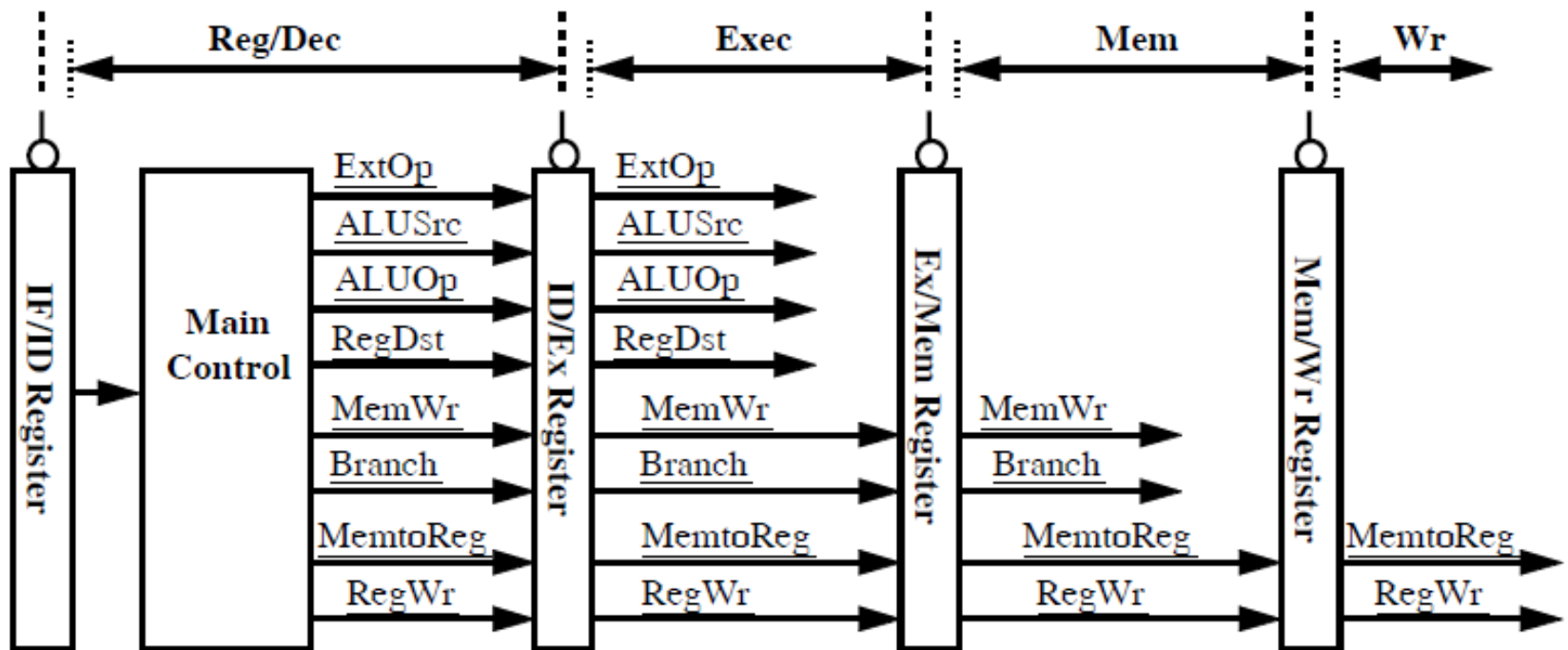
# Pipeline Control

- The Main Control generates the control signals during Reg/Dec
  - Control signals for Exec (ExtOp, ALUSrc, ...) are used 1 cycle later
  - Control signals for Mem (MemWr Branch) are used 2 cycles later
  - Control signals for Wr (MemtoReg MemWr) are used 3 cycles later



We need to add more fields for holding control bits to the intermediate register structures we defined in the previous fields.
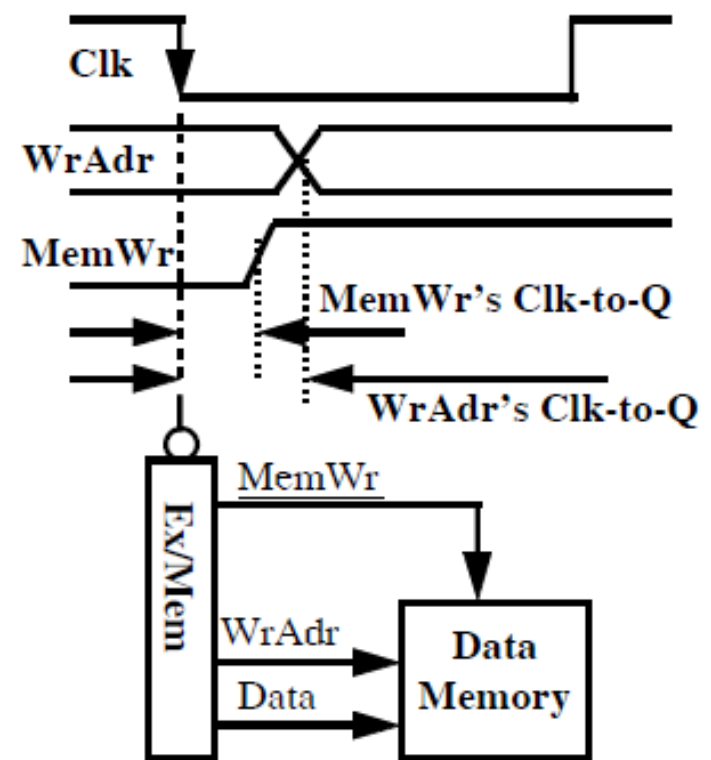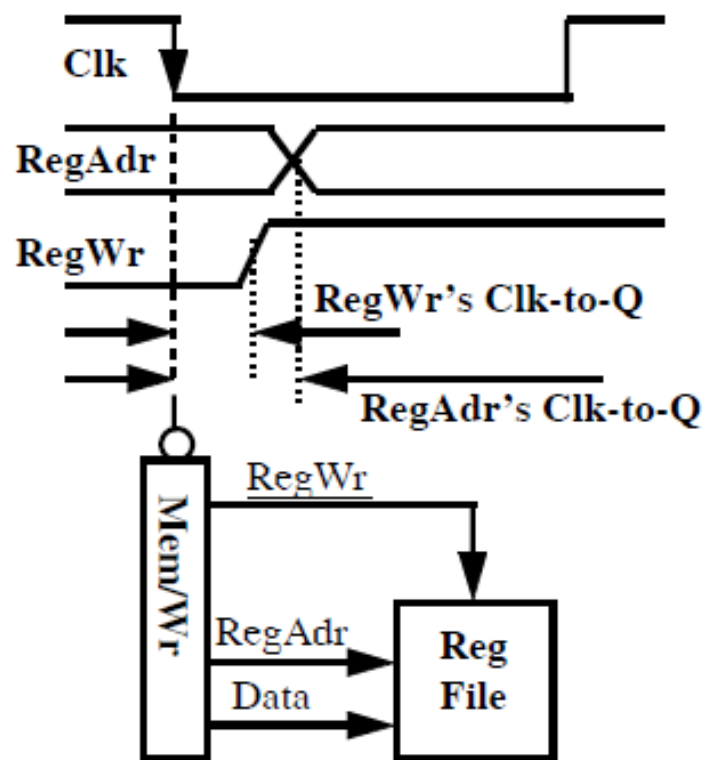
## Beginning of the Wr's Stage: A Real World Problem




- At the beginning of the Wr stage, we have a problem if:
  - $\text{RegAdr's (Rd or Rt) Clk-to-Q} > \text{RegWr's Clk-to-Q}$
- Similarly, at the beginning of the Mem stage, we have a problem if:
  - $\text{WrAdr's Clk-to-Q} > \text{MemWr's Clk-to-Q}$
- We have a race condition between Address and Write Enable!



 
# The Pipeline Problem

- Multiple Cycle design prevents race condition between Addr and WrEn:
  - Make sure Address is stable by the end of Cycle N
  - Asserts WrEn during Cycle N + 1
- This approach can NOT be used in the pipeline design because:
  - Must be able to write the register file every cycle
  - Must be able write the data memory every cycle


 
# Synchronize Register File & Synchronize Memory

- Solution: And the Write Enable signal with the Clock
  - This is the **ONLY** place where gating the clock is used
  - **MUST** consult circuit expert to ensure no timing violation:
    - Example: Clock High Time > Write Access Delay




## Synchronize Memory and Register File

Address, Data, and WrEn must be stable at least 1 set-up time before the Clk edge

Write occurs at the cycle following the clock edge that captures the signals


## A More Extensive Pipelining Example

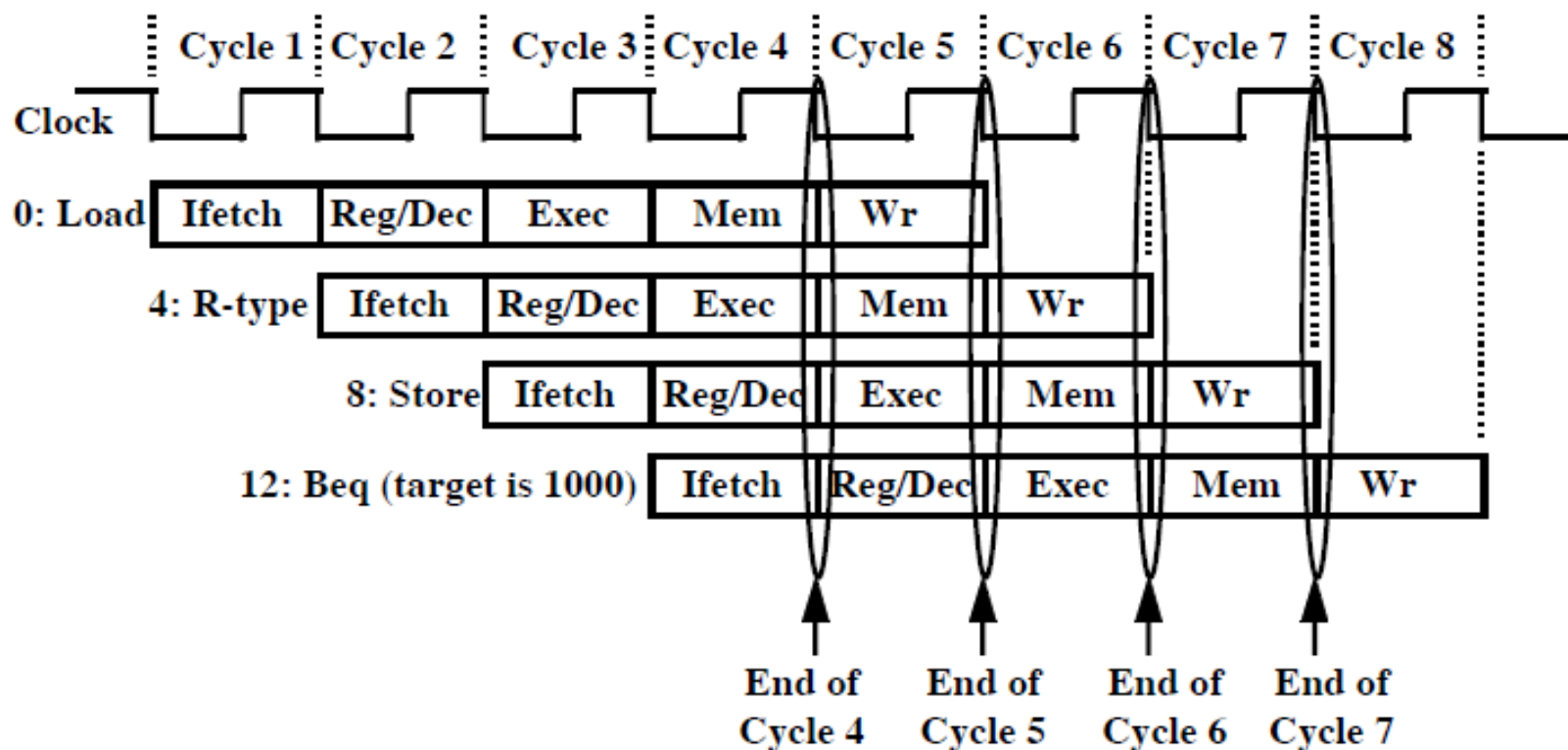

- End of Cycle 4: Load's Mem, R-type's Exec, Store's Reg, Beq's Ifetch
- End of Cycle 5: Load's Wr, R-type's Mem, Store's Exec, Beq's Reg
- End of Cycle 6: R-type's Wr, Store's Mem, Beq's Exec
- End of Cycle 7: Store's Wr, Beq's Mem


# Pipelining Example: End of Cycle 4

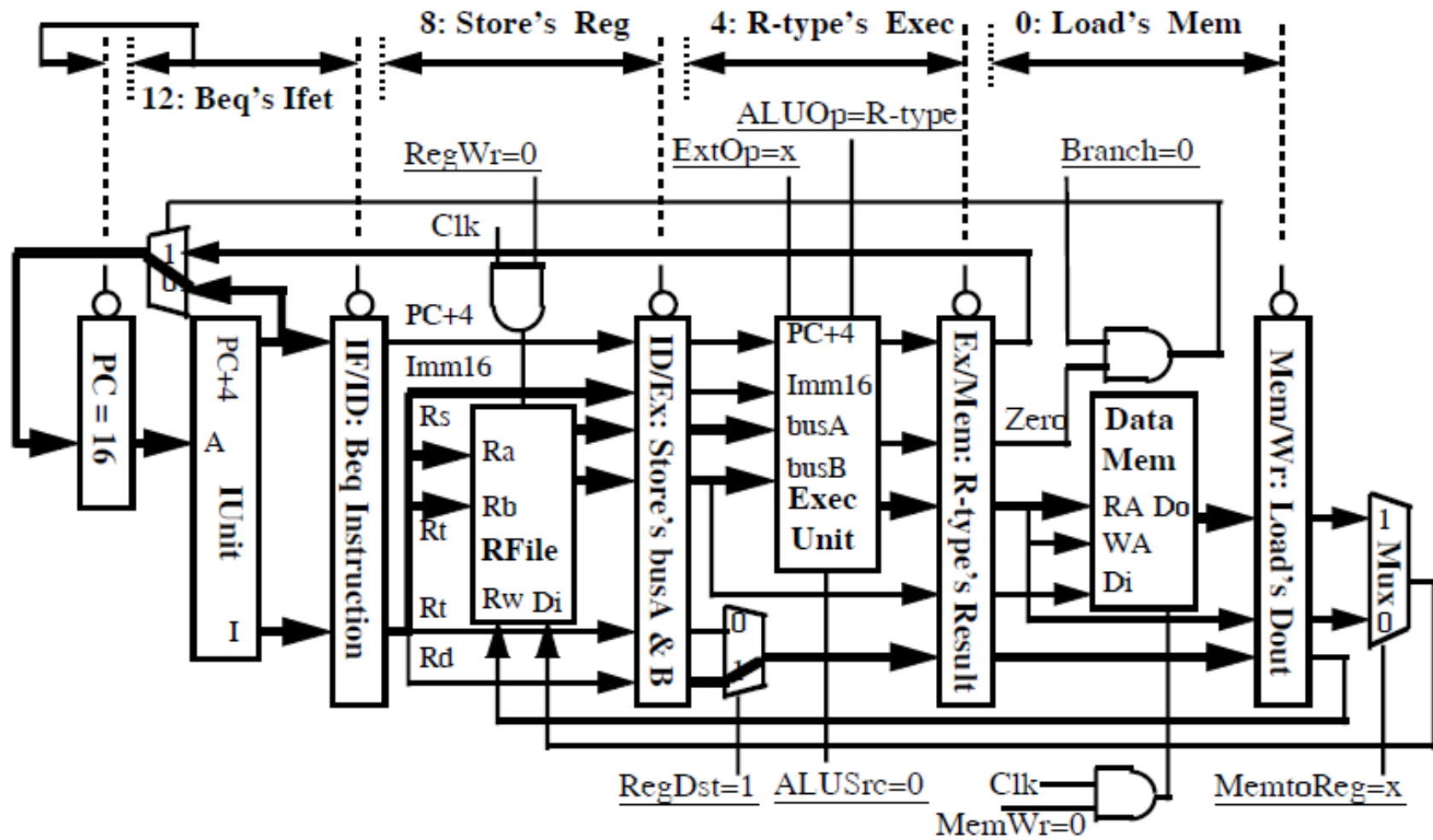- 0: Load's Mem    4: R-type's Exec    8: Store's Reg    12: Beq's Ifetch




# Pipelining Example: End of Cycle 5

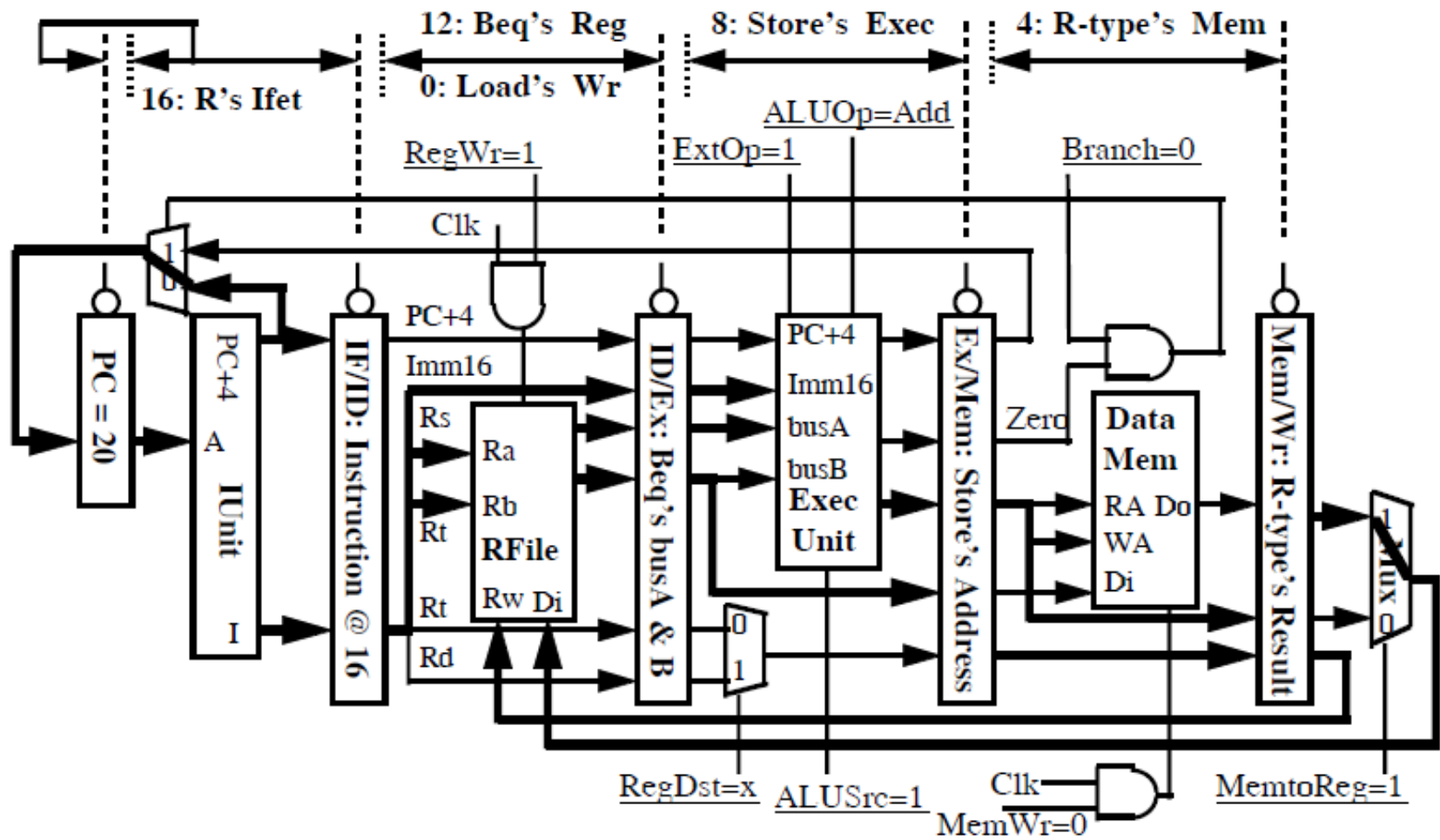- 0: Lw's Wr    4: R's Mem    8: Store's Exec    12: Beq's Reg    16: R's Ifetch




## Pipelining Example: End of Cycle 6

 - 4: R's Wr    8: Store's Mem    12: Beq's Exec    16: R's Reg    20: R's Ifet




## Pipelining Example: End of Cycle 7

 - 8: Store's Wr    12: Beq's Mem    16: R's Exec    20: R's Reg    24: R's Ifet




## The Delay Branch Phenomenon

 

- Although Beq is fetched during Cycle 4:
  - Target address is NOT written into the PC until the end of Cycle 7
  - Branch's target is NOT fetched until Cycle 8
  - 3-instruction delay before the branch take effect
- This is referred to as Branch Hazard:
  - Clever design techniques can reduce the delay to ONE instruction



## The Delay Load Phenomenon

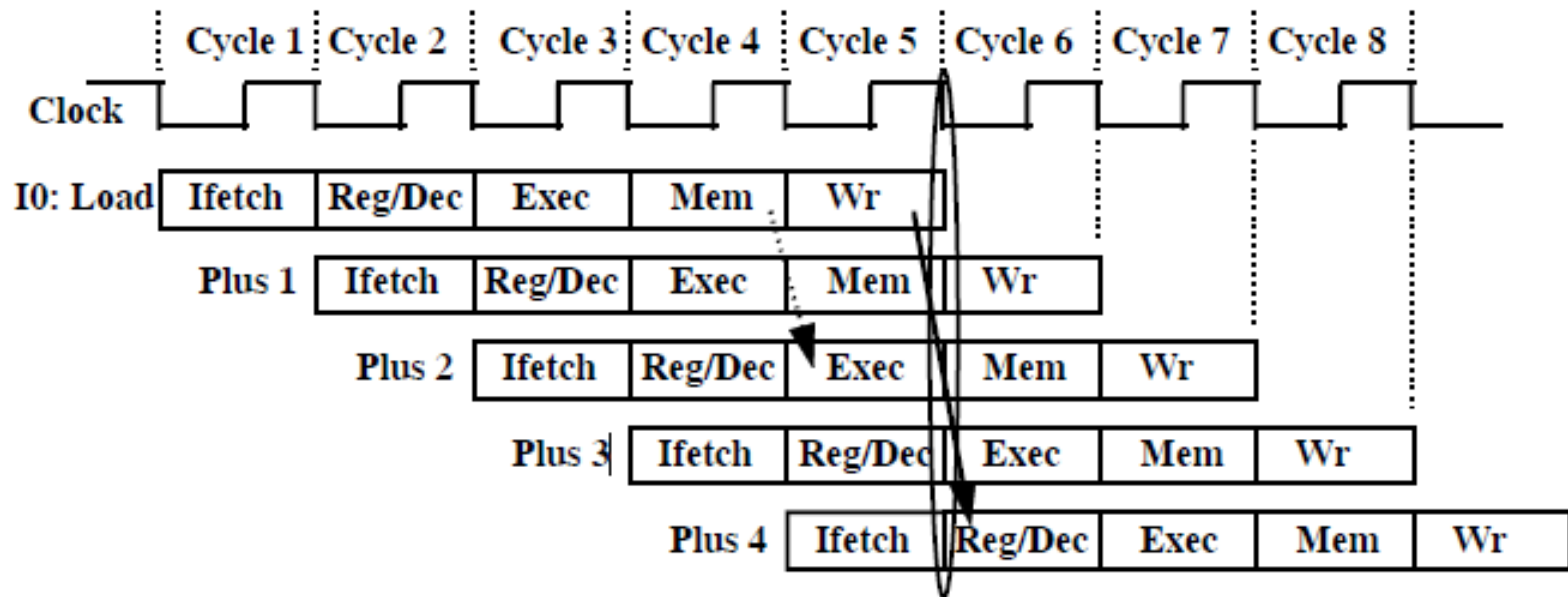


- Although Load is fetched during Cycle 1:
  - The data is NOT written into the Reg File until the end of Cycle 5
  - We cannot read this value from the Reg File until Cycle 6
  - 3-instruction delay before the load take effect
- This is referred to as Data Hazard:
  - Clever design techniques can reduce the delay to ONE instruction


# Summary

- Disadvantages of the Single Cycle Processor
  - Long cycle time
  - Cycle time is too long for all instructions except the Load
- Multiple Clock Cycle Processor:
  - Divide the instructions into smaller steps
  - Execute each step (instead of the entire instruction) in one cycle
- Pipeline Processor:
  - Natural enhancement of the multiple clock cycle processor
  - Each functional unit can only be used once per instruction
  - If an instruction is going to use a functional unit:
    - it must use it at the same stage as all other instructions
  - Pipeline Control:
    - Each stage's control signal depends **ONLY** on the instruction that is currently in that stage
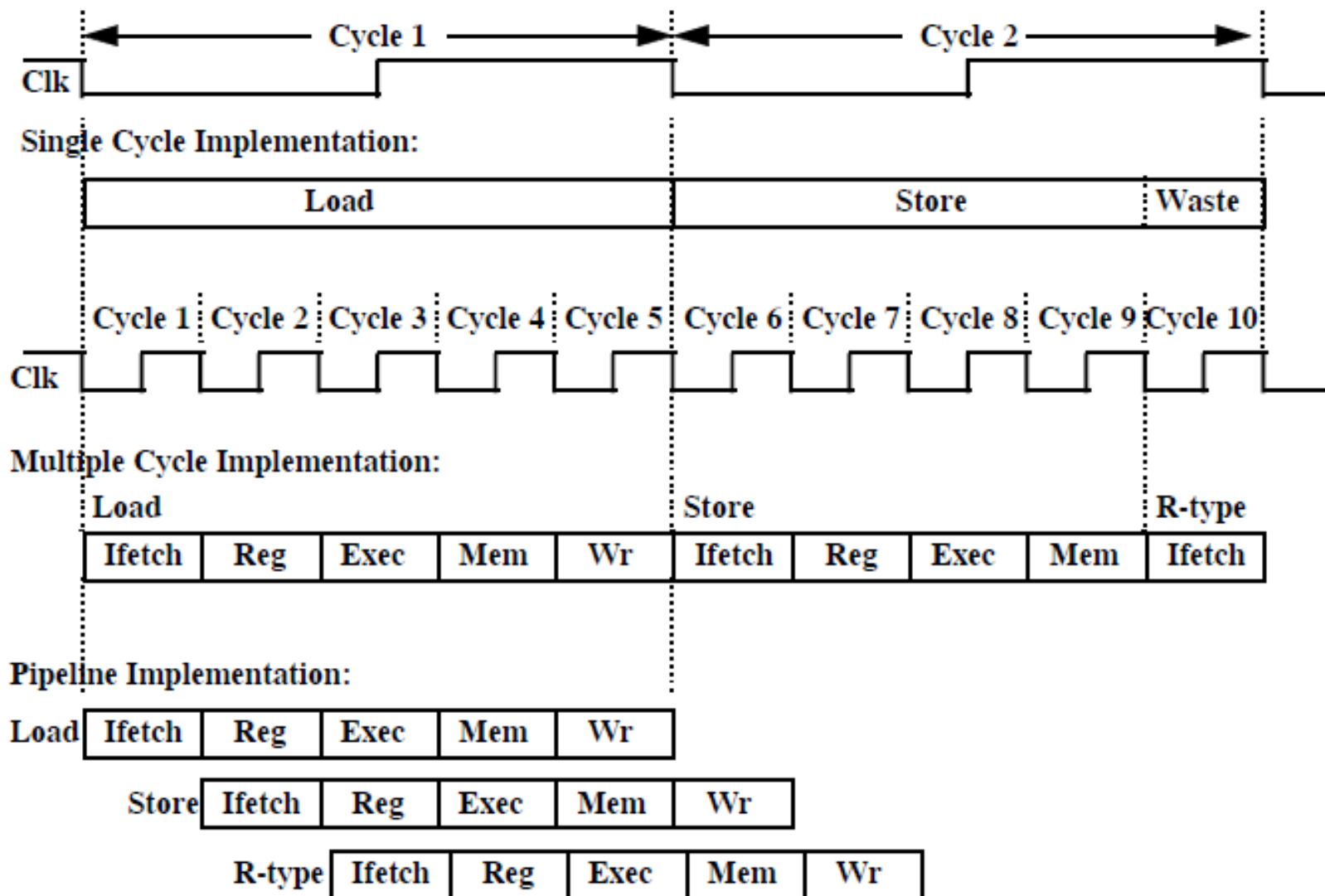
# Single Cycle, Multiple Cycle, vs. Pipeline



# A Pipelined Datapath

 

## Pipeline Control “Data Stationary Control”

- The Main Control generates the control signals during Reg/Dec
  - Control signals for Exec (ExtOp, ALUSrc, ...) are used 1 cycle later
  - Control signals for Mem (MemWr Branch) are used 2 cycles later
  - Control signals for Wr (MemtoReg MemWr) are used 3 cycles later

