

International Institute of Information Technology, Hyderabad

CVEST

Introduction to VLSI (ECE361) & Advanced VLSI, Spring 2013

Assignment-2

Due: Mon., 28-1-2013

## CMOS INVERTER CHARACTERISTICS IN THE PRESENCE OF PROCESS VARIATION

### Problem-1

Design a CMOS inverter with  $\frac{W_P}{L_P} = K \frac{W_N}{L_N}$  and  $K=3$  and obtain its transfer characteristics. Analyse the Noise Margins( $NM_H$  and  $NM_L$ ) of the designed inverter for typical process corners.

### Problem-2

Analyse the Noise Margins for (a) Slow and (b) Fast process corners.

### Problem-3

1. Perform Monte Carlo simulations for variations in the  $W$ ,  $L$ ,  $V_{th}$ .
2. Perform mismatch analysis for different values of 'K'.

### Problem-4

Analyse the effect of supply voltage scaling(by 10 %) on the inverter's characteristics.

### Tools and Technology

You will be using LTSPICE or other tools for the simulations using 90nm MOS corner models.

### Deliverables

A pdf document containing

1. A brief write up on the theoretical analysis of the problem.
2. Circuit schematics and SPICE results (graphs) along with your detailed observations on the results.