

# Test Compression

**Dr. Shubhajit Roy Chowdhury,**

**Centre for VLSI and Embedded Systems Technology,**

**IIIT Hyderabad, India**

**Email: [src.vlsi@iiit.ac.in](mailto:src.vlsi@iiit.ac.in)**



*Dr. Shubhajit Roy Chowdhury*


**CVEST, IIIT HYDERABAD**

# Test Compression

- Decompressor
  - Add some additional on-chip hardware before the scan chains to decompress the test stimulus
  - Use lossless compression
- Compactor
  - Add some additional on-chip hardware after scan chains to compact the response
  - The compaction is lossy
- Advantages:
  - Reduce ATE memory
  - Reduce test data volume and test application time



# Test Compression Architecture

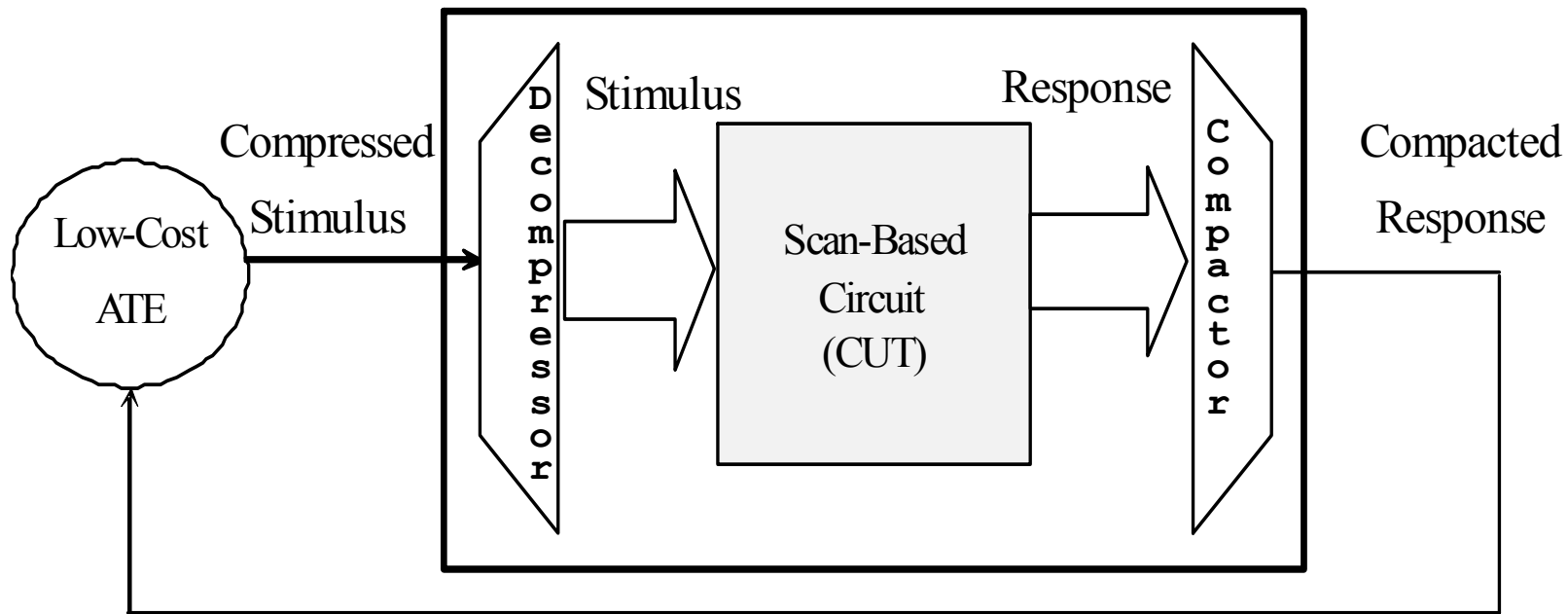

# Circuits for Test Stimulus Compression

- Linear-Decompression-Based Schemes
  - Combinational linear decompressors
  - Sequential linear decompressors
- Broadcast-Scan-Based Schemes
  - Broadcast scan
  - Illinois scan
  - Multiple-input broadcast scan
  - Reconfigurable broadcast scan
  - Virtual scan
- Comparison




# Linear-Decompression-Based Schemes

- Linear Decompressor Concept
  - Consists of only XOR gates and Flip-Flops
  - Its output space is a linear subspace that is spanned by a Boolean matrix.
- Combinational Linear Decompressor
  - Consists of only XOR gates
- Sequential Linear Decompressor
  - Consists of XOR gates and Flip-Flops
  - Flip-flops provides additional free variables for state encoding.


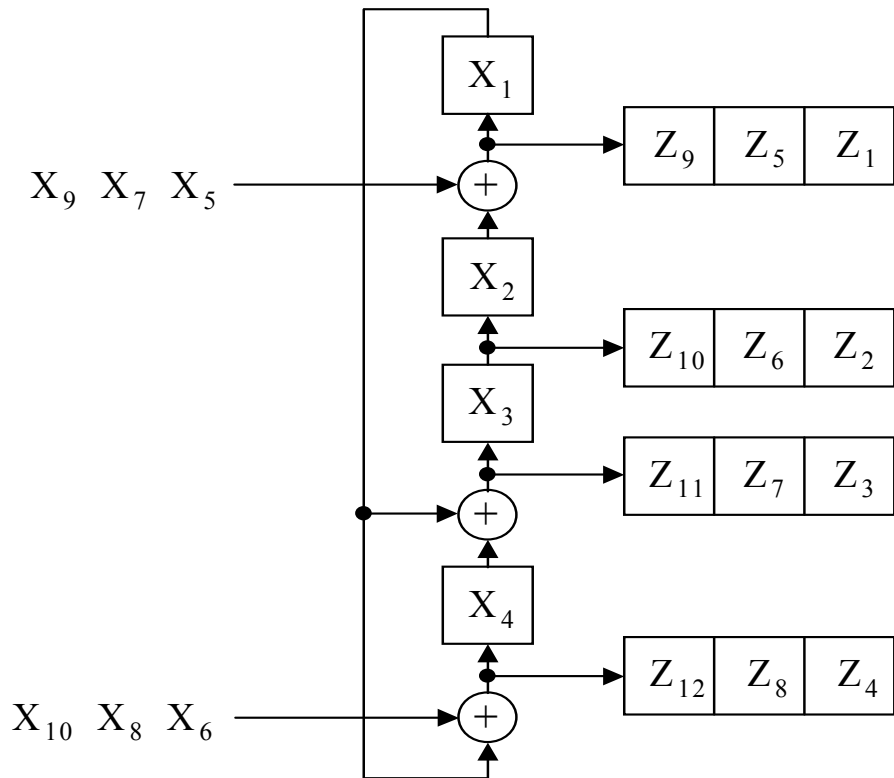
# Example of symbolic simulation for linear decompressor



$Z_9 = X_1 \oplus X_4 \oplus X_9$	$Z_5 = X_3 \oplus X_7$	$Z_1 = X_2 \oplus X_5$
$Z_{10} = X_1 \oplus X_2 \oplus X_5 \oplus X_6$	$Z_6 = X_1 \oplus X_4$	$Z_2 = X_3$
$Z_{11} = X_2 \oplus X_3 \oplus X_5 \oplus X_7 \oplus X_8$	$Z_7 = X_1 \oplus X_2 \oplus X_5 \oplus X_6$	$Z_3 = X_1 \oplus X_4$
$Z_{12} = X_3 \oplus X_7 \oplus X_{10}$	$Z_8 = X_2 \oplus X_5 \oplus X_8$	$Z_4 = X_1 \oplus X_6$



$$\begin{pmatrix}
 0 & 1 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\
 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\
 1 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\
 1 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\
 0 & 0 & 1 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\
 1 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\
 1 & 1 & 0 & 0 & 1 & 1 & 0 & 0 & 0 & 0 \\
 0 & 1 & 0 & 0 & 1 & 0 & 0 & 1 & 0 & 0 \\
 1 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 1 & 0 \\
 1 & 1 & 0 & 0 & 1 & 1 & 0 & 0 & 0 & 0 \\
 0 & 1 & 1 & 0 & 1 & 0 & 1 & 1 & 0 & 0 \\
 0 & 0 & 1 & 0 & 0 & 0 & 1 & 0 & 0 & 1
 \end{pmatrix}
 \begin{pmatrix}
 X_1 \\
 X_2 \\
 X_3 \\
 X_4 \\
 X_5 \\
 X_6 \\
 X_7 \\
 X_8 \\
 X_9 \\
 X_{10}
 \end{pmatrix}
 =
 \begin{pmatrix}
 Z_1 \\
 Z_2 \\
 Z_3 \\
 Z_4 \\
 Z_5 \\
 Z_6 \\
 Z_7 \\
 Z_8 \\
 Z_9 \\
 Z_{10} \\
 Z_{11} \\
 Z_{12}
 \end{pmatrix}$$

System of linear equations for the decompressor



# Combinational Linear Decompressor

- Advantage:
  - Simpler hardware and control because only XOR gates are used
- Disadvantages:
  - Low Encoding Efficiency
    - Because no free variables are used
    - Can be improved by dynamically adjusting the number of scan chains that are loaded in each clock cycle.






# Sequential Linear Decompressor

- Based on linear finite-state machines
  - Examples: LFSRs, cellular automata, ring generators
- Advantages:
  - Allow free variables from earlier clock cycles
  - Much greater flexibility than combinational linear decompressor
- Two classes
  - Static reseeding
    - Drawbacks
      - The tester is idle while the LFSR is running in autonomous mode.
      - The LFSR must be at least as large as the number of specified bits in the test cube.
  - Dynamic reseeding

# Typical Sequential Linear Decompressor

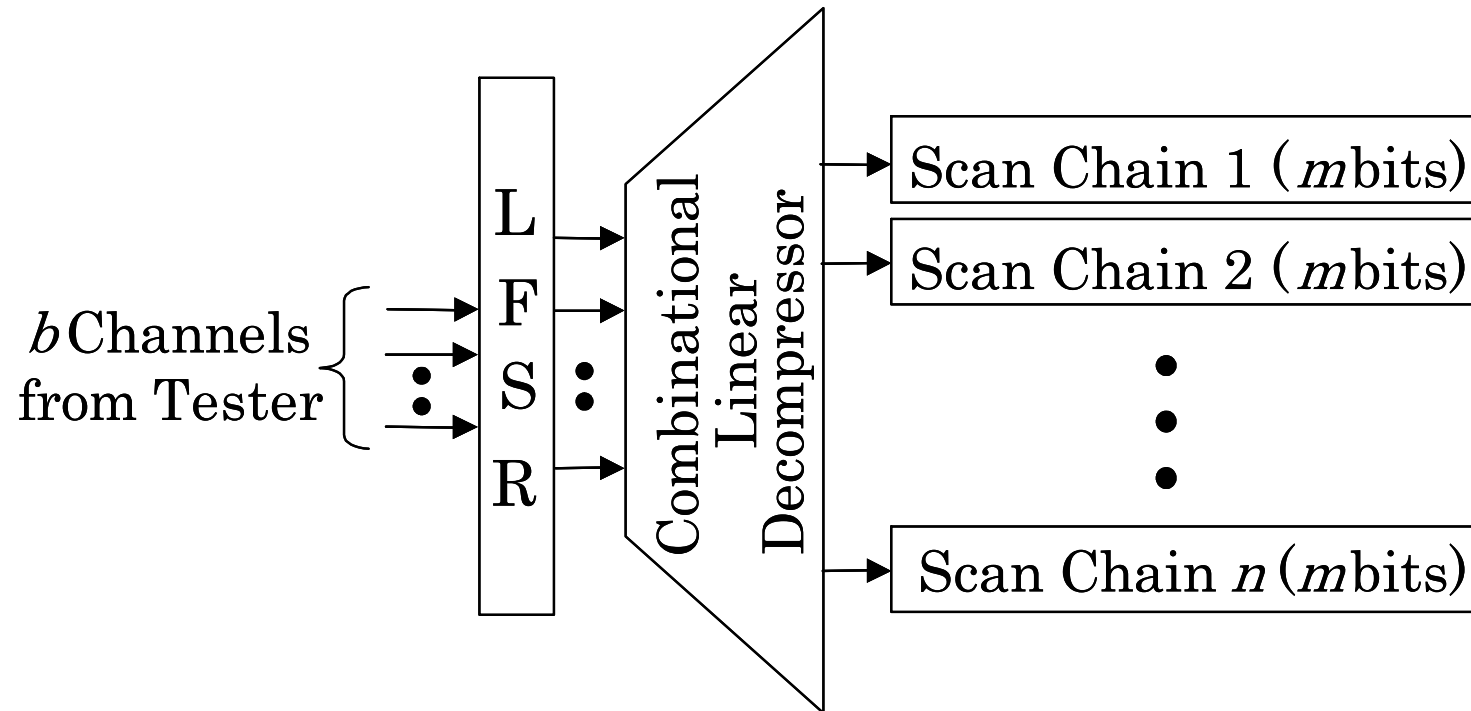

Dynamic reseeding calls for the injection of free variables coming from the tester into the LFSR as it loads the scan chains




# Broadcast-Scan-Based Schemes

- Broadcast scan
- Illinois Scan
- Multiple input broadcast scan
- Reconfigurable broadcast scan
- Virtual scan



# Broadcast Scan

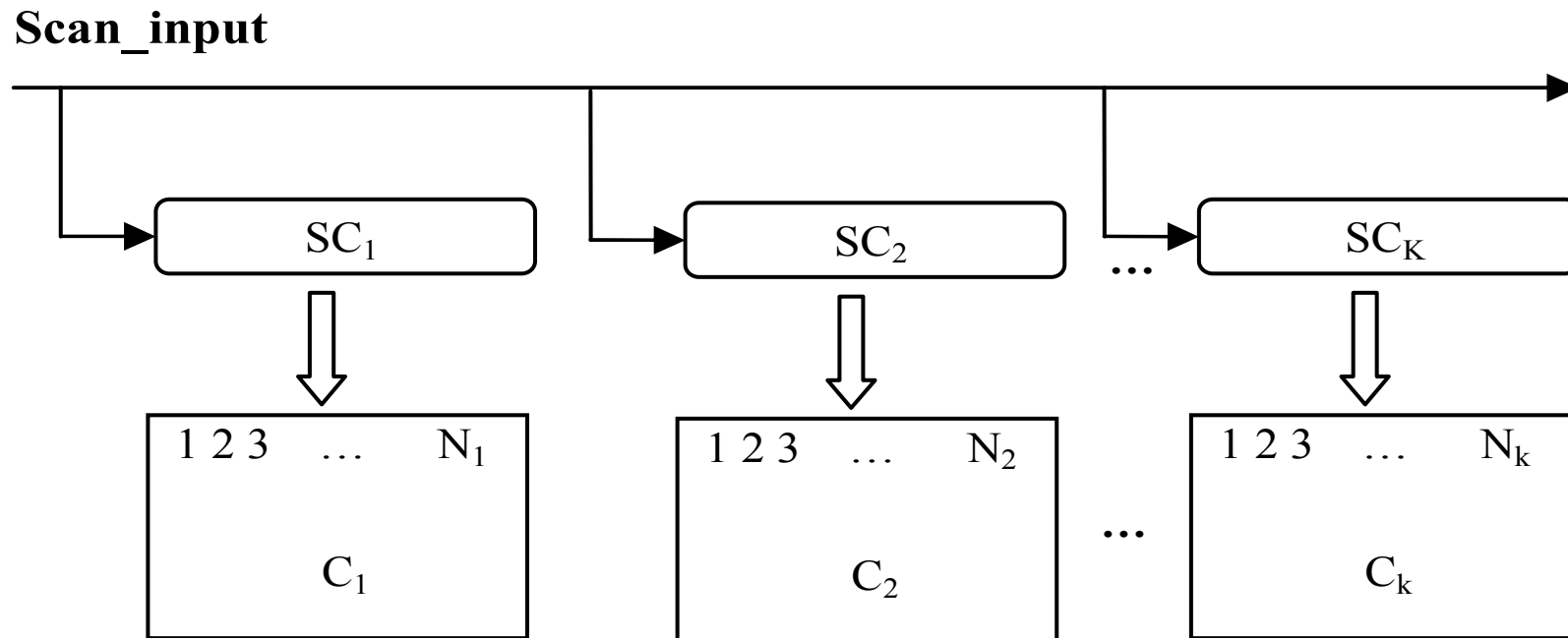

- Broadcasting to scan chains driving independent circuit
- Won't affect fault coverage if all circuits are independent





# Illinois Scan

- Consists of two modes of operations
  - Broadcast mode
  - Serial scan mode
- Main Drawback
  - No test compression in serial scan mode
- Ways to reduce number of patterns
  - Multiple-Input broadcast scan
  - Reconfigurable broadcast scan



# Illinois Scan Architecture

 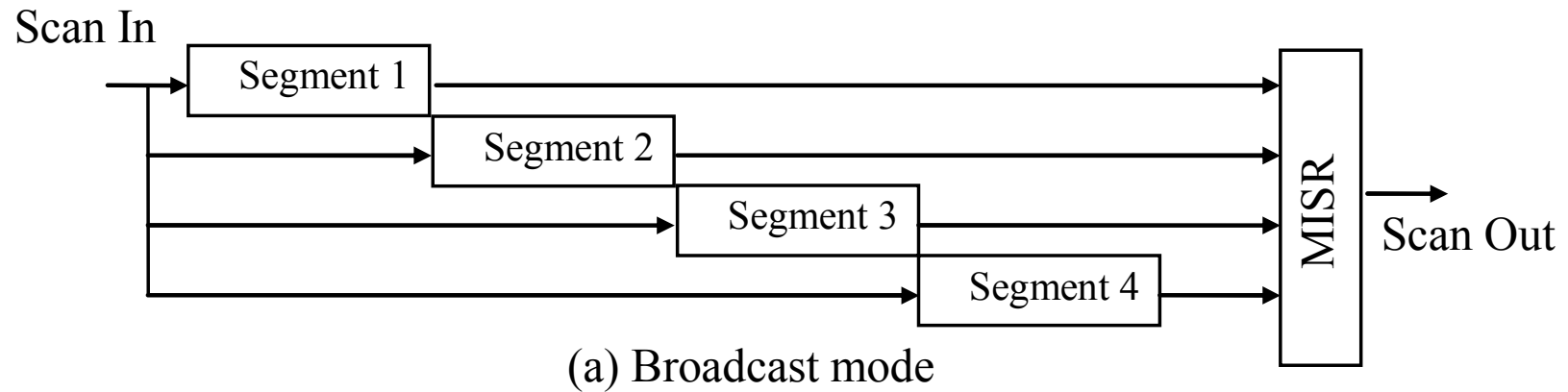

Two Mode of Illinois Scan Architecture



# Multiple-input broadcast scan

- Use more than one channel to drive all scan chains
- The shorter each scan chain is, the easier to detect more faults because fewer constraints are placed on the ATPG




# Reconfigurable Broadcast Scan

- Reduce the number of required channels compared to multiple-input broadcast scan
- Provide the capability to reconfigure the set of scan chains
- Two possible reconfiguration schemes
  - Static reconfiguration
  - Dynamic reconfiguration
    - Need more control information *versus* static reconfiguration




 
## Example MUX Network with Control Line(s) connected only to select pins of the multiplexers




# Virtual Scan

- Use Combinational logic network for stimulus decompression – called Broadcaster
  - Buffers, inverters, AND/OR gates, MUXs, XOR gates
- Advantages
  - One-Step ATPG – No need to solve linear equations as required in sequential linear decompressor.
  - Dynamic compaction can be effectively utilized during the ATPG process.



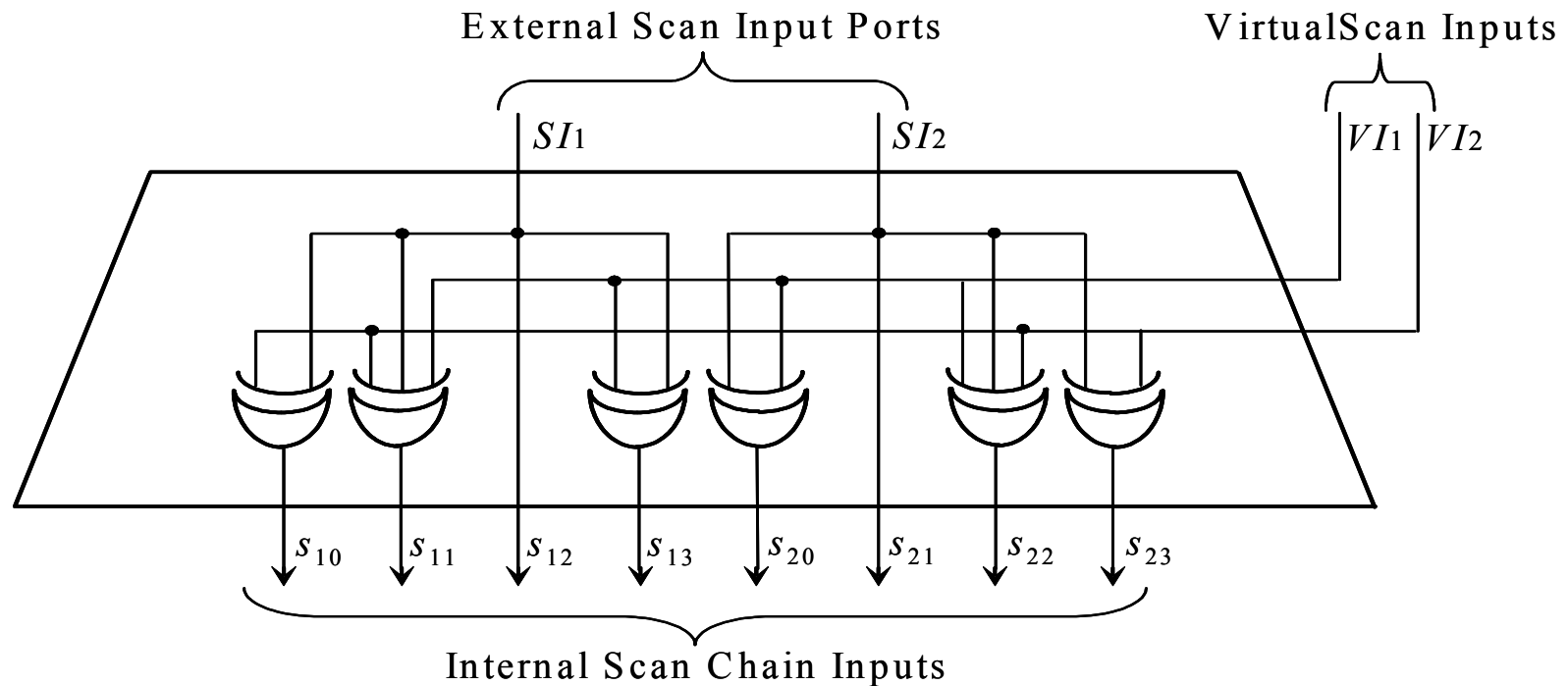
# Example Virtual Scan Broadcaster Using an XOR Network



Broadcaster using an example XOR network with additional VirtualScan Inputs to reduce coverage loss



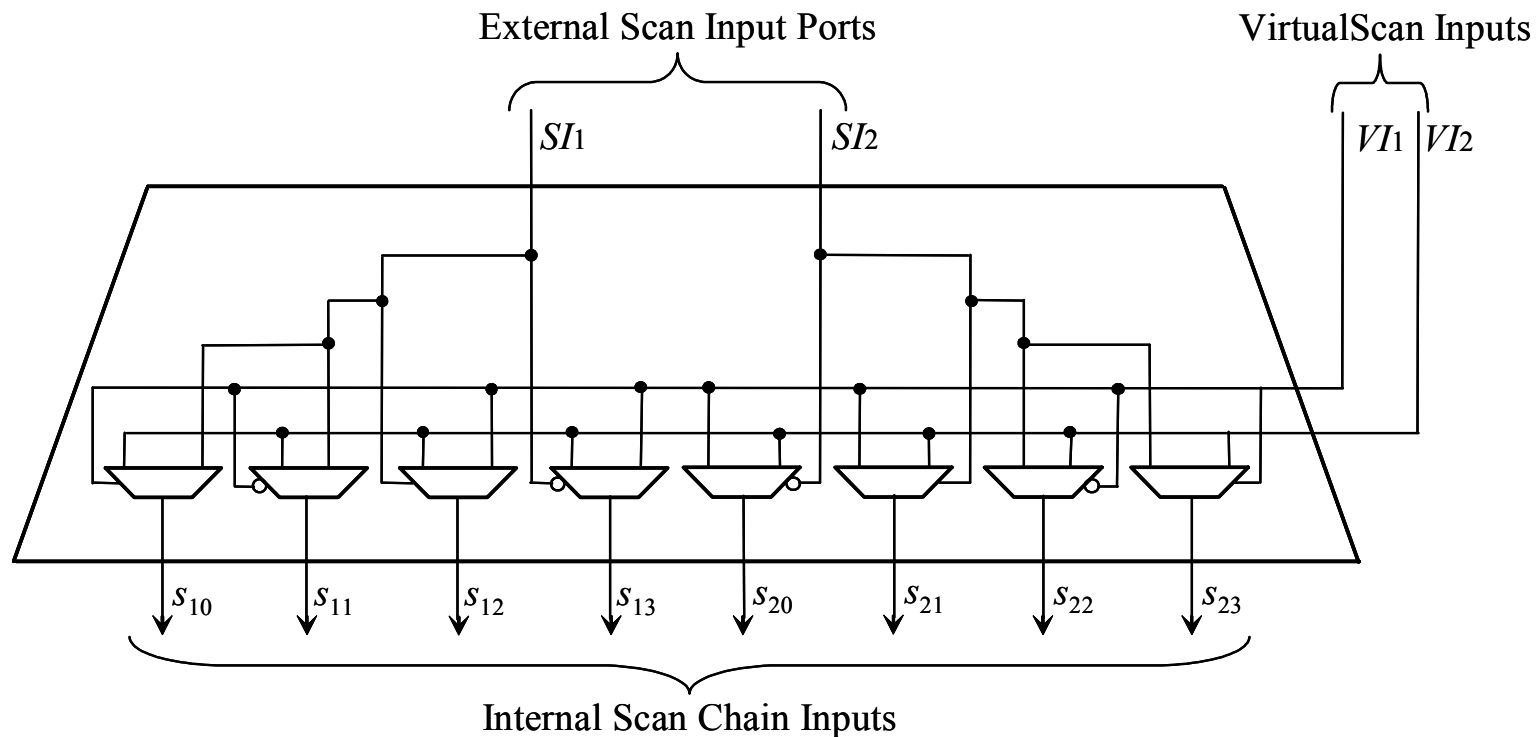
# Example Virtual Scan Broadcaster Using a MUX Network



Broadcaster using an example MUX network with additional VirtualScan inputs that can also be connected to data pins of the multiplexers



# Comparison

 

Encoding flexibility among combinational decompression schemes



*Dr. Shubhajit Roy Chowdhury*

**CVEST, IIIT HYDERABAD**

# Circuits for Test Response Compaction

- Performed at the output of scan chains
- To reduce the amount of test response
- Grouped into three categories
  - Space compaction
  - Time compaction
  - Mixed space and time compaction




# Space Compaction

- Space compactor is combinational
- Inverse procedure of linear expansion
- Compaction Techniques
  - X-Compact
  - X-Blocking
  - X-Masking
  - X-Impact



# X-tolerant Response Compaction

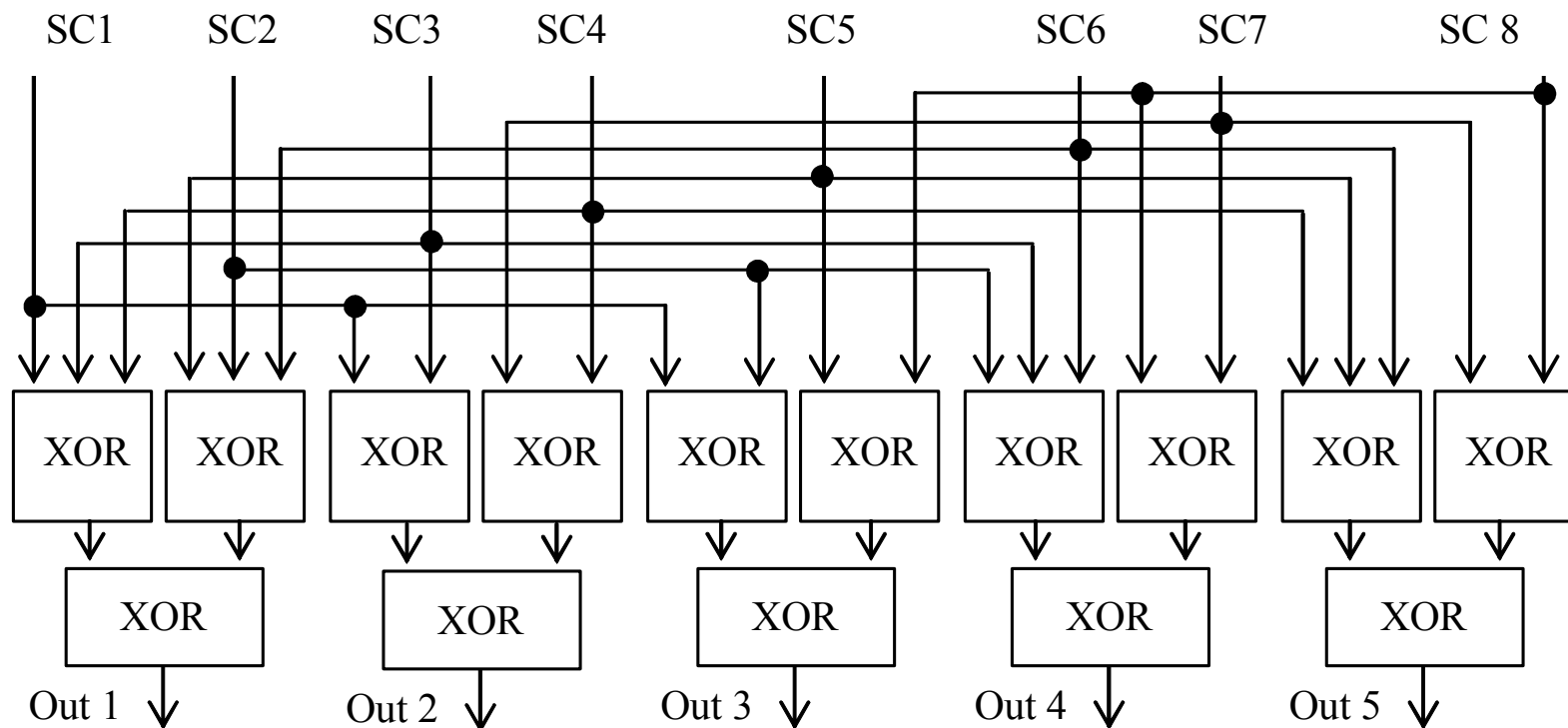

An X-compactor with 8 inputs and 5 outputs






# X-Blocking (X-Bounding)

- Block X's before reaching the response compactor
- Scan design rule checker for identifying potential X-generators
- Impact
  - No X's will be observed
  - Fault coverage loss
  - Add area overhead
  - May impact delay due to the inserted logic


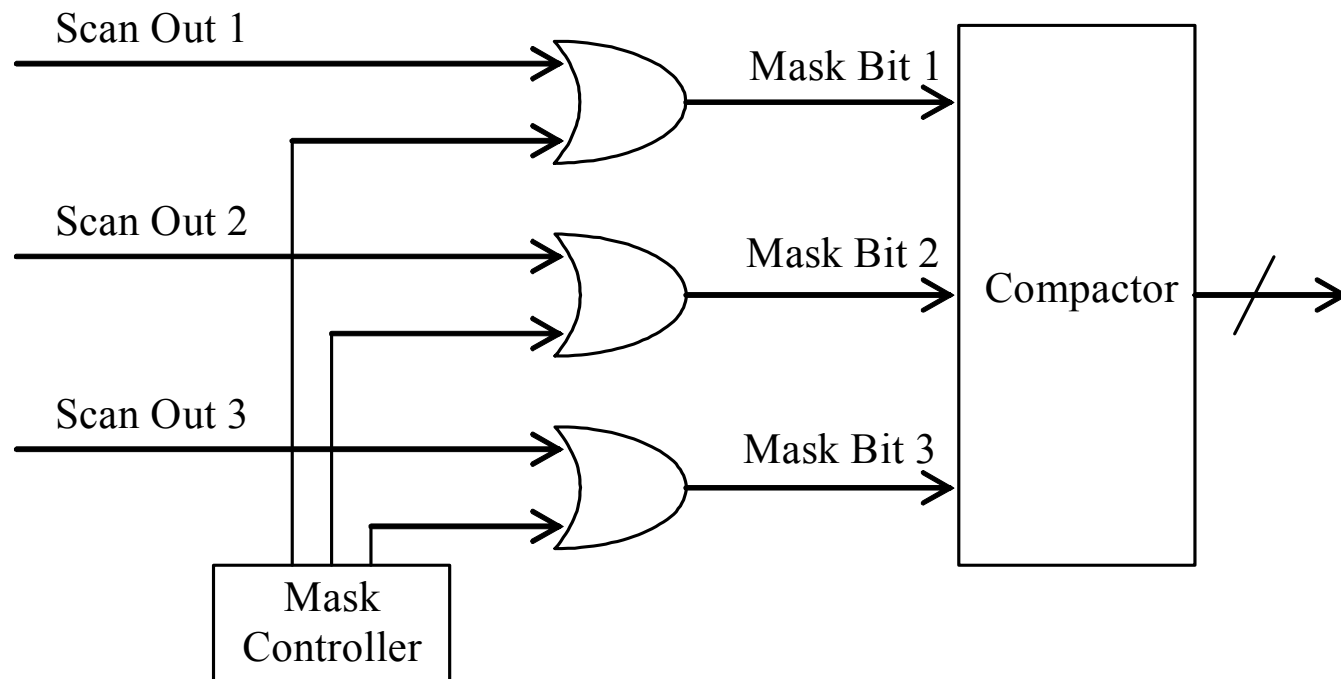
# X-Masking


Mask off X's right before the response compactor



An example X-masking circuit




# X-Impact

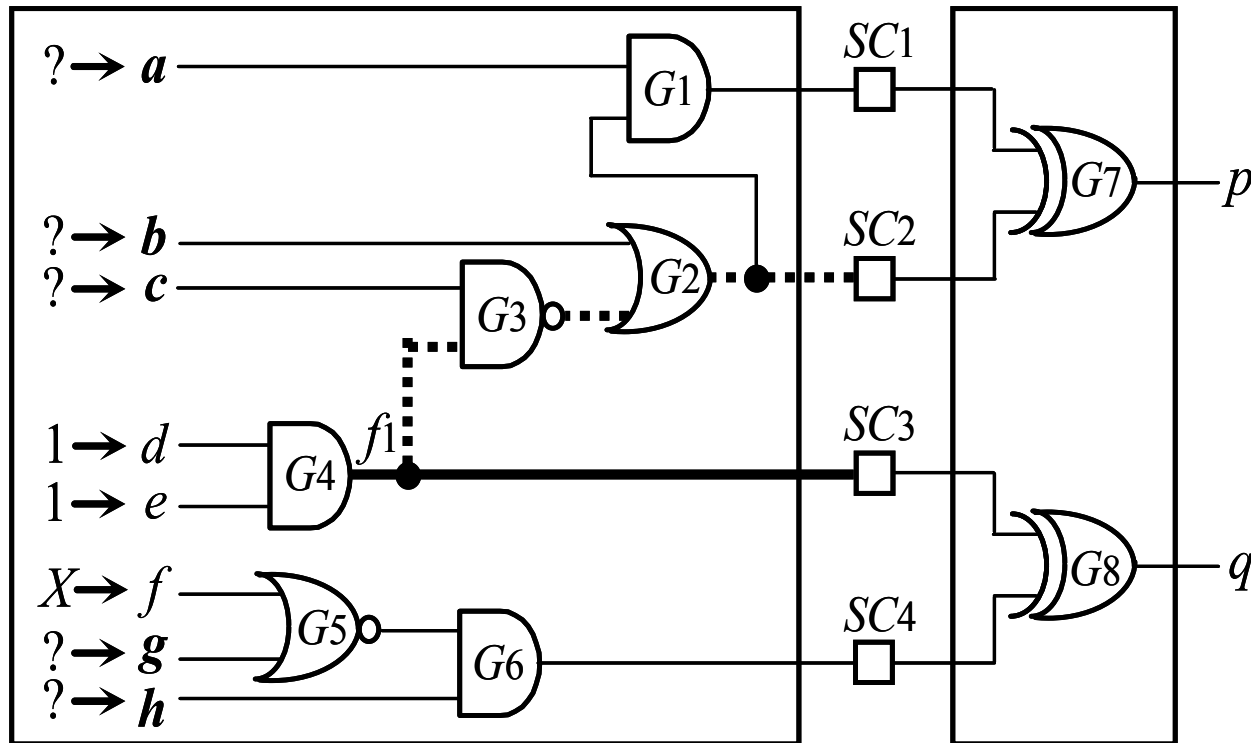

Handling of X-Impact



# X-Impact

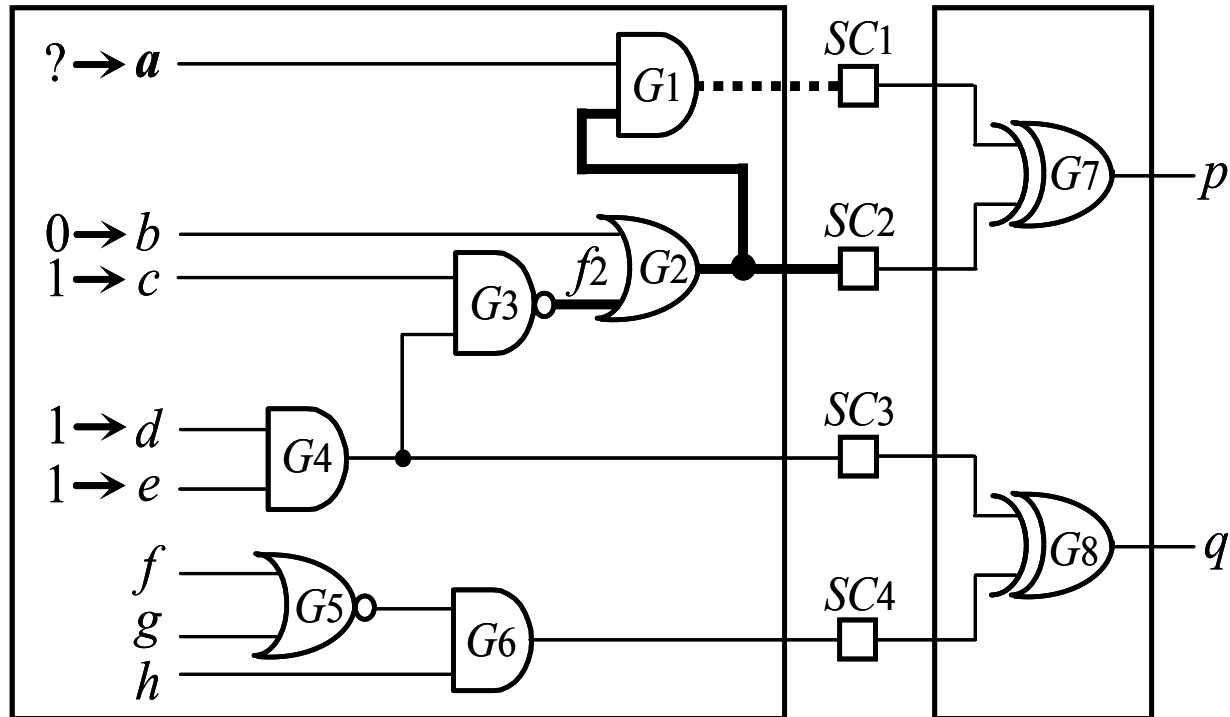

Handling of Aliasing




# Time compaction

- Uses sequential logic to compact test response
- No unknown (X) values are allowed to reach the compactor; otherwise X-bounding, X-masking must be employed.
- MISR is most widely used


 
# Multiple Input Signature Register (MISR)



## Problem to solve

Consider a four stage MISR represented by function  $f(x) = 1 + x + x^4$ . Let  $M0=\{10010\}$ ,  $M1=\{11000\}$ ,  $M2=\{11000\}$  and  $M3=\{10011\}$ .

Evaluate the final signature stored in the MISR.




# Mixed Time and Space Compaction

- Combine the advantages of a time compactor and a space compactor but with high area overhead
- Examples of mixed time and space compactors
  - OPMISR
  - Convolutional Compactor
  - q-compactor
    - No feedback path





# q-compactor

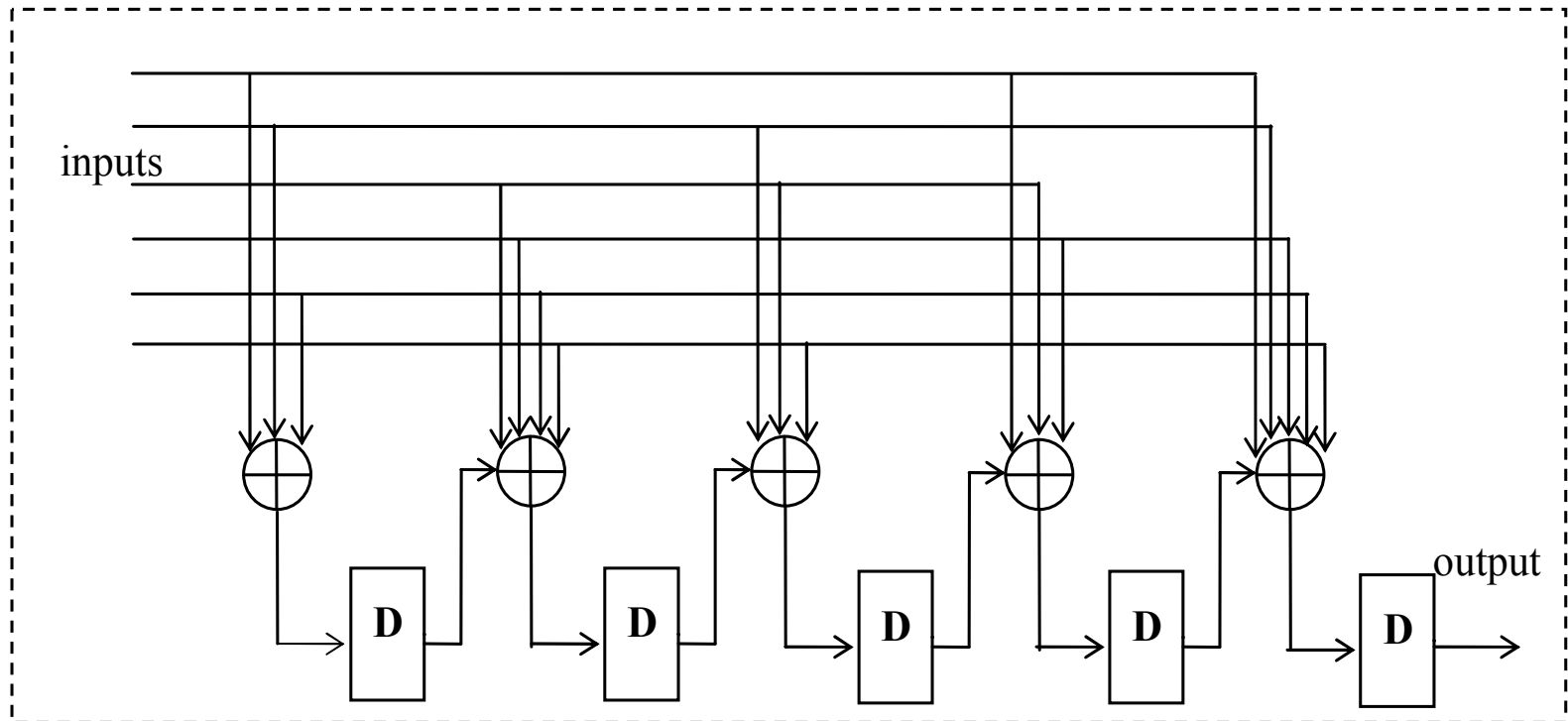

An example q-compactor with single output




# Low-Power Test Compression Architectures

- Low-Power architectures
  - The Bandwidth-match low-power scan design can be used for test compression
- An Example – The UltraScan Architecture
  - Time-Division Demultiplexer (TDDM)
  - Time-Division Multiplexer (TDM)
  - Clock Controller
  - The TDDM/TDM circuit operates at 10 MHz and slow down the shift clock frequency to 1 MHz resulting in 10X reduction in shift power dissipation



# UltraScan

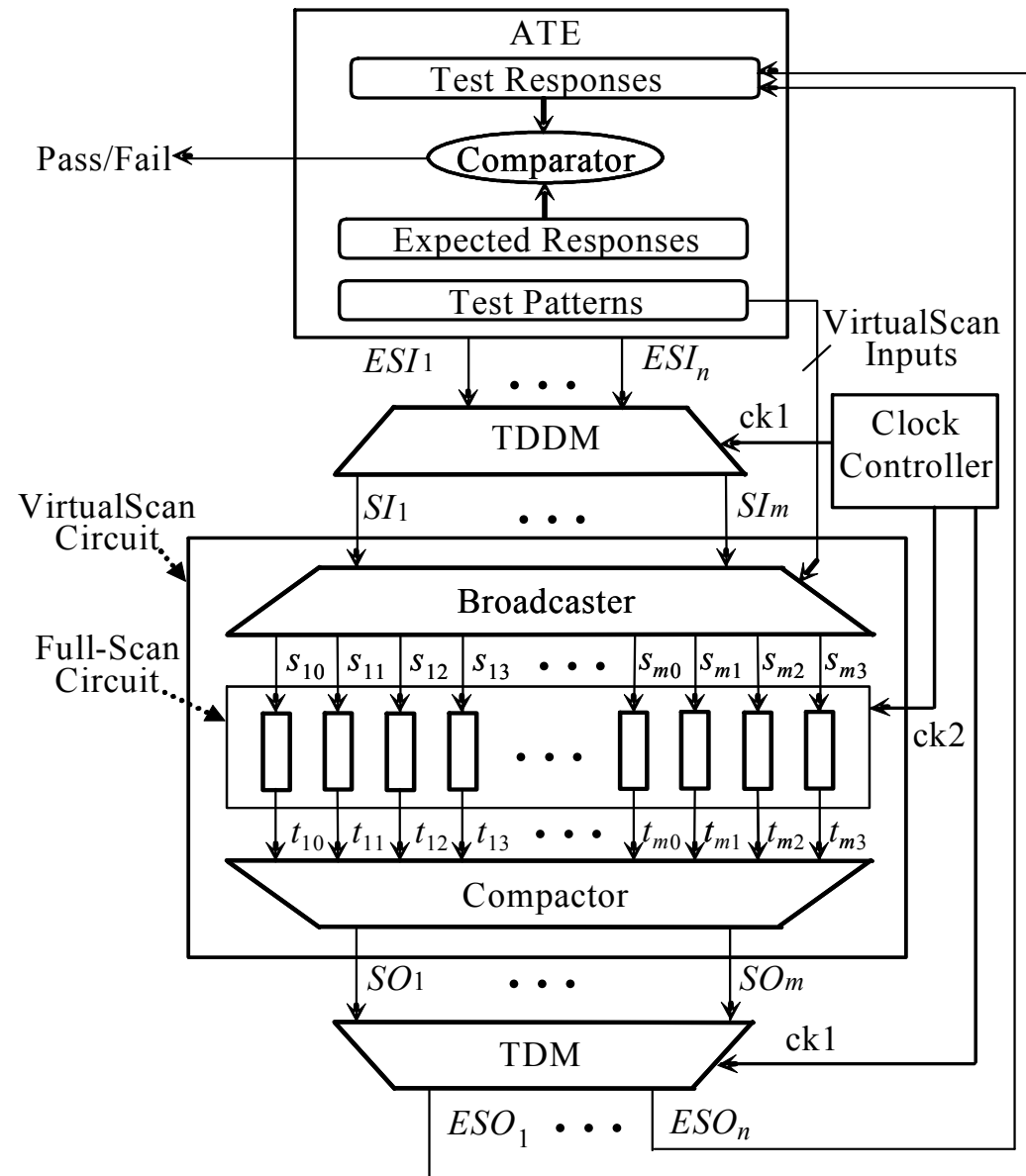

# Questions?



*Dr. Shubhajit Roy Chowdhury*

**CVES*T*, IIIT HYDERABAD**