

Two-level Logic Synthesis and Optimization

Dr. Shubhajit Roy Chowdhury,

Centre for VLSI and Embedded Systems Technology,
IIIT Hyderabad, India

Email: src.vlsi@iiit.ac.in



Dr. Shubhajit Roy Chowdhury

CVES, IIIT HYDERABAD

Circuit Optimization

- **Goal: To obtain the simplest implementation for a given function**
- **Optimization is a more formal approach to simplification that is performed using a specific procedure or algorithm**
- **Optimization requires a cost criterion to measure the simplicity of a circuit**
- **Distinct cost criteria we will use:**
 - Literal cost (L)
 - Gate input cost (G)
 - Gate input cost including inverters (GN)



Literal Cost

- Literal – a variable or its complement
- Literal cost – the number of literal appearances in a Boolean expression corresponding to the logic circuit diagram
- Example: Boolean expressions for F
 - $F = B D + A \bar{B} C + A \bar{C} \bar{D}$ L = 8
 - $F = B D + A \bar{B} C + A \bar{B} \bar{D} + A B \bar{C}$ L = 11
 - $F = (A+B)(A+D)(B+C+\bar{D})(\bar{B}+\bar{C}+D)$ L = 10
 - Which solution is best?

First solution is best



Gate Input Cost

- Gate Input Cost: Count of total number of inputs to the gates in the logic circuit implementation

- Two gate input costs are defined:

G = Count of gate inputs without counting Inverters

GN = Count of gate inputs + count of Inverters

- For SOP and POS equations, the gate input cost can be found from the Boolean expression by finding the sum of:

- All literal appearances
- Number of terms excluding single literal terms (added to G)
- Number of distinct complemented single literals (added to GN)

- Example:

$$F = B D + \overline{A} \overline{B} C + \overline{A} \overline{C} \overline{D}$$


$$L = 8$$

$$G = L + 3 = 11$$



Cost Criteria

 - Example:
- $F = A B C + \bar{A}\bar{B}\bar{C}$
- $L = 6 \quad G = 8 \quad GN = 11$
- $F = (A + \bar{C})(\bar{B} + C)(\bar{A} + B)$
- $L = 6 \quad G = 9 \quad GN = 12$
- Same function and same literal cost
- But first circuit has better gate input count and better gate input count with NOTs
- Select first circuit!



Cost Criteria Summary

- Literal Count:
 - Simple to evaluate by counting all literals
 - However, does not represent circuit complexity accurately in all cases
- Gate Input Cost (or Count):
 - Good measure of logic implementation
 - Proportional to the number of transistors and wires used in the implementation
 - Important when measuring cost of circuits with more than two levels




Boolean Function Optimization

- Minimizing the gate input (or literal) cost of a Boolean equation reduces the circuit cost
- We choose gate input cost
- Boolean Algebra and graphical techniques are tools to minimize cost criteria values
- Some important questions:
 - When do we stop trying to reduce the cost?
 - Do we know when we have a minimum cost?
- Treat optimum or near-optimum cost functions for two-level (SOP and POS) circuits first
- Introduce a graphical technique using Karnaugh maps (K-maps for short)




General Logic Structure

 

- Combinational optimization
 - keep latches/registers at current positions, keep their function
 - optimize combinational logic in between
- Sequential optimization
 - change latch position/function (retiming)



What is logic synthesis?

 

Given: Finite-State Machine $F(X, Y, Z)$, where:

X : Input alphabet

Y : Output alphabet


Z : Set of internal states

$\lambda : X \times Z \rightarrow Z$ (next state function, *Boolean*)

$\delta : X \times Z \rightarrow Y$ (output function, *Boolean*)



Combinational logic

 


Sequential logic

Target: Circuit $C(G, W)$ where:

- G : set of circuit components
{Boolean gates, flip-flops, etc}
- W : set of wires connecting G



Basic Model of Sequential Circuit: FSM

 

$M(X, Y, S, S_0, \delta, \lambda)$:

X : Inputs

Y : Outputs

S : Current State

S_0 : Initial State(s)

δ : $X \times S \rightarrow S$ (next state function)

λ : $X \times S \rightarrow Y$ (output function)

Sequential synthesis:

find (multi-level) implementation of $\delta(X)$ and $\lambda(X)$ that minimize its cost (area, delay, power)

Delay elements:

- **Clocked**: synchronous
 - single-phase clock, multiple-phase clocks
- **Unclocked**: asynchronous



Optimization Criteria for Synthesis


The optimization criteria for logic optimization is to *minimize* some function of:

- Area occupied by the logic gates and interconnect (approximated by literals = transistors in technology independent optimization)
- Critical path delay of the longest path through the logic
- Degree of testability of the circuit, measured in terms of the percentage of faults covered by a specified set of test vectors for an approximate fault model (e.g. single or multiple stuck-at faults)
- Power consumed by the logic gates
- Noise Immunity
- Place-ability, Wire-ability

while simultaneously satisfying misc. constraints



Two-Level (PLA) vs. Multi-Level

 


PLA

- control logic
- constrained layout
- highly automatic
- technology independent
- multi-valued logic
- input, output, state encoding

Very predictable

E.g. Standard Cell Layout

 


Multi-level Logic

- all logic
- general (standard cells, macro cells, blocks)
- automatic
- partially technology independent
- part of multi-level logic


Very hard to predict



Two-level Logic: the PLA

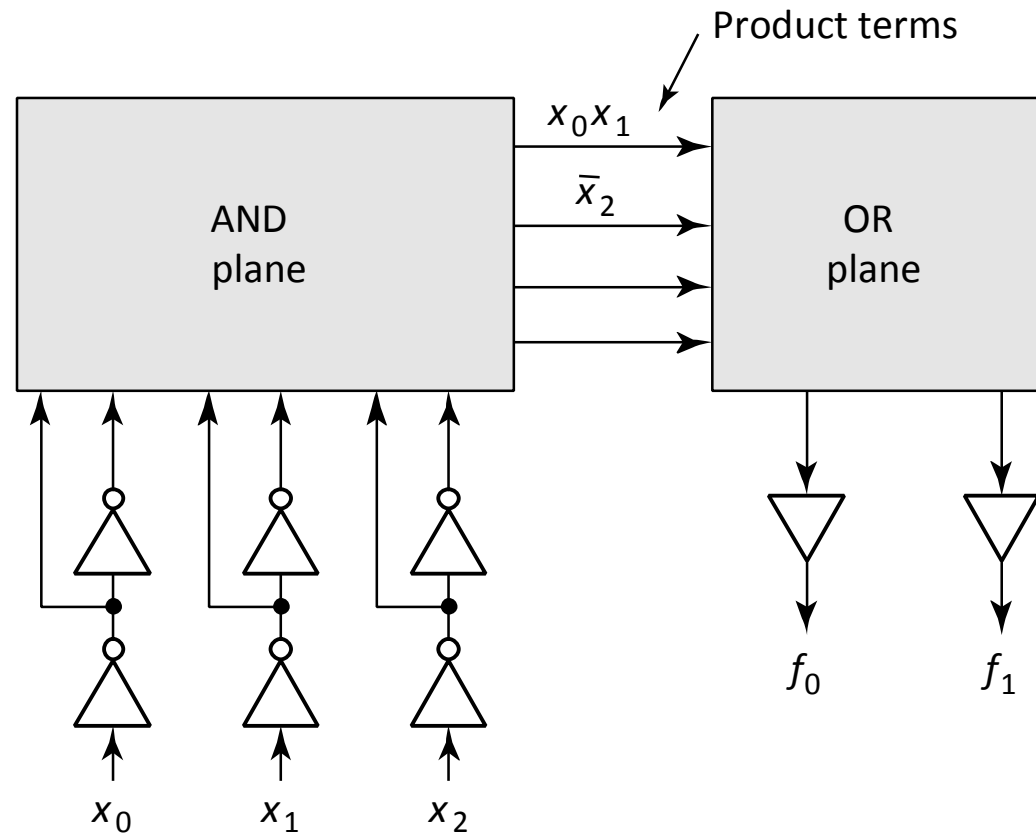

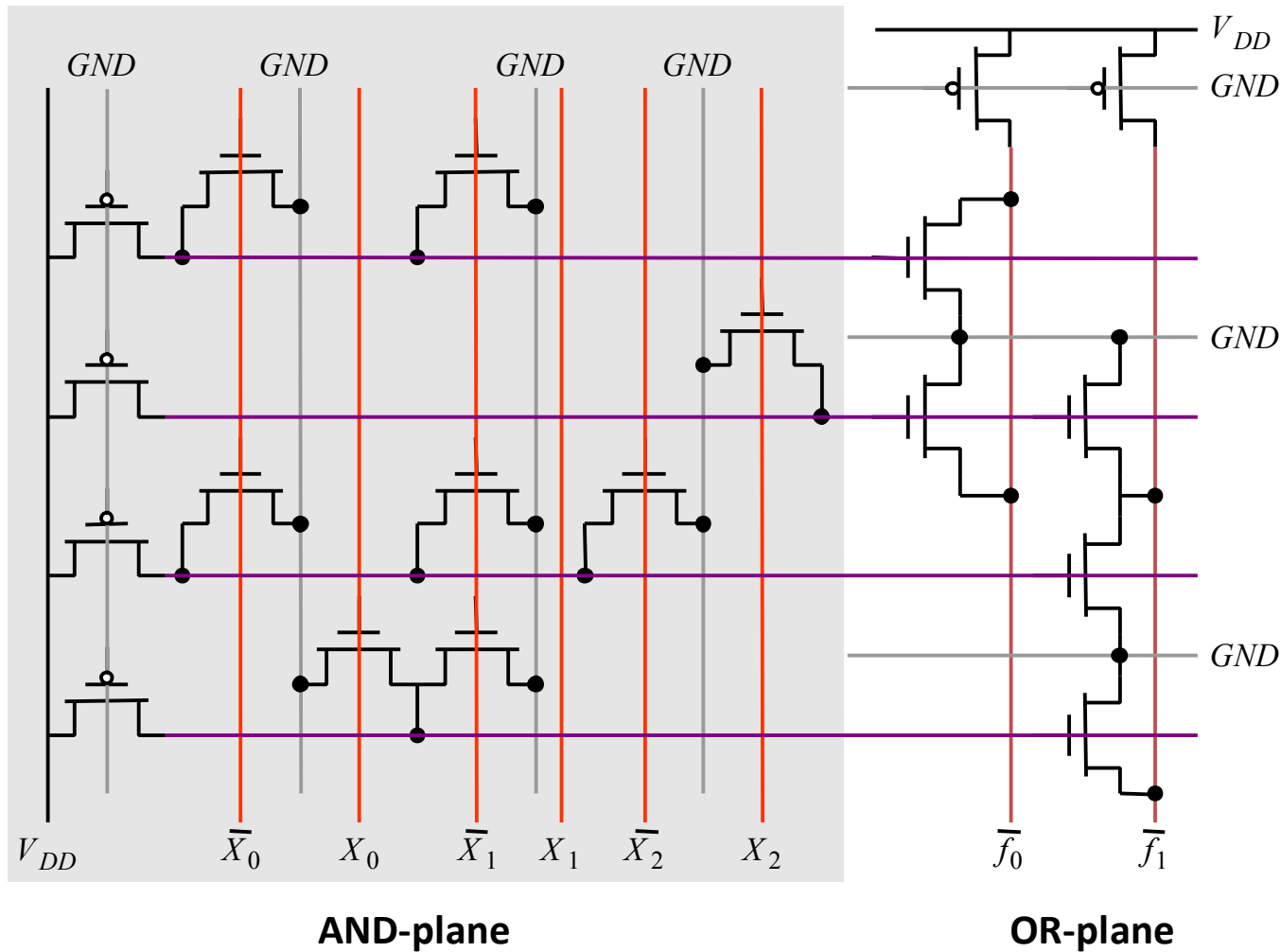Programmable Logic Array: Pseudo NMOS PLA



Multiple-Level Optimization

- Multiple-level circuits - circuits that are more than two levels (inverters are not counted)
- Multiple-level circuits can have reduced gate input cost compared to two-level (SOP and POS) circuits
- Multiple-level optimization is performed by applying transformations to circuits represented by equations while evaluating cost



Transformations

- **Factoring**: finding a factored form from SOP or POS expression
 - **Decomposition**: expressing a function as a set of new functions
 - **Substitution** of H into F: Expressing F as a function of H and some of its original variables
 - **Elimination**: Inverse of substitution, called also flattening
 - **Extraction**: decomposition applied to multiple functions simultaneously
-



Factorization

- Algebraic Factoring

$$F = \bar{A} \bar{C} \bar{D} + \bar{A} B \bar{C} + A B C + A C \bar{D} \quad (G = 16)$$

- Factoring:

$$F = \bar{A} (\bar{C} \bar{D} + B \bar{C}) + A (B C + C \bar{D}) \quad (G = 16)$$

- Factoring again:

$$F = \bar{A} \bar{C} (B + \bar{D}) + A C (B + \bar{D}) \quad (G = 12)$$

- Factoring again:

$$F = (\bar{A} \bar{C} + A C) (B + \bar{D}) \quad (G = 10)$$

This factoring example has reduced G from 16 to 10
Resulting circuit has three levels plus input inverters



Decomposition Example

- Given the following function:

$$F = (A (B + C) + D) (B + C) \quad (G = 10)$$

- Define 2 new functions X and Y as follows:

$$X = (B + C) \text{ and } Y = (A X + D)$$

- Then function F can be decomposed as follows:

$$F = X Y, \text{ where}$$

$$X = (B + C) \text{ and}$$

$$Y = (A X + D) \quad (G = 8)$$



Elimination

- Given a set of functions:

$$X = B + C, \quad Y = A + B, \quad \text{and} \quad Z = \bar{A} X + C Y \quad (G = 10)$$

- Eliminate X and Y from Z :

$$Z = \bar{A} (B + C) + C (A + B) \quad (G = 10)$$

- Flatten Z (Convert to SOP expression):

$$Z = \bar{A} B + \bar{A} C + A C + B C \quad (G = 12)$$

- Two-Level Optimization (using K-map):

$$Z = \bar{A} B + C \quad (G = 4)$$

This example shows that elimination begins with any set of functions. It can increase gate input cost (G) temporarily, but can result in a final solution with optimum cost (G)



Substitution

- Given the following function:

$$H = A(\bar{C} + \bar{D})(E + F) + B C D \bar{E} \bar{F} \quad (G = 14)$$

- Define X and Y as new functions :

$$X = C D \text{ and } Y = E + F$$

- The complement of X and Y are:

$$\bar{X} = (\bar{C} + \bar{D}) \text{ and } \bar{Y} = \bar{E} \bar{F}$$

- Substitute $C D$ with X and $(\bar{C} + \bar{D})$ with \bar{X}

Substitute $(E + F)$ with Y and $\bar{E} \bar{F}$ with \bar{Y}

$$H = A \bar{X} Y + B X \bar{Y}$$

$$\text{where, } X = C D \text{ and } Y = E + F \quad (G = 12)$$



Extraction

- Given the following two functions:

$$E = A B D + A B D$$

$$H = B C D + B C D \quad (G = 16)$$

- Find a common factor for E and H
- Define the common factor as a function:

$$F = B D + B D$$

- Perform extraction by expressing E and H as a function of F:

$$F = B D + B D, E = A F, H = C F \quad (G = 10)$$

- Reduced cost because of the sharing of F



Thank You!!!



Dr. Shubhajit Roy Chowdhury

CVES^T, IIIT HYDERABAD