

VLSI Design

CMOS Inverter



C CMOS Inverter

- Series connection of nmos and pmos
- DC characteristics
- Solving $V_{inn}=V_{inp}$ and $I_{dsn}=I_{dsp}$
- Regions of operations – 5
 - $0 < V_{in} < V_{tn}$,
 - $V_{in} = V_{DD/2}$
 - $V_{in} > V_{in} - V_{DD}$,
 - $V_{tn} < V_{in} < V_{DD/2}$,
 - $V_{DD/2} < V_{in} < V_{DD} + V_{tp}$,

C CMOS Inverter

- β_n/β_p ratio effect
- Noise margin
 - Allowable noise at i/p
 - o/p should not get affected
- Inverter as an Amplifier
 - Formula

Static load inverters

- Many other forms
- Resistor – transistor in linear region
- Current source – in saturation region
- Pseudo nMOS inverter
- Saturated load inverters
 - NMOS
 - PMOS