

## Intro to VLSI


### Assignment #4

Deadline: 22<sup>nd</sup> March 2012 (In Class)

 Q1. Find dynamic power for the following circuit.

Assume  $V_{DD} = 3V$ ,  $f_{clk} = 1.5 \text{ GHz}$  and inputs have following probability values that change on +ive edge of clock.

$P(A=1) = 0.5$ ,  $P(B=1) = 0.3$ ,  $P(C=1) = 0.2$ ,  $P(D=1) = 0.1$



Q2. Considering all NMOS transistors to be of same dimensions (W/L) in a 3-input XOR gate, find the dimensions of an equivalent transistor.

Q3. The path from the data cache to the register file of a microprocessor involves 500 ps of gate delay and 500 ps of wire delay along a repeated wire. The chip is scaled using constant field scaling and reduced height wires to a new generation with  $S=2$ . Estimate the gate and wire delays of the path. By how much did the overall delay improve?

Q4. Find the rising and falling propagation delays of a 2-1 AOI (And-Or-Invert) gate using the Elmore delay model.

Q5. Describe the various limitations in CMOS scaling.