

Read Only Memory Architecture

Dr. Shubhajit Roy Chowdhury,

Centre for VLSI and Embedded Systems Technology,
IIIT Hyderabad, India


Email: src.vlsi@iiit.ac.in




Dr. Shubhajit Roy Chowdhury

CVEST, IIIT HYDERABAD


Read-Only Memory Cells

 




Diode ROM

 


MOS ROM 1

 


MOS ROM 2

   

MOS OR ROM

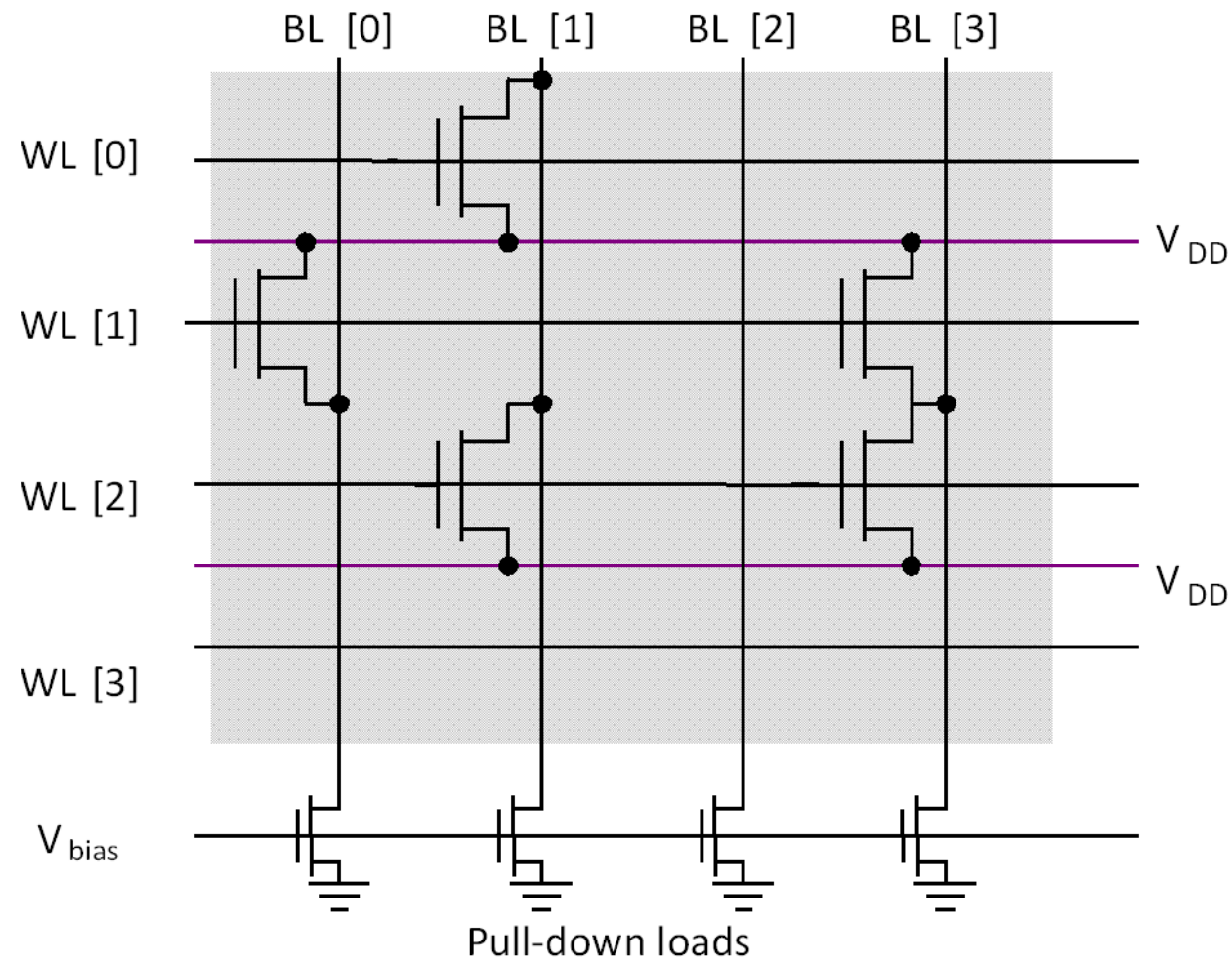


MOS NOR ROM

  
 



MOS NOR ROM Layout

Cell ($11\lambda \times 7\lambda$)




Programming using
the Contact Layer Only

-  Polysilicon
-  Metal1
-  Diffusion
-  Metal1 on Diffusion




MOS NAND ROM

 

All word lines high by default with exception of selected row




MOS NAND ROM Layout

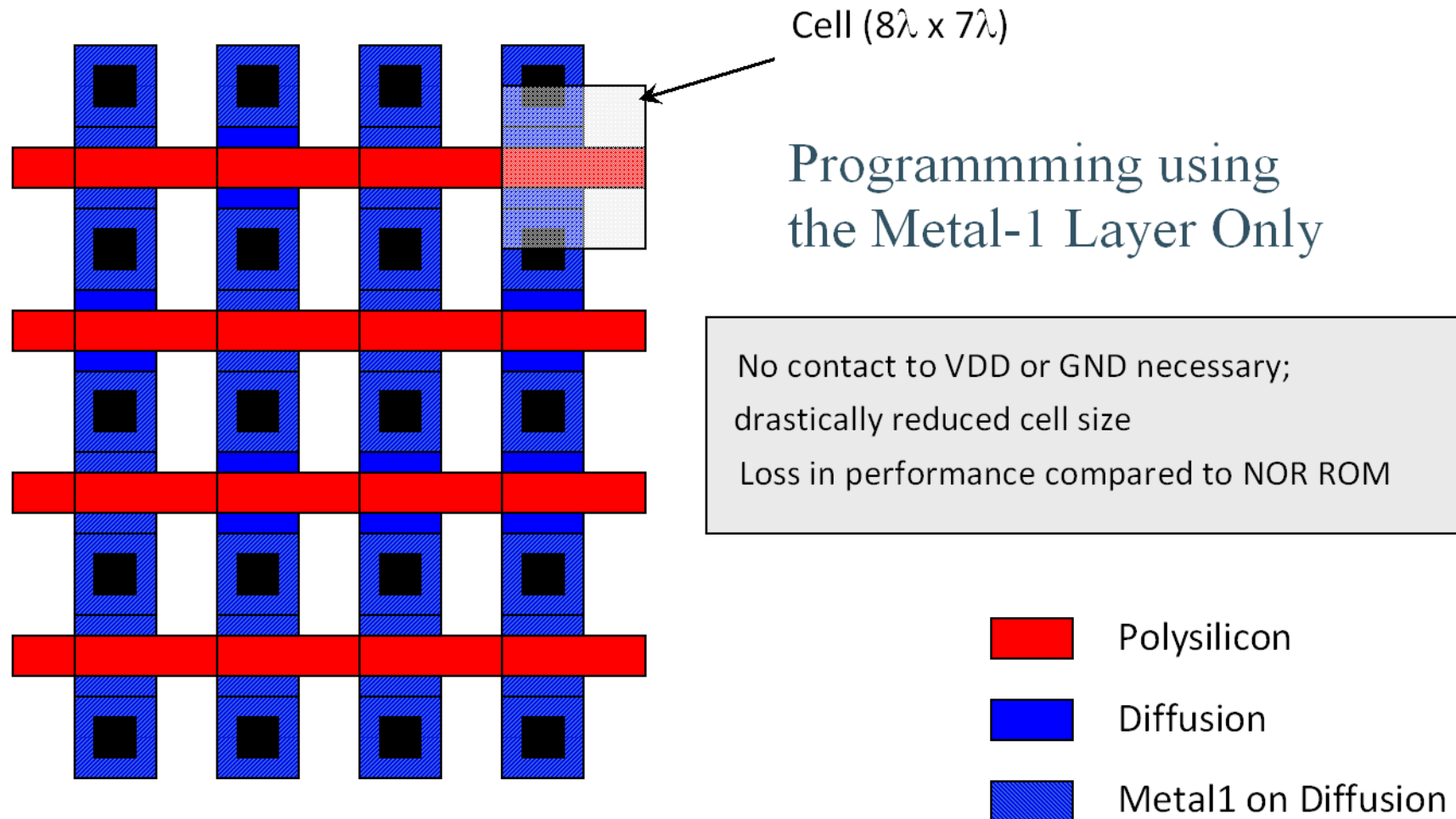




NAND ROM Layout

 Cell ($5\lambda \times 6\lambda$)




Programmming using
Implants Only

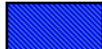-  Polysilicon
-  Threshold-altering implant
-  Metal1 on Diffusion



Equivalent Transient Model for MOS NOR ROM

Model for NOR ROM

 


- Word line parasitics
 - Wire capacitance and gate capacitance
 - Wire resistance (polysilicon)
- Bit line parasitics
 - Resistance not dominant (metal)
 - Drain and Gate-Drain capacitance



Equivalent Transient Model for MOS NAND ROM


Model for NAND ROM

 


- ❑ Word line parasitics
 - Similar to NOR ROM
- ❑ Bit line parasitics
 - Resistance of cascaded transistors dominates
 - Drain/Source and complete gate capacitance



Decreasing Word Line Delay

 

 (a) Driving the word line from both sides




(b) Using a metal bypass

(c) Use silicides



Precharged MOS NOR ROM

 


PMOS precharge device can be made as large as necessary,
but clock driver becomes harder to design.




Non-Volatile Memories

The Floating-gate transistor (FAMOS)

 


Device cross-section

 


Schematic symbol




Floating-Gate Transistor Programming

 

Avalanche injection

 

 
Removing programming voltage leaves charge trapped




Programming results in higher V_T .




A “Programmable-Threshold” Transistor

 

FLOTOX EEPROM

 


FLOTOX transistor

 

Fowler-Nordheim
I-V characteristic





EEPROM Cell

 

Absolute threshold control
is hard
Unprogrammed transistor
might be depletion
⇒ 2 transistor cell




NAND Flash Memory

 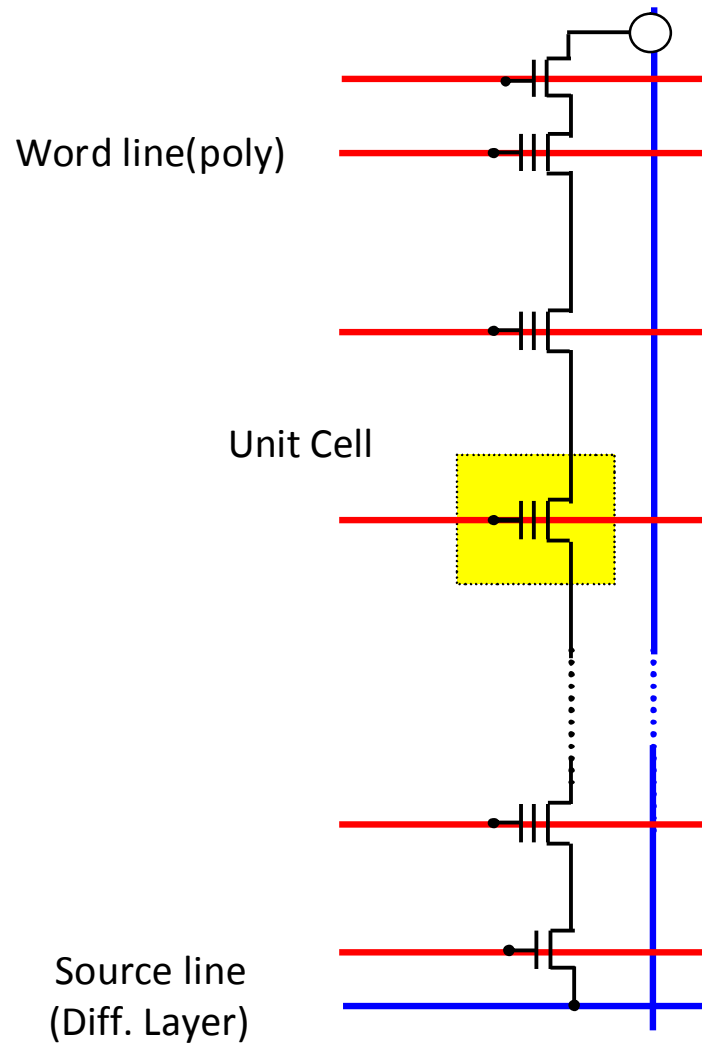

Courtesy Toshiba



NAND Flash Memory

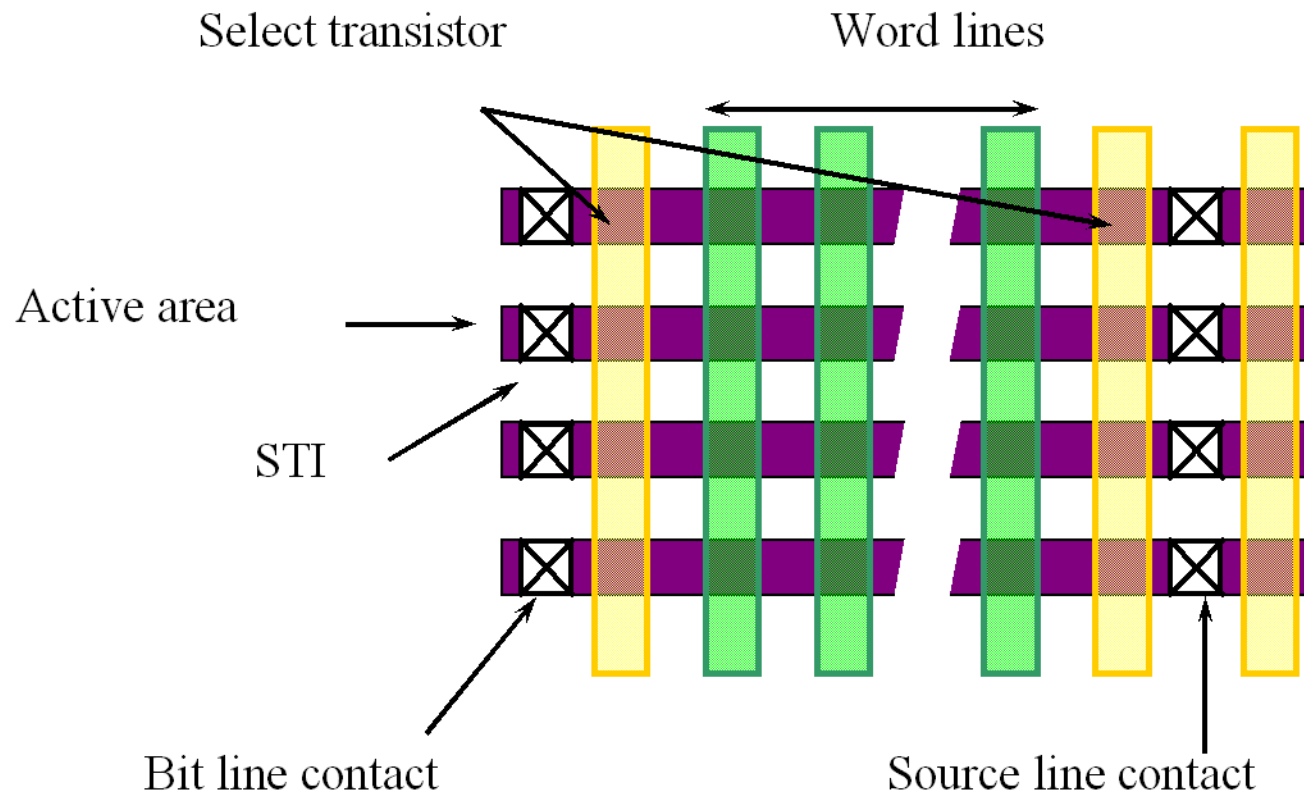

Courtesy Toshiba



Characteristics of State-of-the-art NVM

Table 12-1 Comparison between nonvolatile memories ([Itoh01]).



$V_{DD} = 3.3$ or 5 V; $V_{PP} = 12$ or 12.5 V.

	Cell— Nr. of Transistors	Cell Area (ratio wrt EPROM)	Mechanism		External Power Supply		Program/ Erase Cycles
			Erase	Write	Write	Read	
MASK ROM	1 T (NAND)	0.35–5	—	—	—	V_{DD}	0
EPROM	1 T	1	UV Exposure	Hot electrons	V_{PP}	V_{DD}	~100
EEPROM	2 T	3–5	FN Tunneling	FN Tunneling	V_{PP} (int)	V_{DD}	10^4 – 10^5
Flash Memory	1 T	1–2	FN Tunneling	Hot electrons	V_{PP}	V_{DD}	10^4 – 10^5
			FN Tunneling	FN Tunneling	V_{PP} (int)	V_{DD}	10^4 – 10^5



Building Logic with ROMs

  - Use ROM as lookup table containing truth table
 - n inputs, k outputs requires 2^n words \times k bits
 - Changing function is easy – reprogram ROM
- Finite State Machine
 - n inputs, k outputs, s bits of state
 - Build with $2^{n+s} \times (k+s)$ bit ROM and $(k+s)$ bit register



THANK YOU



Dr. Shubhajit Roy Chowdhury

CVES, IIT HYDERABAD