

Overview of Fault Models

Dr. Shubhajit Roy Chowdhury,

Centre for VLSI and Embedded Systems Technology,

IIIT Hyderabad, India

Email: src.vlsi@iiit.ac.in



Dr. Shubhajit Roy Chowdhury


CVES, IIIT HYDERABAD

Why Fault Models?

- ❑ **Too many actual number of physical defects in circuits.**
 - Not possible to consider individually.
 - Difficult to analyze.
- ❑ **Some logical fault models are considered.**
 - A fault model identifies targets for testing.
 - Drastically reduces number of faults to be handled.
 - Makes analysis possible.
 - Effectiveness measurable by experiments.



Levels of abstraction in circuits

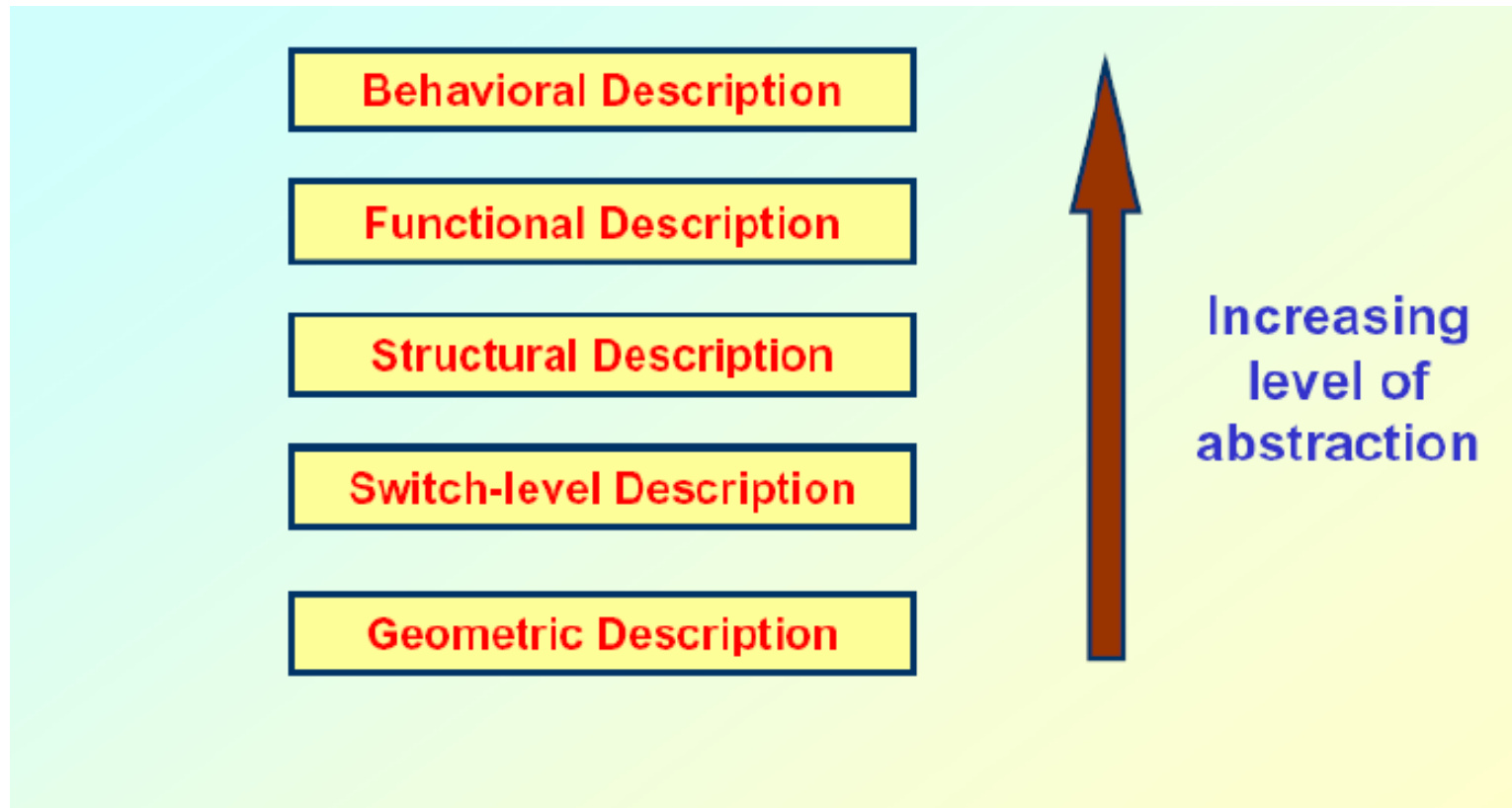

Observations

- ❑ Faults modeled at the lowest level of abstraction will be more accurate.
 - Will resemble closely with actual physical defects.
- ❑ Typically higher-level abstractions are used.
 - To reduce complexity.
 - **An example:**
 - 50 million transistors
 - 500 million possible defects
 - 5 million gates



Fault Models at Different Levels

❑ Behavioral Fault Model

- Related to failure modes of the constructs in HDL.
- Ex: assignment, condition failures etc.

❑ Functional Fault Model

- Try to ensure that the given functional block executes the function it was designed for.
- Ex: Adder, Multiplexer etc.

❑ Structural Fault Model

- The circuit is given as a netlist of blocks.
- Here we try to make sure that the interconnections in the given structure are fault-free, and are able to carry both '0' and '1' signals.
 - The blocks (e.g. gates) assumed to be fault-free.
 - Leads to the *stuck-at-fault* model.



Stuck at fault model

❑ Stuck-at-Fault Model:

- Some line(s) in the circuit are permanently stuck at logic 0 or logic 1
- Denoted as s-a-0 & s-a-1, or as a/0 & a/1 for line 'a'.
- A fan-out stem and fan-out branches are considered different lines.

❑ Two Variants:

- **Single Stuck-at-Fault**
 - 'k' lines \rightarrow '2k' number of faults
- **Multiple Stuck-at-Fault**
 - 'k' lines \rightarrow ' 3^k-1 ' number of faults




Stuck at fault

❑ Why single stuck-at faults?

- Simpler to handle & reasonably good fault coverage.
- A test set for detecting single stuck-at faults detects a large percentage of multiple stuck-at faults as well.
- Technology independent. Can be applied to TTL, ECL, CMOS etc.
- It is design style independent. Applicable to all design styles: Gate array, standard cell, full custom, etc.

❑ Example:

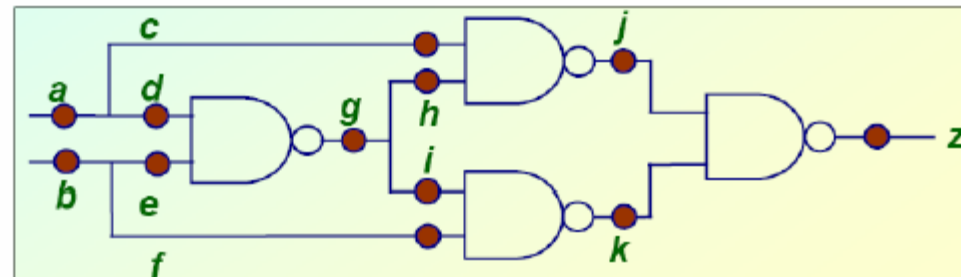

- ❑ 12 lines (a, b, c, d, e, f, g, h, i, j, k, z) of faults
- ❑ $2 \times 12 = 24$ single stuck-at-faults
- ❑ $3^{12} - 1 = 5,31,441$ multiple stuck-at-faults



Fault Models at different levels

❑ Switch-Level Fault Model

- Deals with faults in netlist of transistors in a switch-level description of a circuit.
 - MOS transistors considered as ideal switch.
- Two kinds of faults:
 - *Stuck-open fault and Stuck-short fault*


❑ Geometric Fault Model

- Derived directly from the layout of the circuit.
- Some examples of geometric fault models:
 - Bridging fault model
 - PLA fault model
 - Memory fault model





Bridging Fault Models

 - Tests for resistive shorts between two normally unconnected nets
- Closest fault-model to real defects
- Bridging-faults are caused by manufacturing defects




  Feedback versus Non-feedback Bridging Fault



Delay Faults

 - Affect propagation delay of the circuit, circuit fails at high speeds
- More important for high-speed circuits
- Gate delay fault (GDF): slow 1-to-0 or 0-to-1 transition at a gate output
- Path delay fault (PDF): exists a path from a primary input to primary output that is slow to propagate a 0-to-1 or 1-to-0 transition



Questions?

