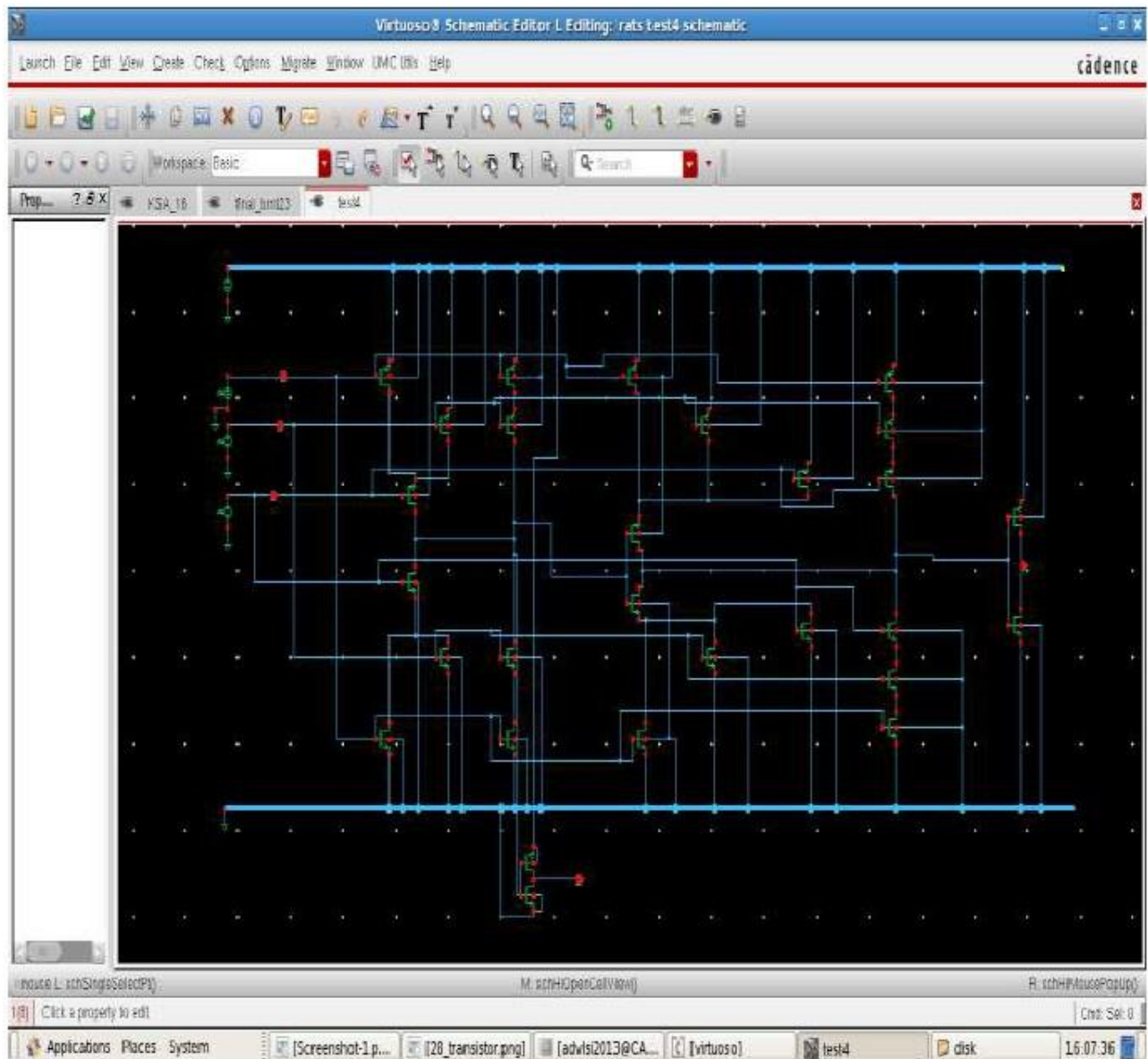



ASSIGNMENT 3: Adder Architectures VLSI ARCHITECTURES

Design a 4 bit ripple carry adder using CADENCE Virtuoso Schematic Editor and simulate it using Spectre simulator. Draw the layout using Virtuoso Layout Editor. Estimate the area, power dissipation and delay of the adder.

Below is the schematic diagram of the 28 transistor single bit full adder.




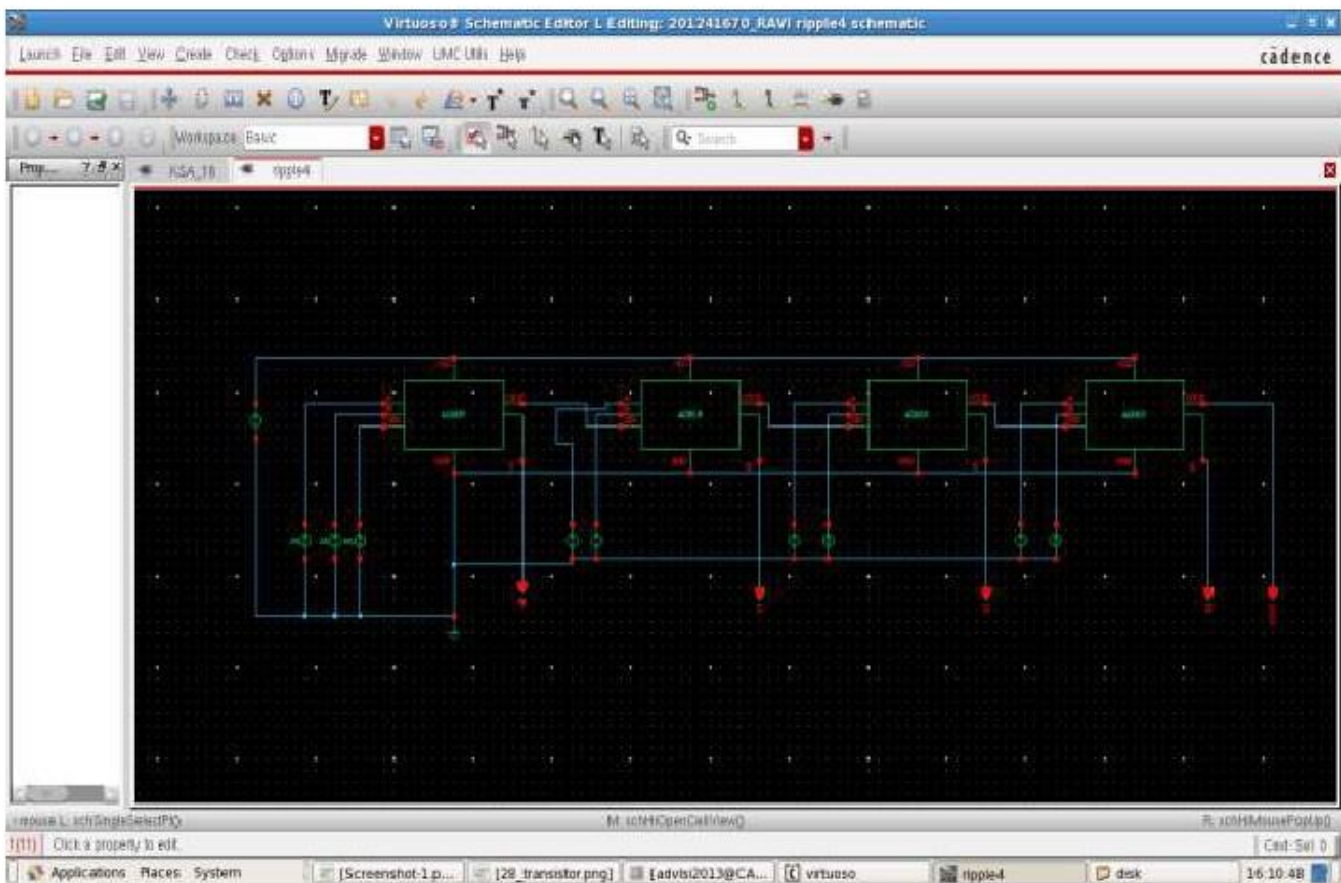The 4 bit ripple carry adder using this as a block is shown below:




The above is the ripple carry adder 4 bit output.
 Simulations of the 4 bit ripple carry adder:

 Simulation results:
 Power dissipation : 43 micro watts
 Delay – 450ps




Current simulation:

 


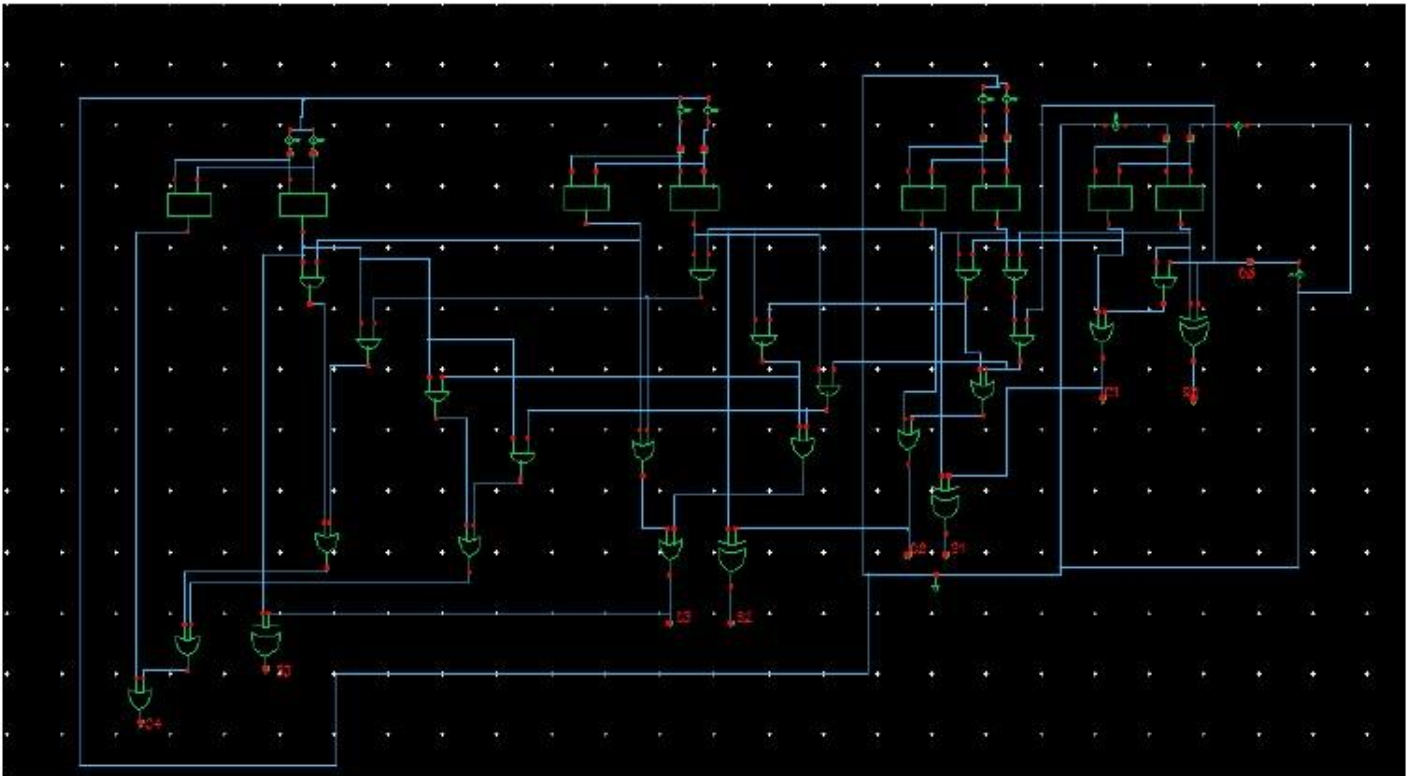Question2:Design a 4 bit carry look ahead adder using CADENCE Virtuoso Schematic Editor and simulate it using Spectre simulator. Draw the layout using Virtuoso Layout Editor. Estimate the area, power dissipation and delay of the adder.

Schematic of the carry look ahead adder:_____




16 BIT CLA:

 


Simulation outputs:

Transient Response

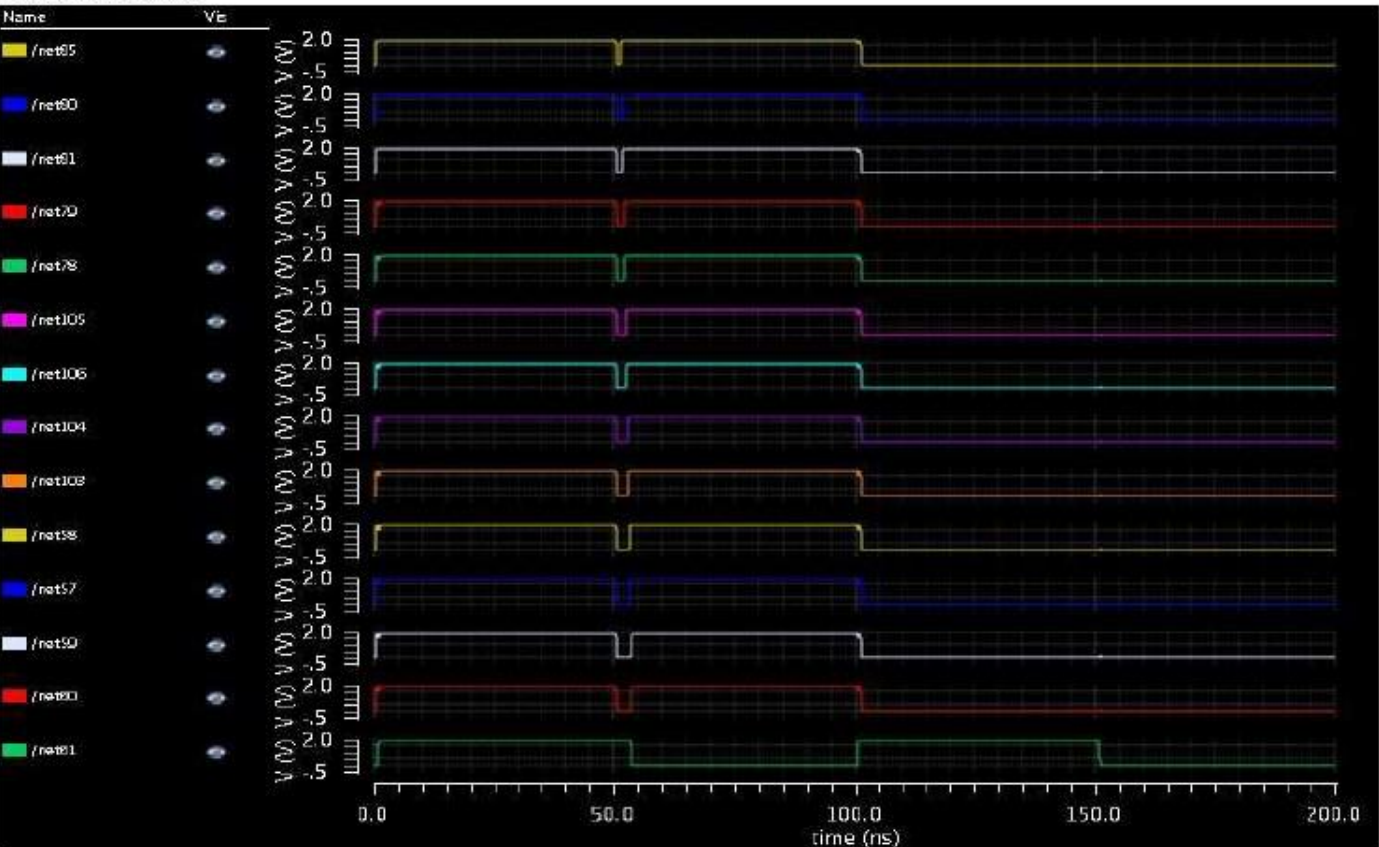


Current graph:

Transient Response

 


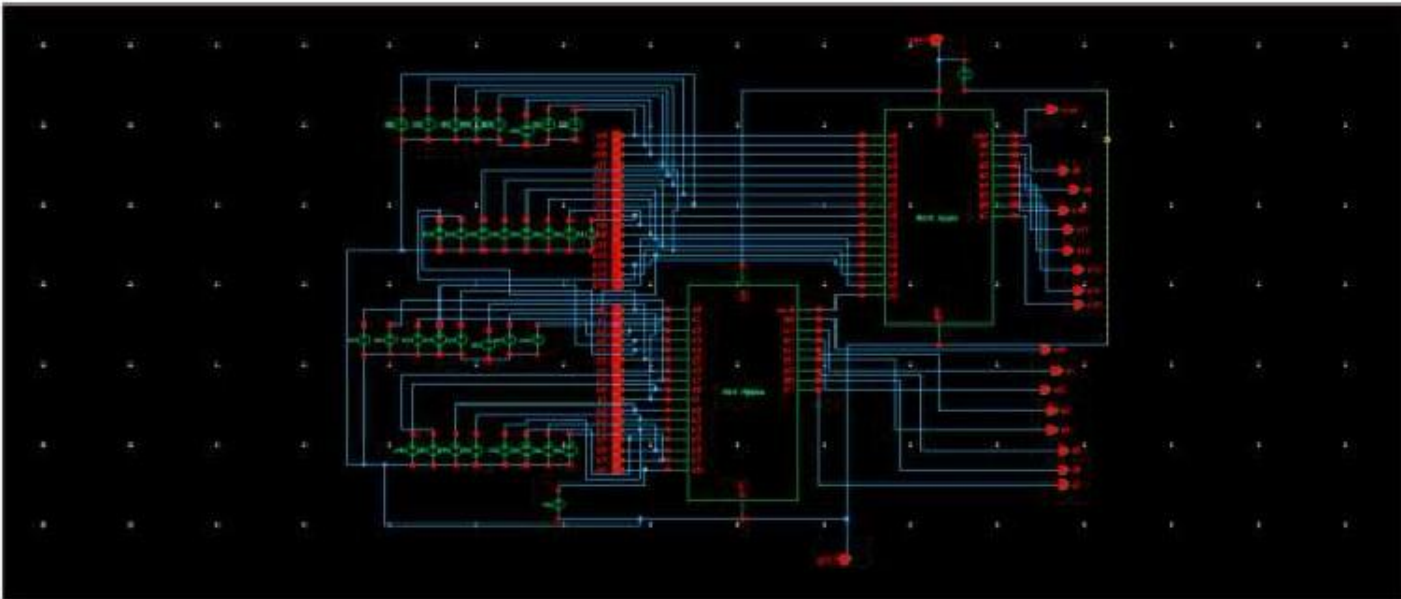3. In problems 1 and 2, redesign the circuits increasing the width of the adders from 4 bits to 16 bits in steps of 1 bit. Draw the layouts of the circuits and estimate the power dissipation, delay and area of the adders. Prepare a table for your comparison. What conclusions can you draw from the table?




16 bit ripple adder

Transient Response

 


current



Transient Response

 

Transient Response

 

SIMULATION OF DELAY:

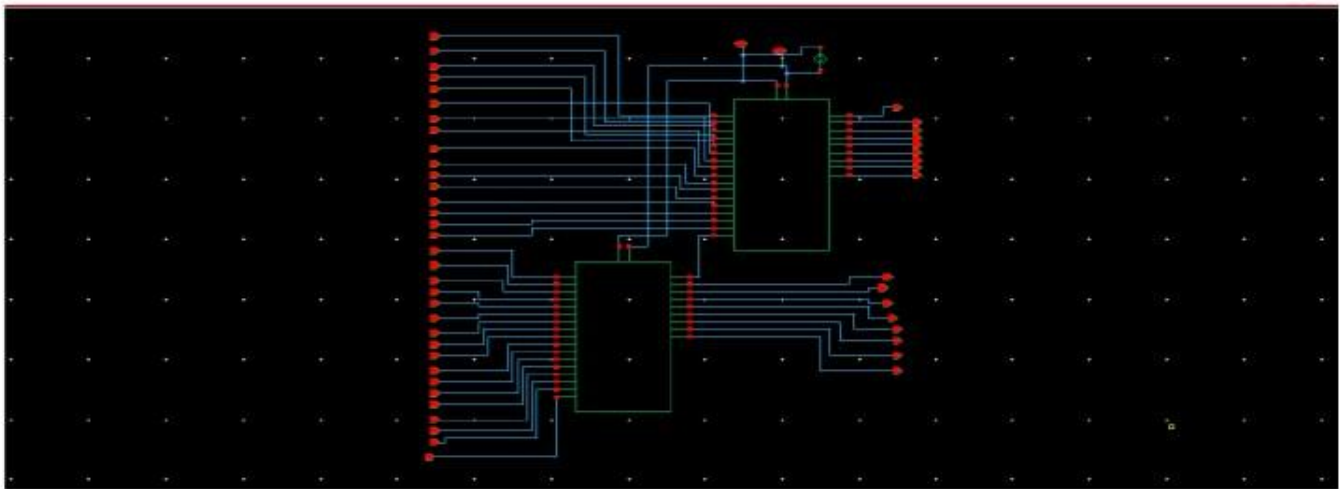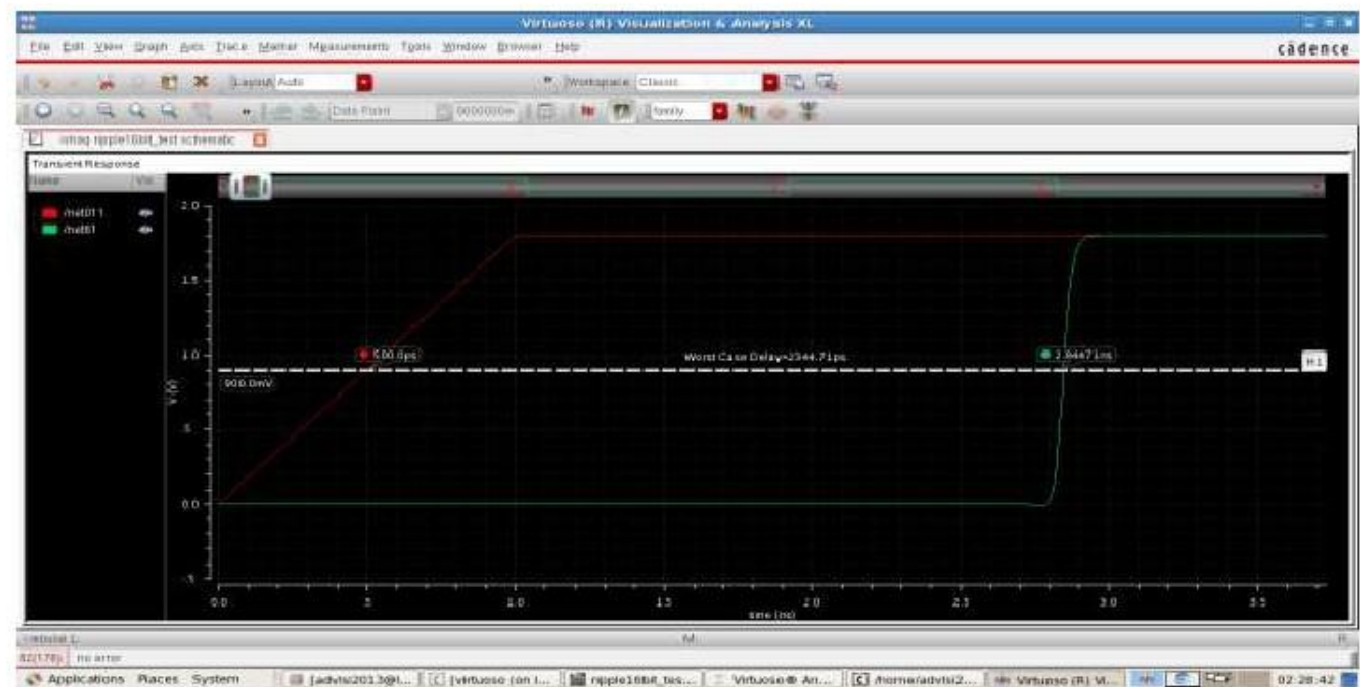


16 bit look ahead adder




DELAY SIMULATIONS

Transient Response

 

simulation


Transient Response

 


Current calc

Question 4: Design 16 bit Brent Kung and Kogge-Stone Adders. Draw the layouts of the three adders. Compare the area and performance parameters of these adders with the ripple carry and carry look ahead adders that you already designed. What conclusions can you draw from this?


Pg logic:

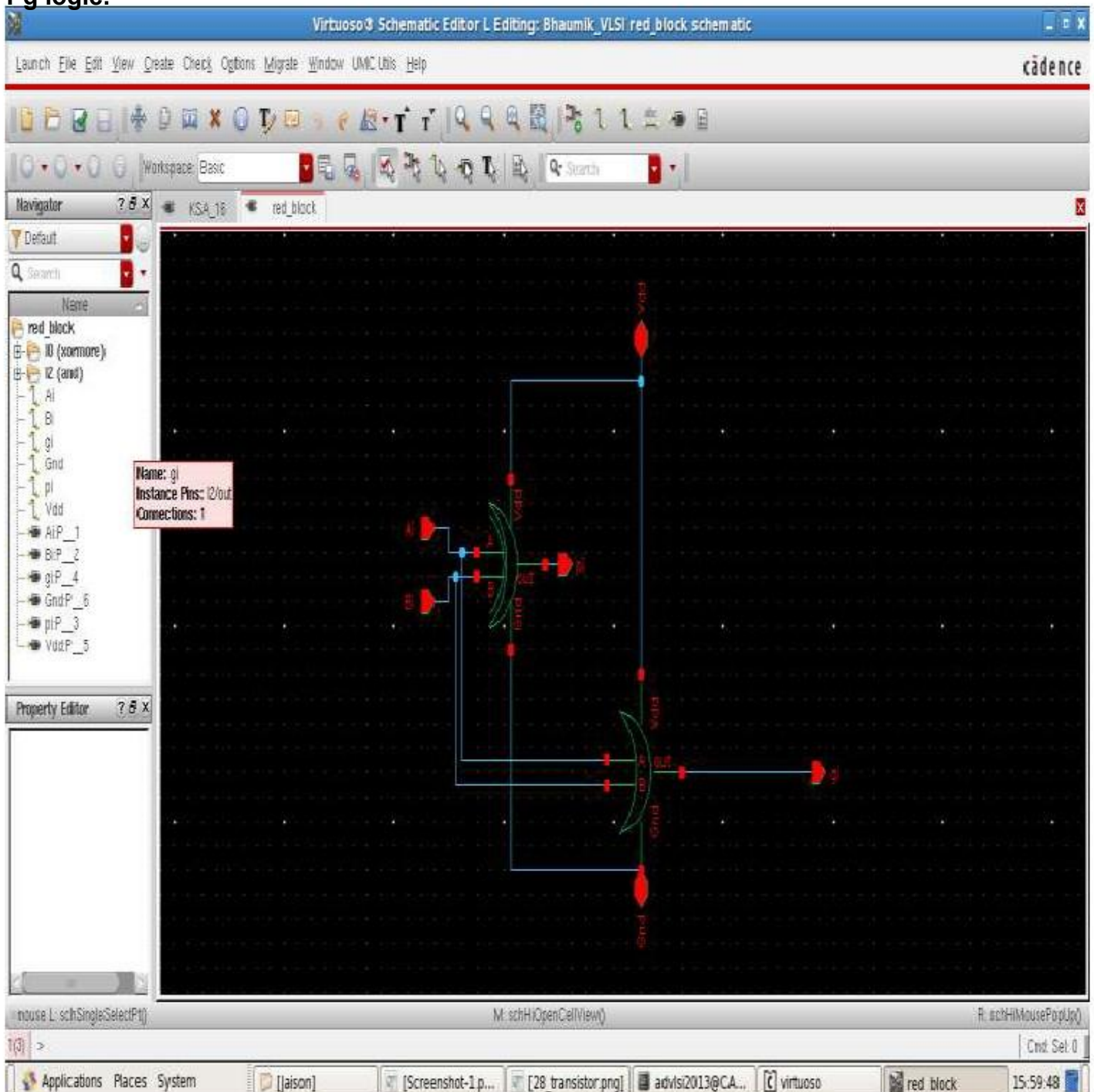


Gray cell:

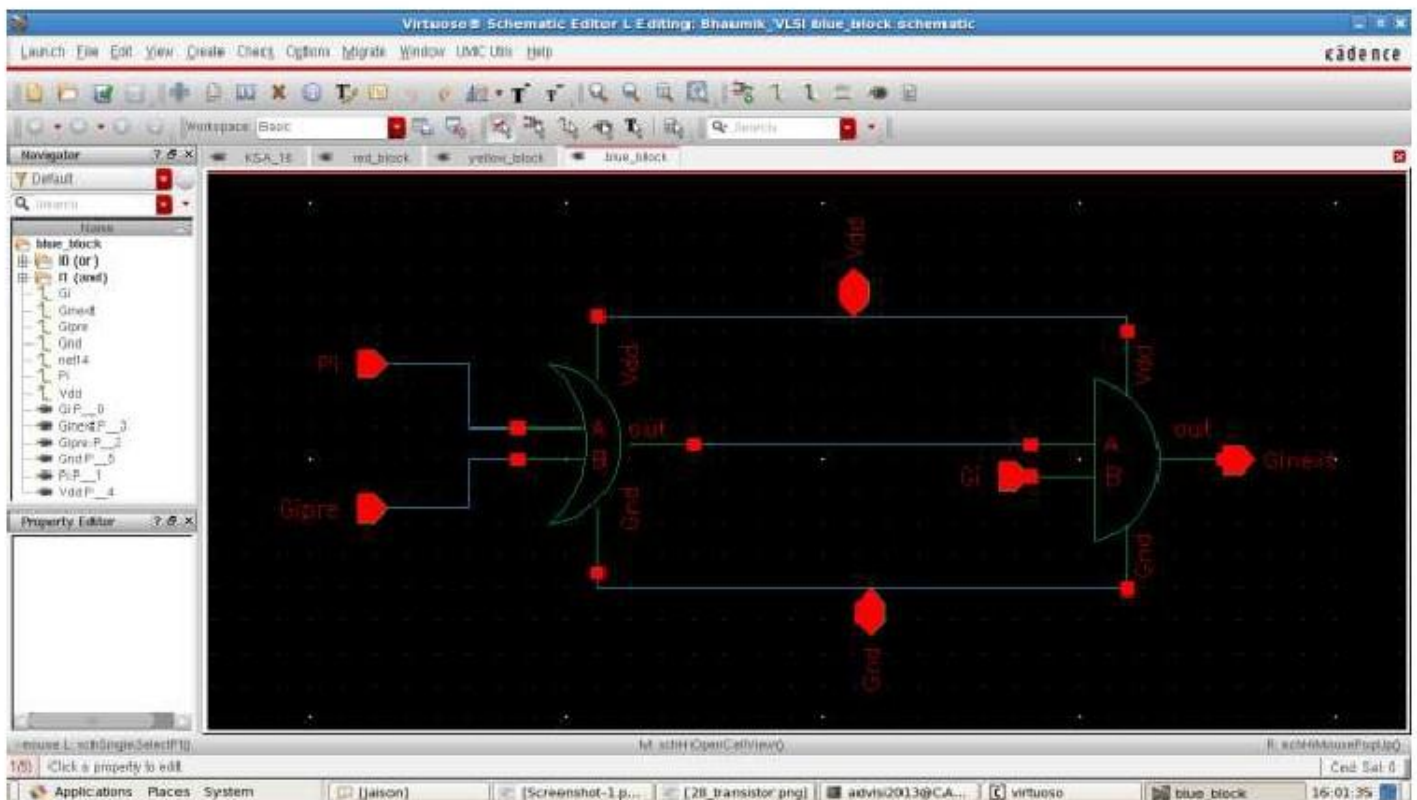


Black cell:

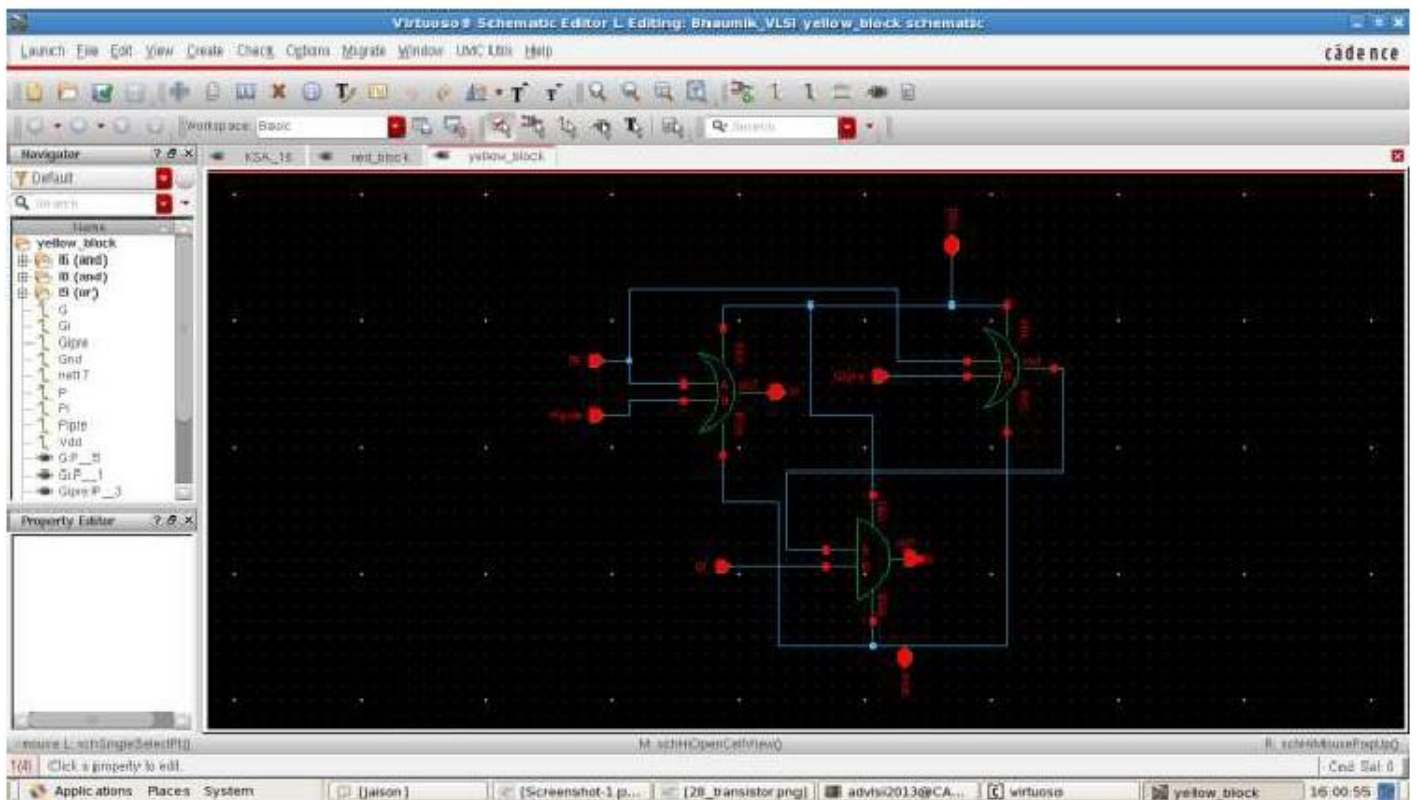


Kogge stone adder:

 


Simulation results:

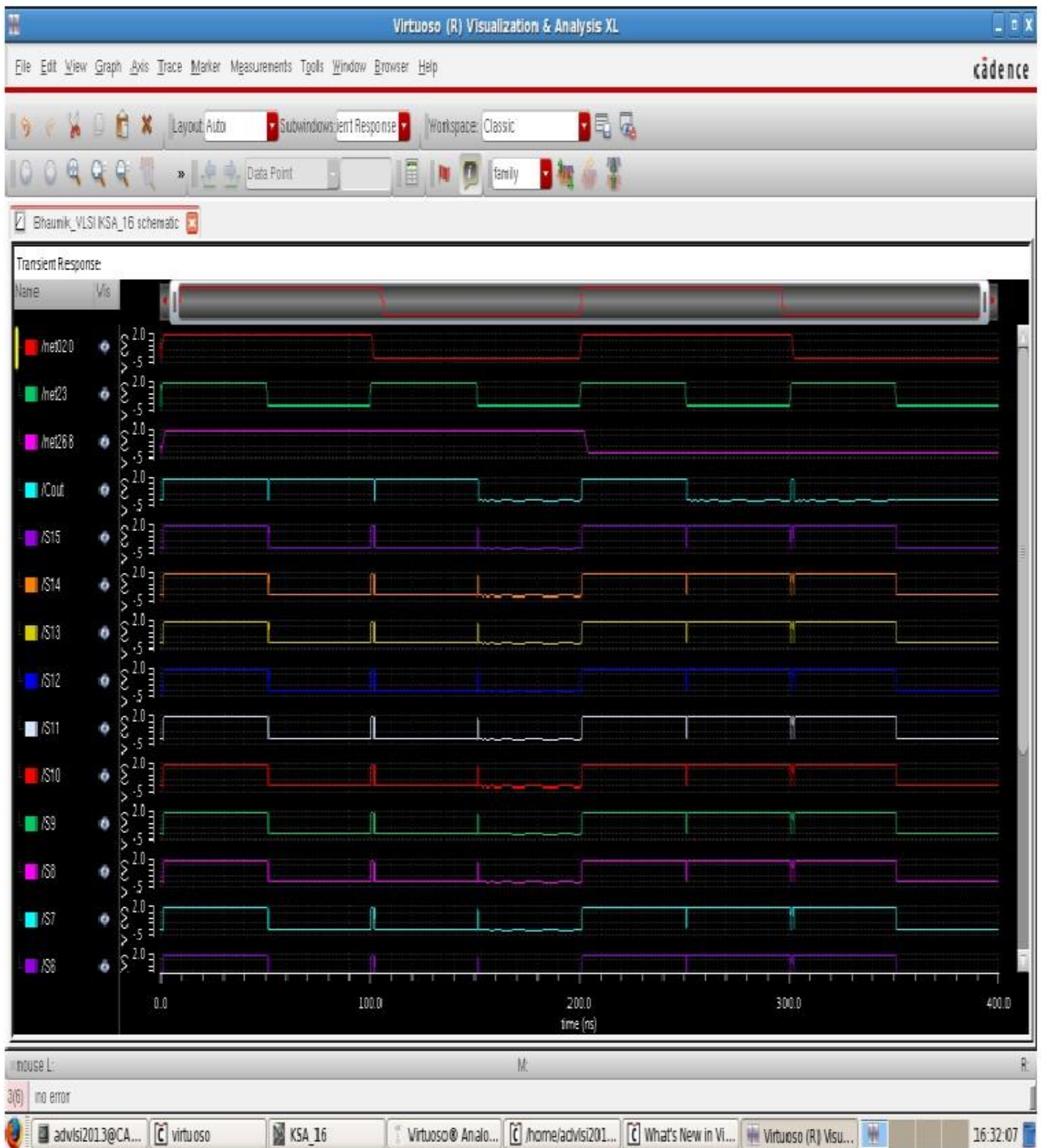


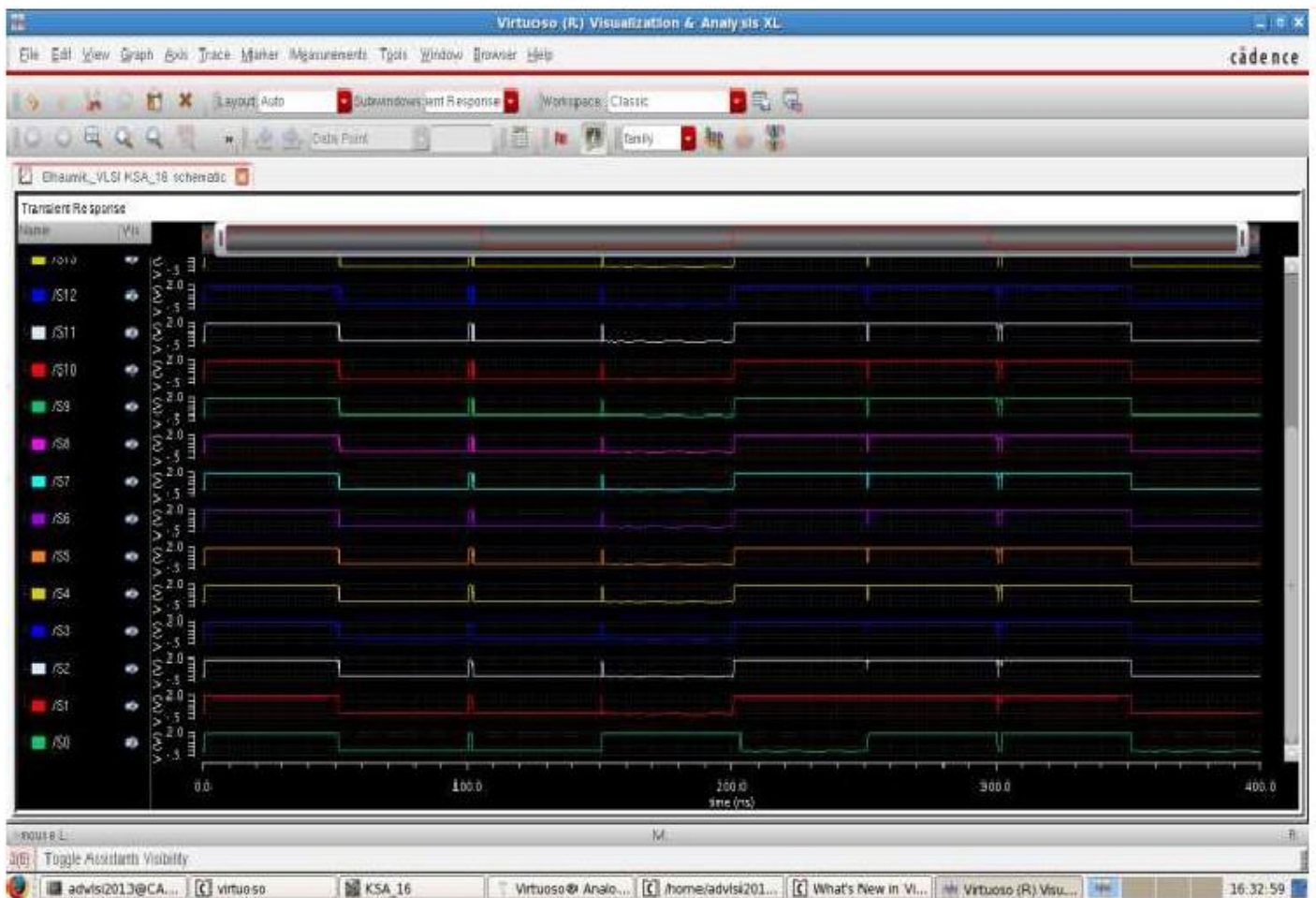


Current graph:

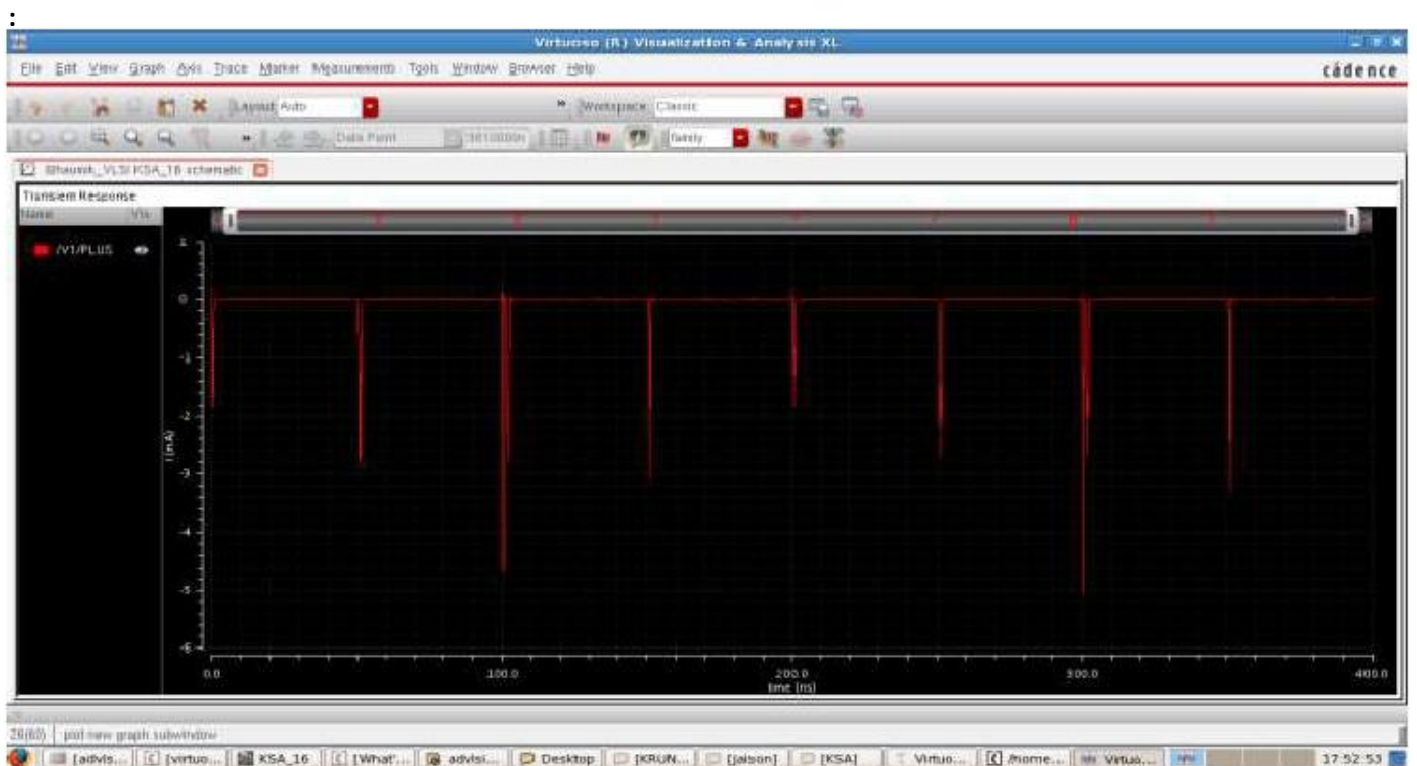

Brent kung:

 

SIMULATION OUTPUTS:

 

Delay calculation

Key: -20.45+1j


Function Panel

Special Functions


PI	compression	den	eyeDiagram	gainBWProc	inteq	overshoot	pov	riseTime	slewRate	unityGainFreq
act	compressionRf	dt	fallTime	gainMargin	inteq	peak	pmr	ms	spectralPower	value
abs_iter	convolve	dtb	tip	getAcclHave	interact	peak	pot	msNone	spectrum	xmax
average	cross	dtl	hysteresis	groupDelay	pn	peakToPeak	puttbb	not	spectrumWcs	xmin
bandwidth	d2a	isbCycle	freq	harmonic	ipnRf	period_iter	ptbdev	nhitt	tbody	xval
clip	d6n	evnQAM	freq_iter	harmonicFreq	loadpull	phaseMargin	ptbdev	sample	tangent	ymax
compare	delay	evnQpsk	frequency	hist	lsht	phaseNone	ptbdev	settingTime	thd	ymin

Current calculation

Transient Response

 

Transient Response

 

-	lavg(pA)	Power(uW)	Tphl(ns)	Tplh(ns)	Tp(ns)
LA4bit	27	48.6	0.380	0.423	0.401
LA8bit	44.5	80.1	0.251	0.295	0.272
LA16bit	135.4	243.7	0.38	0.288	0.268
RA4bit	808.7	1455.6	0.624	0.627	0.626
RA8bit	34.12	61.41	0.245	0.281	0.263
RA16bit	74.61	134.29	0.291	0.582	0.436
Brent Kung	7.78	35	0.523	0.577	0.55
KoggeStone	10.22	46	0.561	0.622	0.591