

GENERATING NOISY SIGNAL

Noisy signal can be generated from the desired signal through two simplest ways

1. Addition of noise to the desired signal


$$s(t) = x(t) + n(t);$$

2. Multiplication of noise with the desired signal

$$s(t) = x(t)n(t);$$

In this experiment we will try to mix the white noise that was generated previously.

Noise , $n(t)$ is

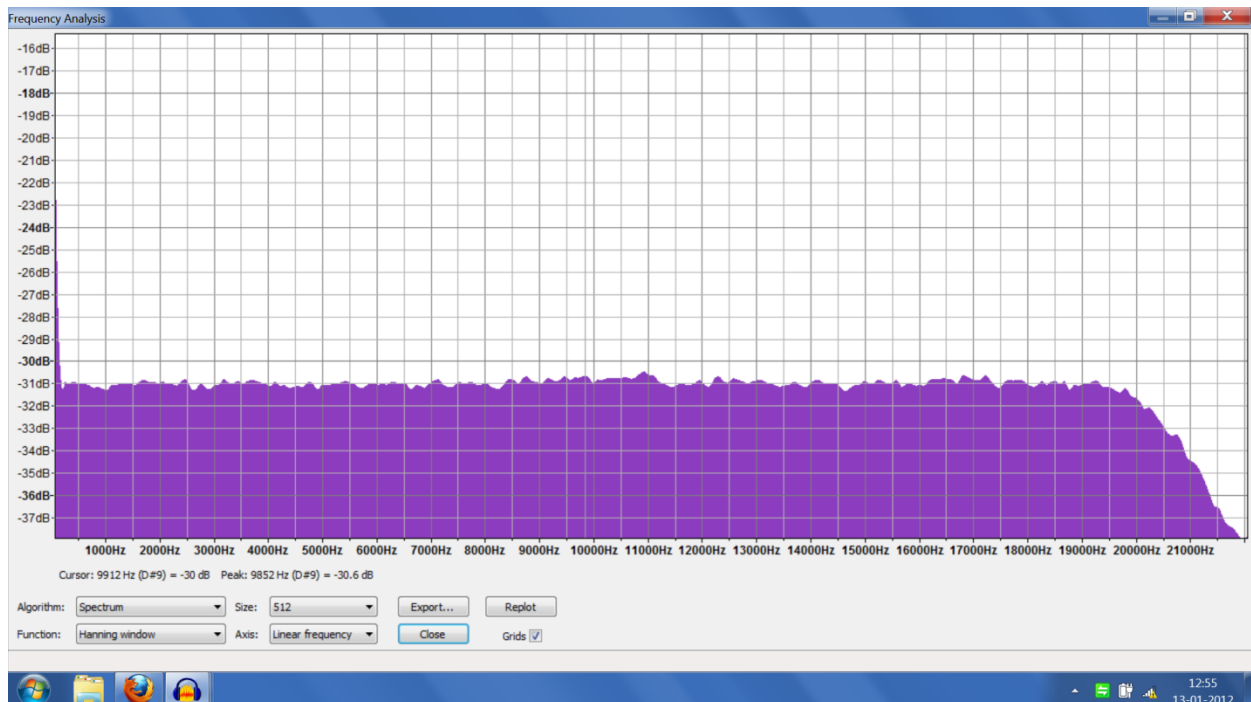


ADDITION :

Addition can be done by using the summer circuit which can be realised using op amp.


The output of the op amp is noise added signal.

When a single tone sine wave is added to the signal the peaks would be visible at frequency of sine wave indicating the addition, there would also be peaks at harmonics of sine wave.

Spectrum at frequency of sine wave 10Khz

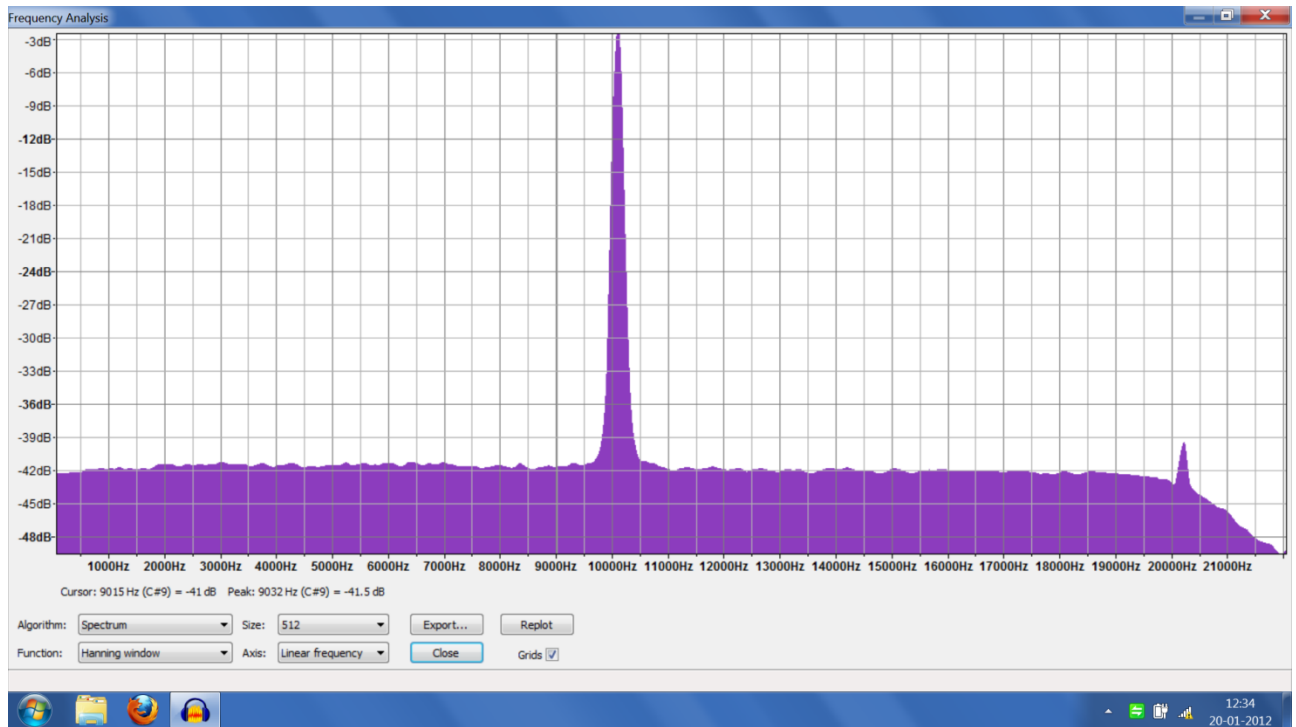


At 5Khz

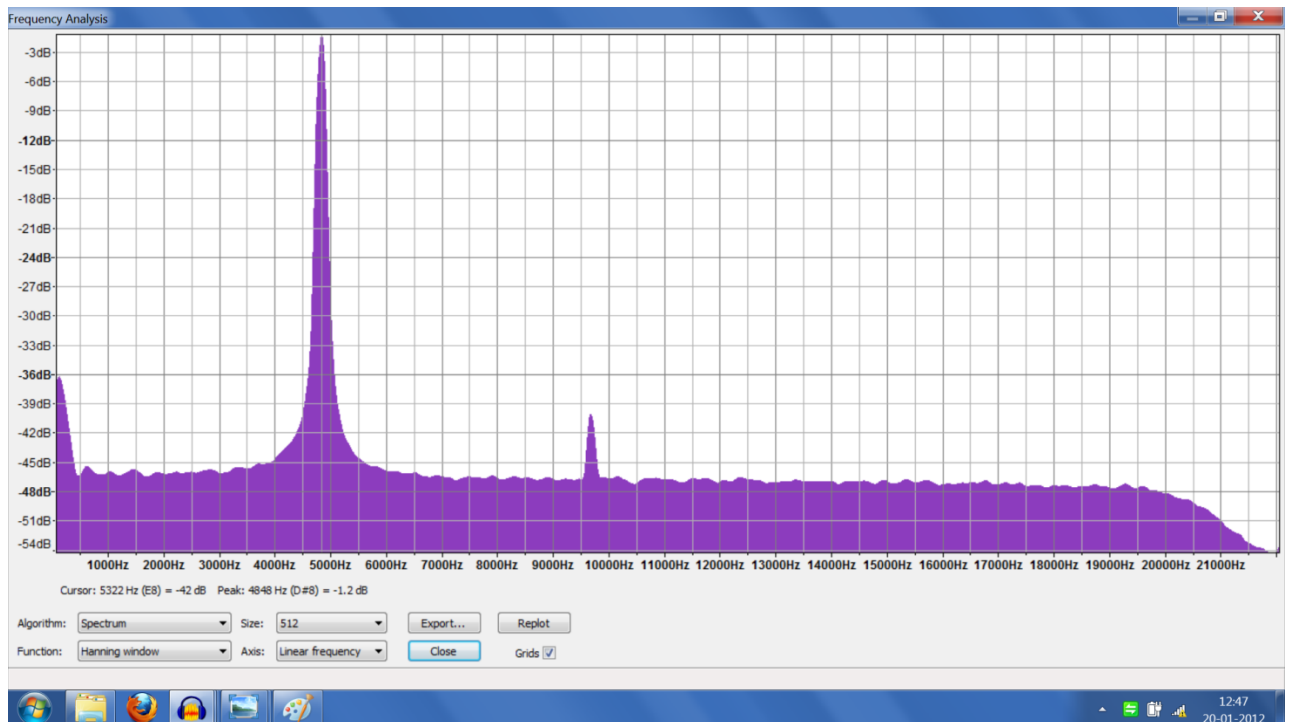

MULTIPLICATION (singletone) :

Multiplication of noise to signal can be realised using AD 633JN.


Noise multiplied signal :

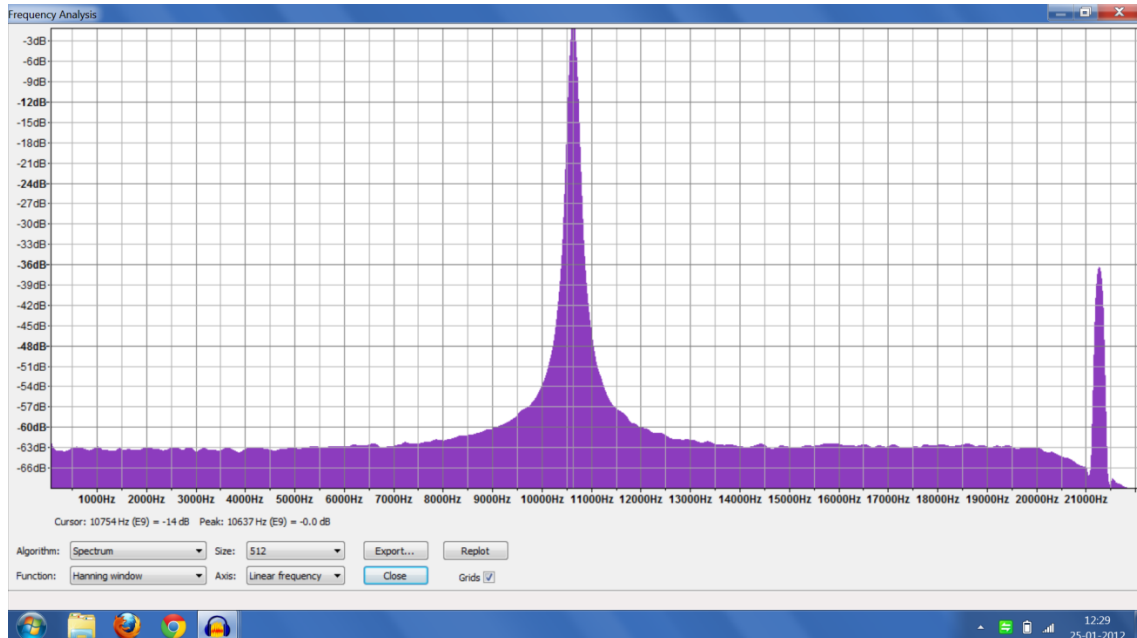


Addition and multiplication of baseband signal :

Triangular wave form of frequency 1khz is chosen for the following purpose and it passed through a lpf. We get the baseband signal.

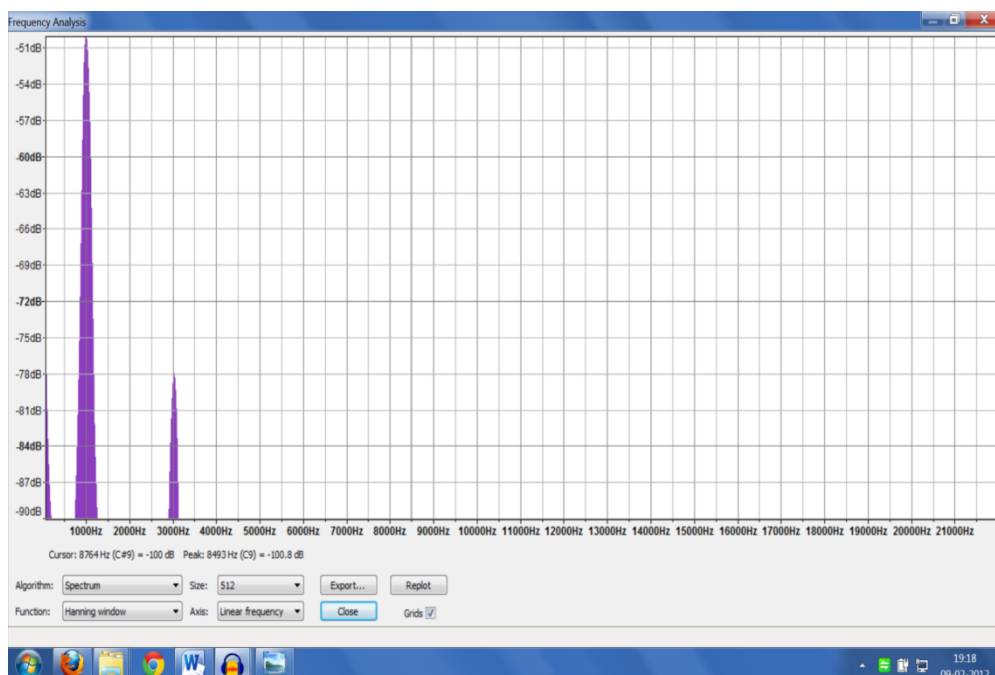Low pass filtered triangular wave's Spectrum :



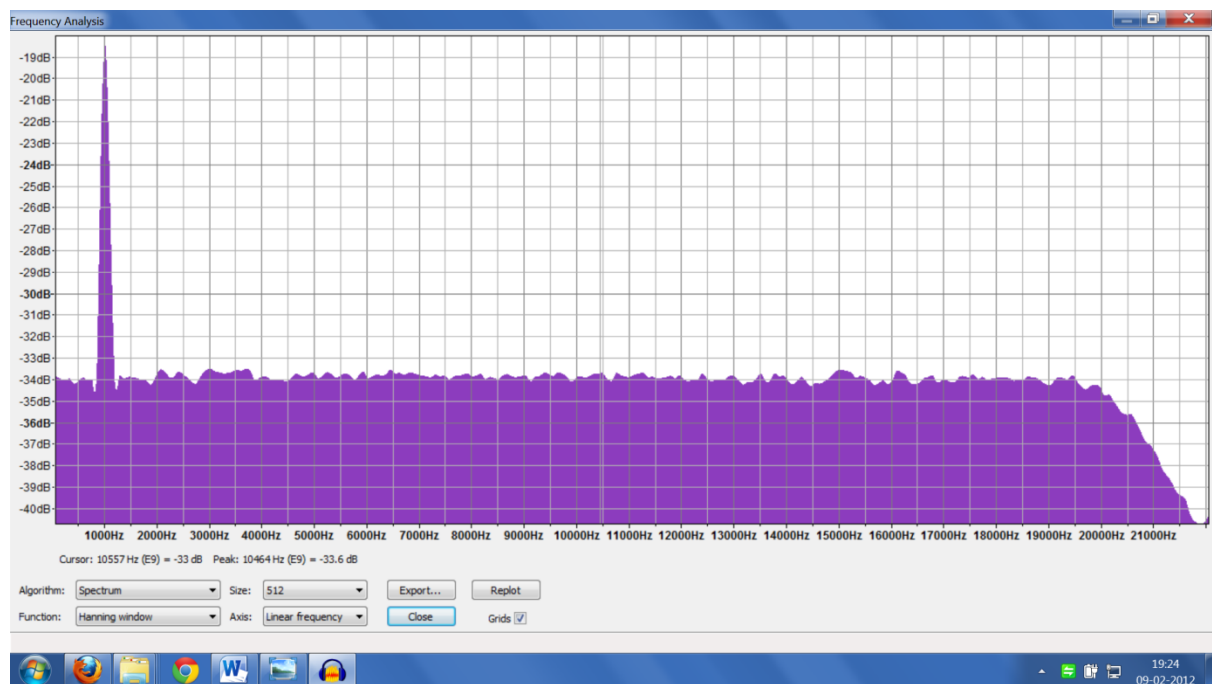Now when the noise is added to signal the spectrum is



Multiplication :

Our output of the multiplier was not as expected. As spectrum should be a flat band but we observed some peaks in spectrum which are not desired.