


Process Variations

Devices parameters vary between runs and even on the same die!

Variations in the process parameters, such as impurity concentration densities, oxide thicknesses, and diffusion depths. These are caused by non-uniform conditions during the deposition and/or the diffusion of the impurities. This introduces variations in the sheet resistances and transistor parameters such as the threshold voltage.

Variations in the dimensions of the devices, mainly resulting from the limited resolution of the photolithographic process. This causes (W/L) variations in MOS transistors and mismatches in the emitter areas of bipolar devices.

Velocity Saturation

 

$$v_n = -\mu_n \xi(x) = \mu_n \frac{dV}{dx}$$

scattering effects (collisions suffered by the carriers)

For p -type silicon, the critical field at which electron saturation occurs is $1.5 \text{ V}/\mu\text{m}$

saturation velocity v_{sat} approximately equals 10^5 m/s

$$v = \frac{\mu_n \xi}{1 + \xi/\xi_c} \quad \text{for } \xi \leq \xi_c$$






$$= v_{sat} \quad \text{for } \xi \geq \xi_c$$

drain current in the resistive region


$$I_D = \kappa(V_{DS})\mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2} \right]$$

For short-channel devices, κ is smaller than
   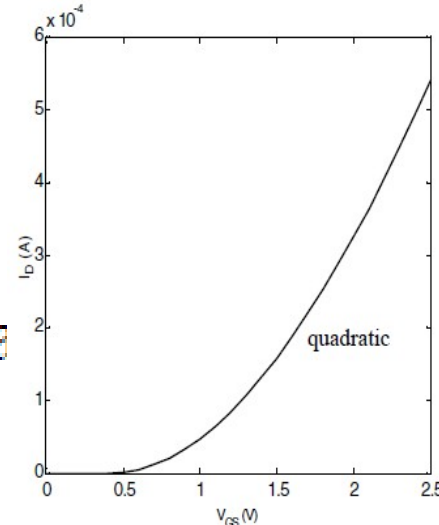 
$$\kappa(V) = \frac{1}{1 + (V/\xi_c L)}$$



Subthreshold Conduction

 

$$I_D = I_S e^{\frac{V_{GS}}{n k T / q}} \left(1 - e^{-\frac{V_{DS}}{k T / q}} \right)$$


measures by how much V_{GS} has to be reduced for the drain current to drop by a factor $S = n \left(\frac{kT}{q} \right) \ln(10)$

DIGITAL GATES


Fundamental Parameters

Noise in Digital Integrated Circuits

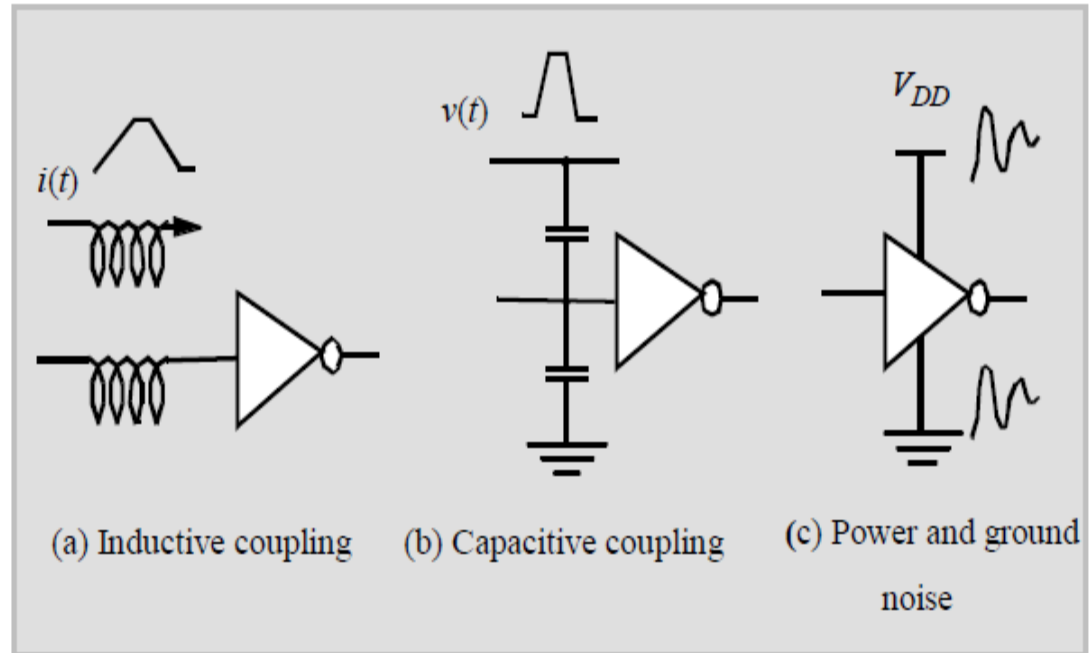
- Functionality
- Reliability, Robustness
- Area
- Performance
 - » Speed (delay)
 - » Power Consumption
 - » Energy



 DC Operation: Voltage Transfer Characteristic




 Mapping between analog and digital signals




$$NM_L = V_{IL} - V_{OL}$$

$$NM_H = V_{OH} - V_{IH}$$

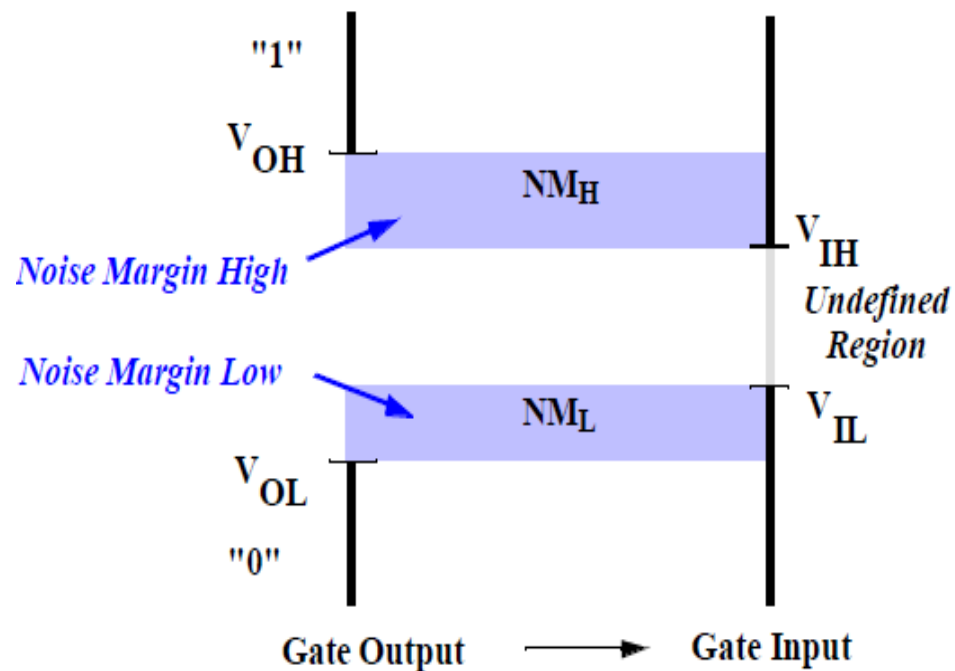


Definition of Noise Margins


The Regenerative Property

 


(a) A chain of inverters.

 


(b) Regenerative gate

 


(c) Non-regenerative gate

 

(a) Fan-out N

 

(b) Fan-in M

 


Noise Immunity

- proportional to the signal swing V_{sw} . The impact on the signal node is expressed as $g V_{sw}$.
- fixed. The impact on the signal node equals $f V_{nf}$, with V_{nf} the amplitude of the noise source, and f the transfer function from noise to signal node.

$$V_{NM} = \frac{V_{sw}}{2} \geq \sum_i f_i V_{Nfi} + \sum_j g_j V_{sw}$$

$$V_{sw} \geq \frac{2 \sum_i f_i V_{Nfi}}{1 - 2 \sum_j g_j}$$


The Ideal Gate

 

$$R_i = \infty$$

$$R_o = 0$$

VTC of Real Inverter

 


$$V_{OH} = 3.5 \text{ V}; \quad V_{OL} = 0.45 \text{ V}$$

$$V_{IH} = 2.35 \text{ V}; \quad V_{IL} = 0.66 \text{ V}$$



$$V_M = 1.64 \text{ V}$$

$$NM_H = 1.15 \text{ V}; \quad NM_L = 0.21 \text{ V}$$

Delay Definitions

 

Ring Oscillator

  

$$T = 2 \times t_p \times N$$

$$2Nt_p \gg t_f + t_r$$

Power Dissipation

$$P_{peak} = i_{peak} V_{supply} = \max(p(t))$$


$$P_{av} = \frac{1}{T} \int_0^T p(t) dt = \frac{V_{supply}}{T} \int_0^T i_{supply}(t) dt$$

Power-Delay Product



$$PDP = t_p \times P_{av}$$

= Energy dissipated per operation

The CMOS Inverter

 

CMOS Inverters

  


Switch Model of CMOS Transistor

Some points to note

- The high and low output levels equal V_{DD} and GND , respectively; in other words, the voltage swing is equal to the supply voltage. This results in high noise margins.
- The logic levels are not dependent upon the relative device sizes, so that the transistors can be minimum size. Gates with this property are called *ratioless*. This is in contrast with *ratioed logic*, where logic levels are determined by the relative dimensions of the composing transistors.
- In steady state, there always exists a path with finite resistance between the output and either V_{DD} or GND . A well-designed CMOS inverter, therefore, has a *low output impedance*, which makes it less sensitive to noise and disturbances. Typical values of the output resistance are in $k\Omega$ range.
- The *input resistance* of the CMOS inverter is extremely high, as the gate of an MOS transistor is a virtually perfect insulator and draws no dc input current. Since the input node of the inverter only connects to transistor gates, the steady-state input current is nearly zero. A single inverter can theoretically drive an infinite number of gates (or have an infinite fan-out) and still be functionally operational; however, increasing the fan-out also increases the propagation delay, as will become clear below. So, although fan-out does not have any effect on the steady-state behavior, it degrades the transient response.

CMOS Inverter: Steady State Response

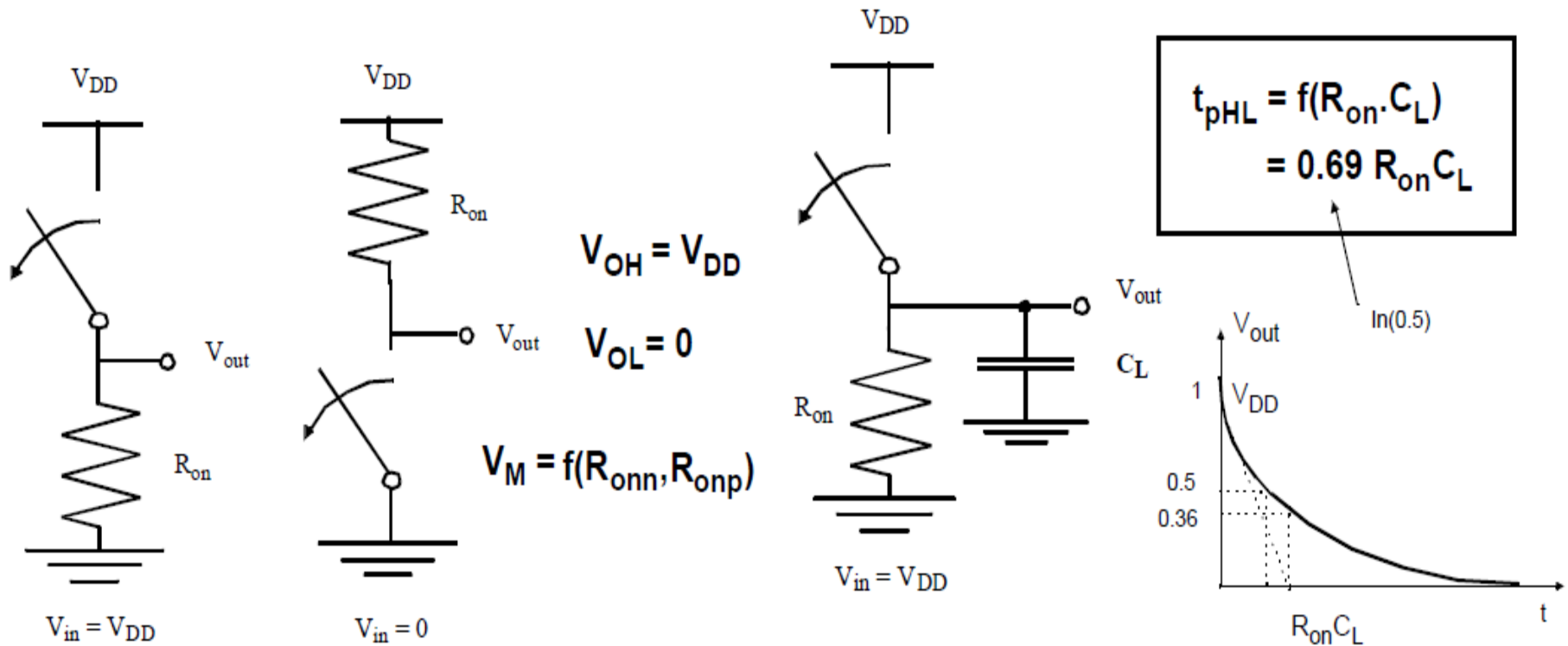


CMOS Inverter: Transient Response


CMOS Properties

- Full rail-to-rail swing
- Symmetrical VTC
- Propagation delay function of load capacitance and resistance of transistors
- No static power dissipation
- Direct path current during switching


PMOS Load Lines

 

CMOS Inverter Load Characteristics

 

CMOS Inverter VTC

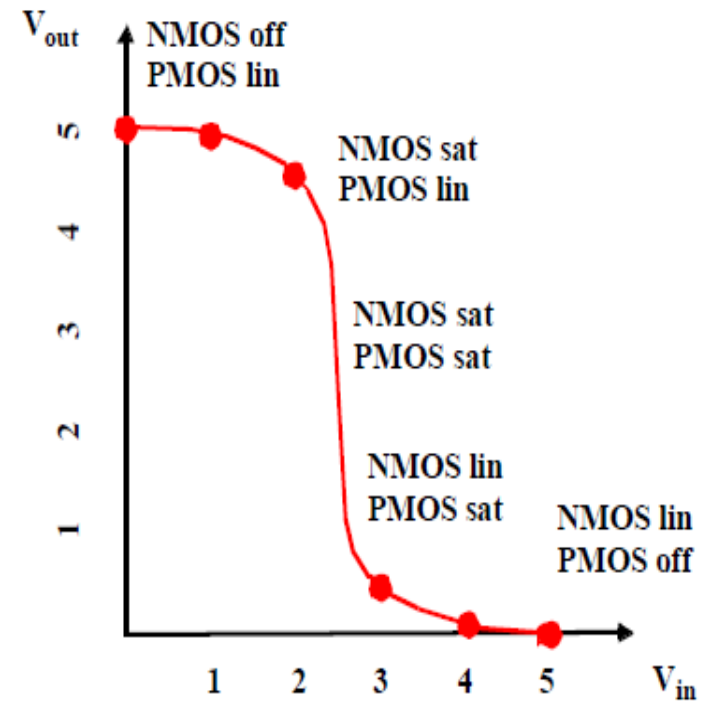

CMOS Inverter: The Static Behavior

The switching threshold, V_M , is defined as the point where $V_{in} = V_{out}$.


$$k_n V_{DSATn} \left(V_M - V_{Tn} - \frac{V_{DSATn}}{2} \right) + k_p V_{DSATp} \left(V_M - V_{DD} - V_{Tp} - \frac{V_{DSATp}}{2} \right) = 0$$

$$V_M = \frac{\left(V_{Tn} + \frac{V_{DSATn}}{2} \right) + r \left(V_{DD} + V_{Tp} + \frac{V_{DSATp}}{2} \right)}{1 + r} \quad \text{with } r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}} = \frac{\mu_{satp} W_p}{\mu_{satn} W_n}$$




$$V_M \approx \frac{r V_{DD}}{1 + r}$$

$$(W/L)_p = (W/L)_n \times (V_{DSATn} k'_n) / (V_{DSATp} k'_p)$$

 
$$\frac{(W/L)_p}{(W/L)_n} = \frac{k'_n V_{DSATn} (V_M - V_{Tn} - V_{DSATn}/2)}{k'_p V_{DSATp} (V_{DD} - V_M + V_{Tp} + V_{DSATp}/2)}$$



   Changing the inverter threshold can improve the circuit reliability



(a) Response of standard inverter

 


(b) Response of inverter with modified threshold


V_M is relatively insensitive to variations in the device ratio

The effect of changing the W_p/W_n ratio is to shift the transient region of the VTC

Simulated VTC

 


Gate Switching Threshold

 

$$V_M = \frac{r(V_{DD} - |V_{Tp}|) + V_{Tn}}{1 + r} \quad \text{with} \quad r = \sqrt{\frac{k_p}{k_n}}$$

Noise Margins

 V_{IH} and V_{IL} are the operational points of the inverter where $\frac{dV_{out}}{dV_{in}} = -1$



$$V_{IH} - V_{IL} = -\frac{(V_{OH} - V_{OL})}{g} = \frac{-V_{DD}}{g}$$

$$V_{IH} = V_M - \frac{V_M}{g} \quad V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$

$$NM_H = V_{DD} - V_{IH} \quad NM_L = V_{IL}$$



$$k_n V_{DSATn} \left(V_{in} - V_{Tn} - \frac{V_{DSATn}}{2} \right) (1 + \lambda_n V_{out}) +$$

$$k_p V_{DSATp} \left(V_{in} - V_{DD} - V_{Tp} - \frac{V_{DSATp}}{2} \right) (1 + \lambda_p V_{out} - \lambda_p V_{DD}) = 0$$

$$\frac{dV_{out}}{dV_{in}} = -\frac{k_n V_{DSATn} (1 + \lambda_n V_{out}) + k_p V_{DSATp} (1 + \lambda_p V_{out} - \lambda_p V_{DD})}{\lambda_n k_n V_{DSATn} (V_{in} - V_{Tn} - V_{DSATn}/2) + \lambda_p k_p V_{DSATp} (V_{in} - V_{DD} - V_{Tp} - V_{DSATp}/2)}$$

$$g = -\frac{1}{I_D(V_M)} \frac{k_n V_{DSATn} + k_p V_{DSATp}}{\lambda_n - \lambda_p}$$
  
$$\approx \frac{1 + r}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)}$$




Assume an inverter in the generic 0.25 μm CMOS technology designed with a PMOS/NMOS ratio of 3.4 and with the NMOS transistor minimum size ($W = 0.375 \mu\text{m}$, $L = 0.25 \mu\text{m}$, $W/L = 1.5$). We first compute the gain at $V_M (= 1.25 \text{ V})$,

$$I_D(V_M) = 1.5 \times 115 \times 10^{-6} \times 0.63 \times (1.25 - 0.43 - 0.63/2) \times (1 + 0.06 \times 1.25) = 59 \times 10^{-6} \text{ A}$$


$$g = -\frac{1}{59 \times 10^{-6}} \frac{1.5 \times 115 \times 10^{-6} \times 0.63 + 1.5 \times 3.4 \times 30 \times 10^{-6} \times 1.0}{0.06 + 0.1} = -27.5$$

This yields the following values for V_{IL} , V_{IH} , NM_L , NM_H :
 
$$V_{IL} = 1.2 \text{ V}, V_{IH} = 1.3 \text{ V}, NM_L = NM_H = 1.2.$$




 Impact of device variations on static CMOS inverter VTC. The “good” device has a smaller oxide thickness (- 3nm), a smaller length (-25 nm), a higher width (+30 nm), and a smaller threshold (-60 mV). The opposite is true for the “bad” transistor.




but it deteriorates for very-low supply voltages

$$V_{DDmin} > 2 \dots 4 \frac{kT}{q}$$

 


MOS Transistor Small Signal Model

 

At V_{IH} (V_{IL}): $\frac{\partial V_{out}}{\partial V_{in}} = -1$



small-signal model of inverter

 

$$g = \frac{v_{out}}{v_{in}} = -(g_{mn} + g_{mp}) \times (r_{on} \parallel r_{op}) = -1$$

Determining V_{IH} and V_{IL}


CMOS Inverter: Transient Response

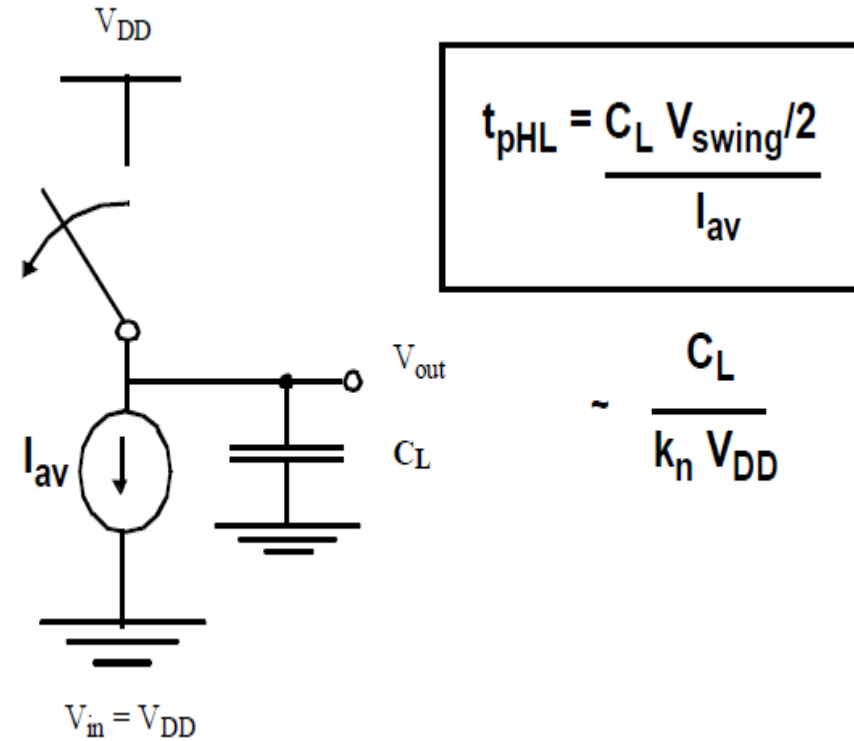 




CMOS Inverter Propagation Delay

Computing the Capacitances

The Miller Effect

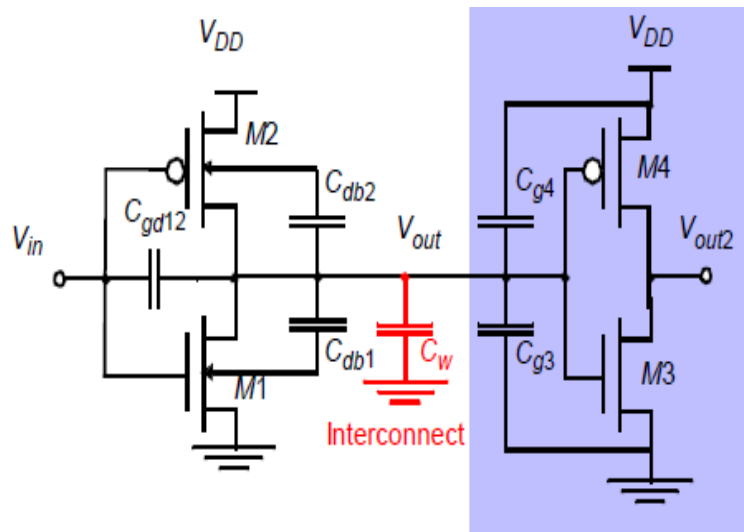


Simplified Model

   

"A capacitor experiencing identical but opposite voltage swings at both its terminals can be replaced by a capacitor to ground, whose value is two times the original value."

Computing the Capacitances


Capacitor	Expression
C_{gd1}	$2 \text{ CGD0 } W_n$
C_{gd2}	$2 \text{ CGD0 } W_p$
C_{db1}	$K_{eqn} (AD_n \text{ CJ} + PD_n \text{ CJSW})$
C_{db2}	$K_{eqp} (AD_p \text{ CJ} + PD_p \text{ CJSW})$
C_{g3}	$C_{ox} W_n L_n$
C_{g4}	$C_{ox} W_p L_p$
C_w	From Extraction
C_L	Σ

 

$$t_{pHL} = \sqrt{t_{pHL(step)}^2 + (t_r/2)^2}$$

Impact of Rise Time on Delay

 Delay as a function of V_{DD} Where Does Power Go in CMOS?



- **Dynamic Power Consumption**

Charging and Discharging Capacitors


- **Short Circuit Currents**

Short Circuit Path between Supply Rails during Switching

- **Leakage**

Leaking diodes and transistors

Dynamic Power Dissipation

 

$$\text{Energy/transition} = \frac{1}{2} C_L V_{dd}^2$$

$$\text{Power} = \text{Energy/transition} \times f = \frac{1}{2} C_L V_{dd}^2 f$$

Not a function of transistor sizes!
Need to reduce C_L , V_{dd} and f to reduce power.

Adobe FrameMaker

D:\Books\SLIDES\slides2

Technology Evolution


Year of Introduction	1994	1997	2000	2003	2006	2009
Channel length (μm)	0.4	0.3	0.25	0.18	0.13	0.1
Gate oxide (nm)	12	7	6	4.5	4	4
V_{DD} (V)	3.3	2.2	2.2	1.5	1.5	1.5
V_T (V)	0.7	0.7	0.7	0.6	0.6	0.6
NMOS I_{Dsat} (mA/ μm) (@ $V_{GS} = V_{DD}$)	0.35	0.27	0.31	0.21	0.29	0.33
PMOS I_{Dsat} (mA/ μm) (@ $V_{GS} = V_{DD}$)	0.16	0.11	0.14	0.09	0.13	0.16

Devices

Digital Integrated Circuits



© Prentice-Hall 1995

43 of 66

 

Propagation Delay Scaling

Number of components per chip

  

Technology Scaling Models

- **Full Scaling (Constant Electrical Field)**

ideal model — dimensions and voltage scale together by the same factor S


- **Fixed Voltage Scaling**

most common model until recently —
only dimensions scale, voltages remain constant

- **General Scaling**

most realistic for today's situation —
voltages and dimensions scale with different factors

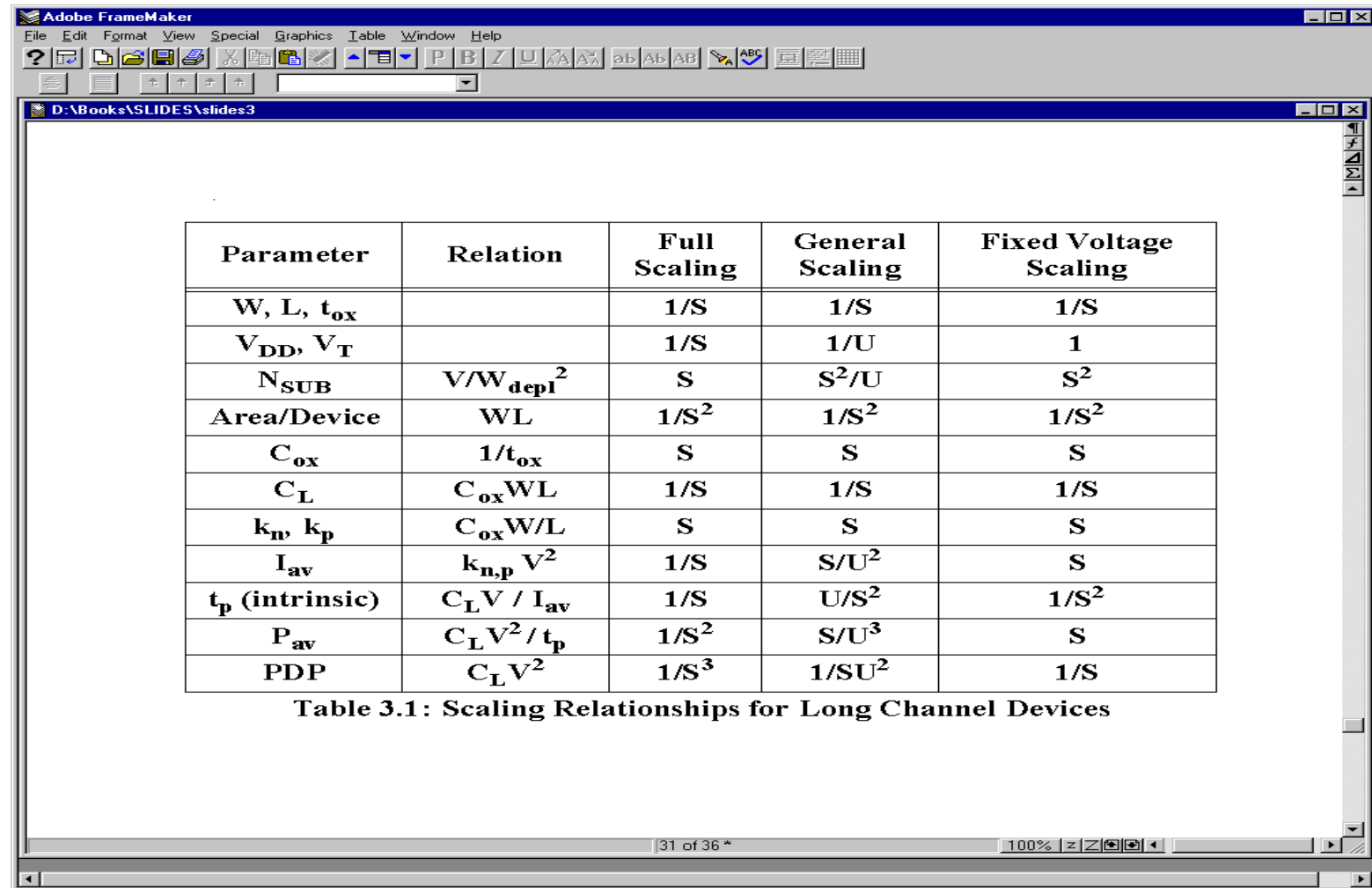Scaling Relationships for Long Channel Devices



The screenshot shows the Adobe FrameMaker application window. The title bar reads "Adobe FrameMaker". The menu bar includes "File", "Edit", "Format", "View", "Special", "Graphics", "Table", "Window", and "Help". The toolbar contains various icons for file operations, editing, and formatting. The main content area displays a table with the following data:

Parameter	Relation	Full Scaling	General Scaling	Fixed Voltage Scaling
W, L, t_{ox}		$1/S$	$1/S$	$1/S$
V_{DD}, V_T		$1/S$	$1/U$	1
N_{SUB}	V/W_{depl}^2	S	S^2/U	S^2
Area/Device	WL	$1/S^2$	$1/S^2$	$1/S^2$
C_{ox}	$1/t_{ox}$	S	S	S
C_L	$C_{ox}WL$	$1/S$	$1/S$	$1/S$
k_n, k_p	$C_{ox}W/L$	S	S	S
I_{av}	$k_{n,p} V^2$	$1/S$	S/U^2	S
t_p (intrinsic)	$C_L V / I_{av}$	$1/S$	U/S^2	$1/S^2$
P_{av}	$C_L V^2 / t_p$	$1/S^2$	S/U^3	S
PDP	$C_L V^2$	$1/S^3$	$1/SU^2$	$1/S$

Table 3.1: Scaling Relationships for Long Channel Devices

The status bar at the bottom of the window shows "31 of 36" and "100%".

Scaling of Short Channel Devices

Adobe FrameMaker

File Edit Format View Special Graphics Table Window Help

D:\Books\SLIDES\slides3

Scaling of Short Channel Devices

Parameter	Relation	Full Scaling	General Scaling	Fixed Voltage Scaling
I_{av}	$C_{ox}WV$	$1/S$	$1/U$	1
J_{av}	I_{av}/Area	S	S^2/U	S^2
t_p (intrinsic)	$C_L V / I_{av}$	$1/S$	$1/S$	$1/S$
P_{av}	$C_L V^2 / t_p$	$1/S^2$	$1/U^2$	1

32 of 36 100%