

Adder Architectures

Dr. Shubhajit Roy Chowdhury,

Centre for VLSI and Embedded Systems Technology,

IIIT Hyderabad, India

Email: src.vlsi@iiit.ac.in



Dr. Shubhajit Roy Chowdhury



CVEST, IIIT HYDERABAD

Outline

- Single bit addition
- Carry ripple adder
- Carry skip adder
- Carry look ahead adder
- Carry select adder
- Carry increment adder
- Tree adder
- Higher valency trees



Single bit addition

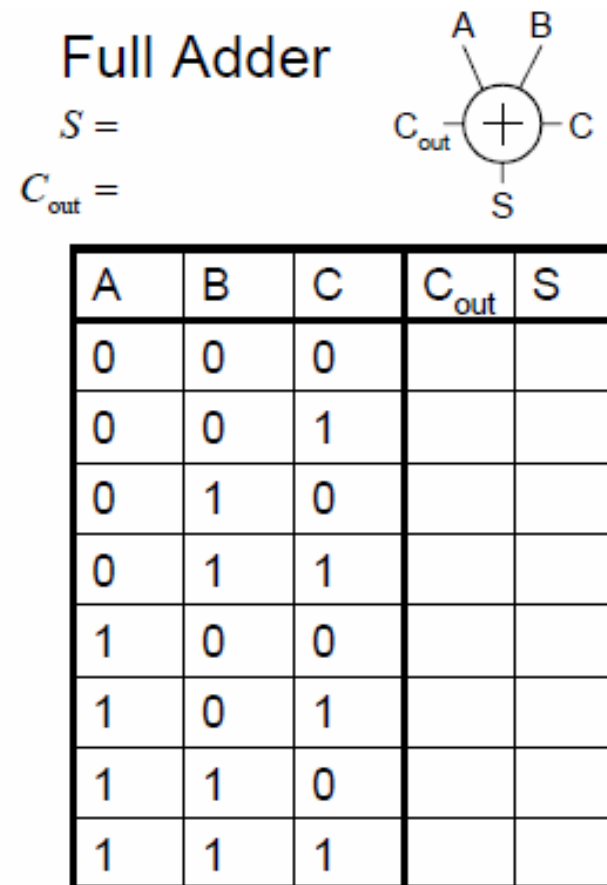 


Full Adder Design I

- ❑ Brute force implementation from eqns


$$S = A \oplus B \oplus C$$

$$C_{\text{out}} = \text{MAJ}(A, B, C)$$

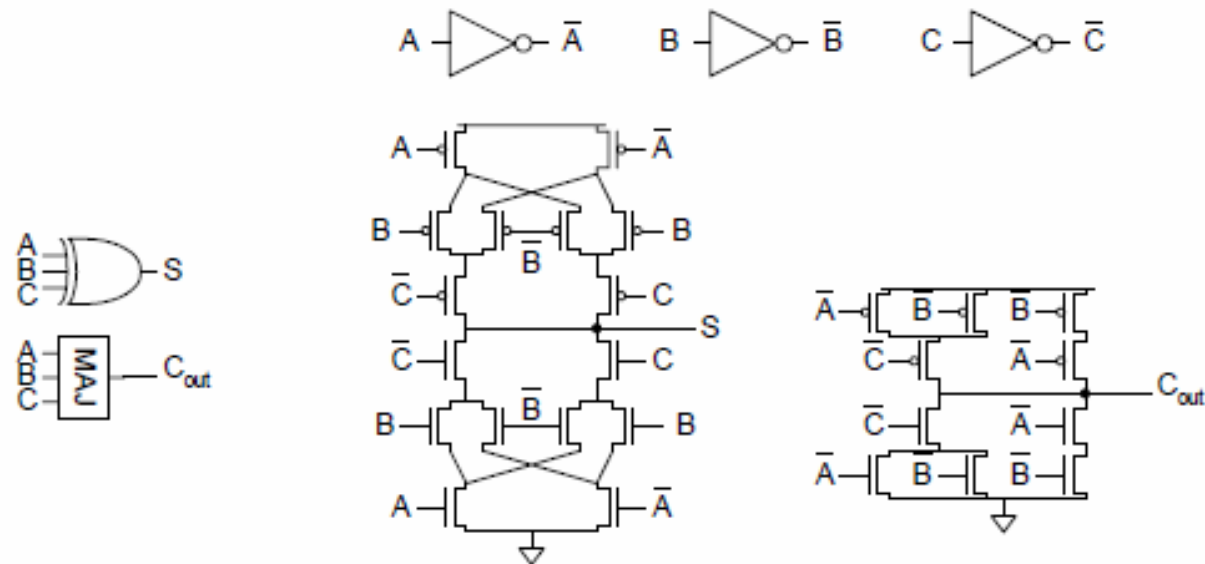


Full Adder Design II

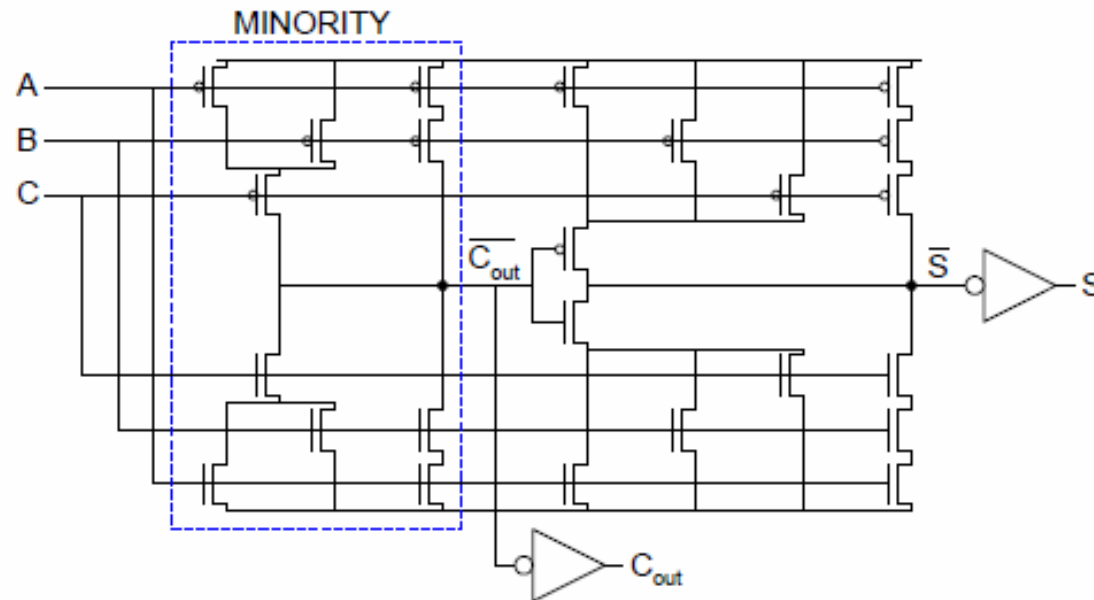- ❑ Factor S in terms of C_{out}
$$S = ABC + (A + B + C)(\sim C_{out})$$
- ❑ Critical path is usually C to C_{out} in ripple adder




Layout of the adder

 


Modified Layout

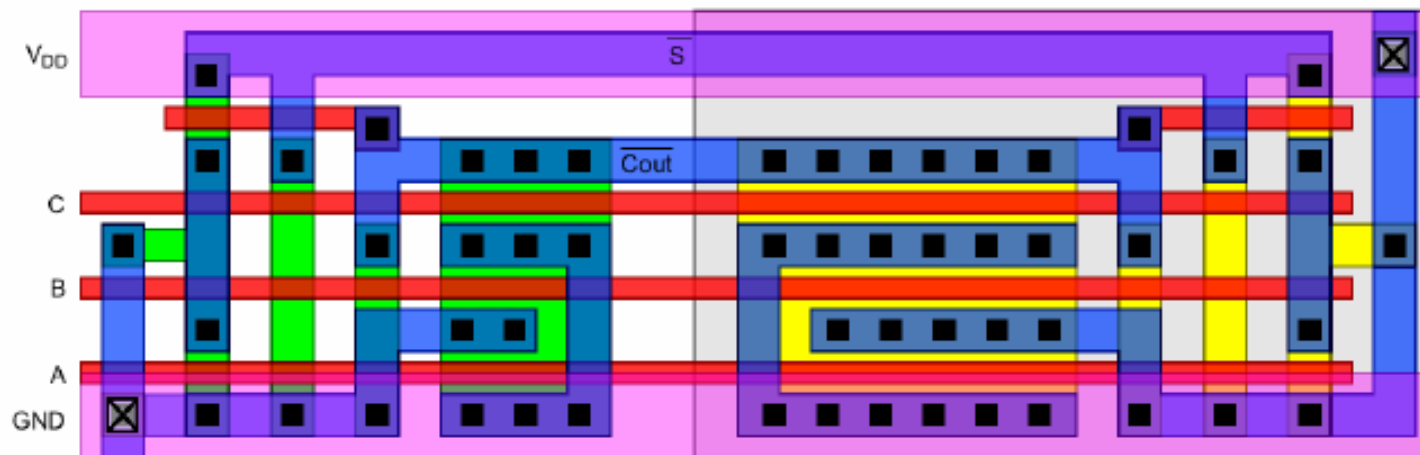- Clever layout circumvents usual line of diffusion
 - Use wide transistors on critical path
 - Eliminate output inverters




Full Adder Design III

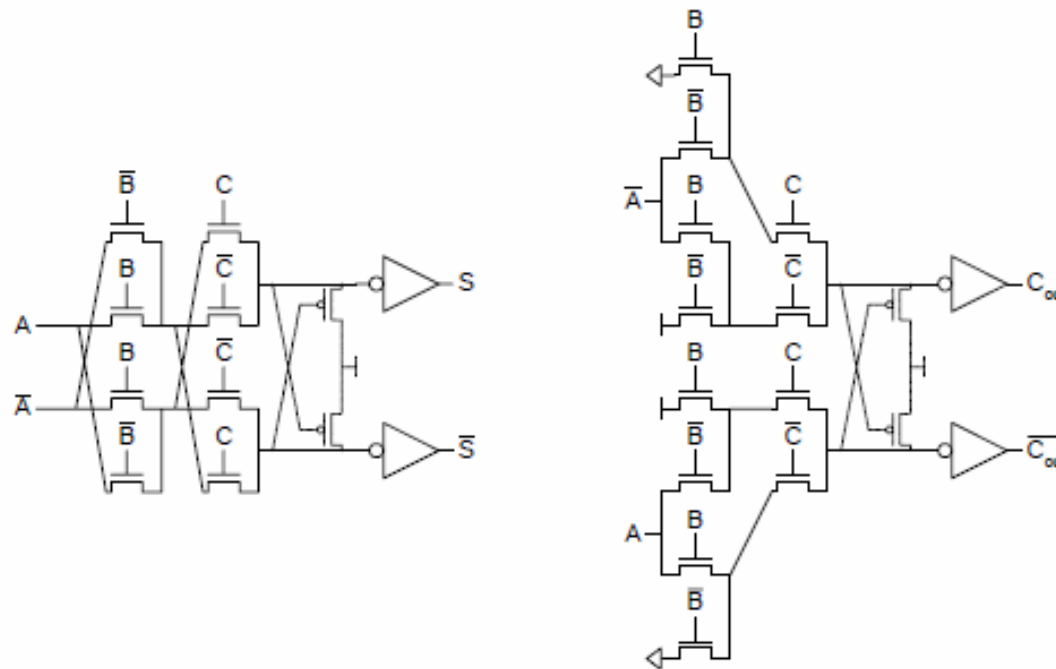- ❑ Complementary Pass Transistor Logic (CPL)
 - Slightly faster, but more area



Full Adder Design IV

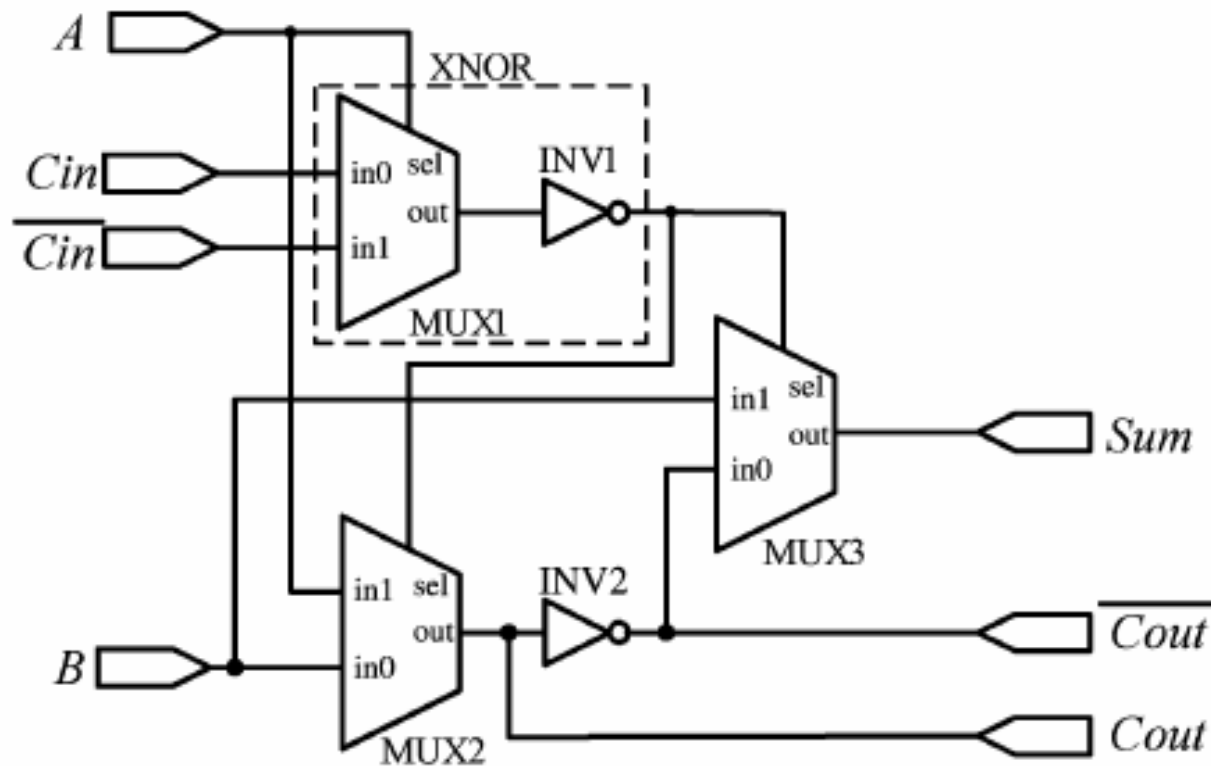


10 Transistor Adder

J.F. Lin et al (2007)



Full Adder Design V

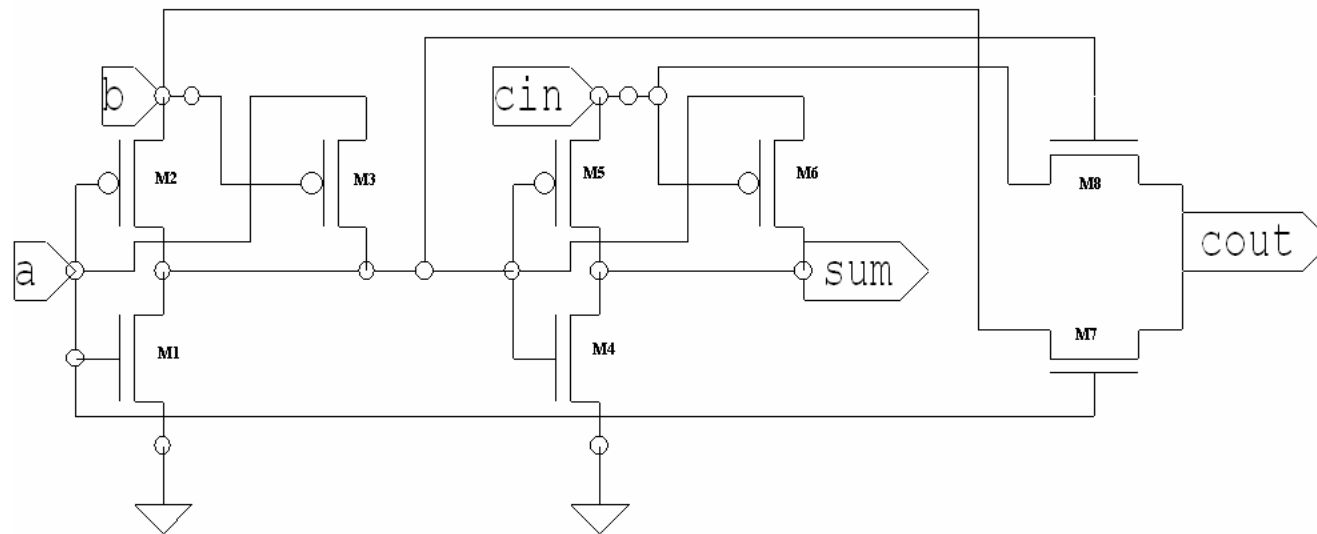


8 Transistor Adder

S. Roy Chowdhury et al (2008)



Carry Propagate Adder

 - N-bit adder called CPA
 - Each sum bit depends on all previous carries
 - How do we compute all these carries quickly?




$$\begin{array}{r} \text{C}_{out} \swarrow \quad \nwarrow \text{C}_{in} \\ \textcircled{0}0000 \\ 1111 \\ +0000 \\ \hline 1111 \end{array}$$

$$\begin{array}{r} \text{C}_{out} \swarrow \quad \nwarrow \text{C}_{in} \\ \textcircled{1}1111 \\ 1111 \\ +0000 \\ \hline 0000 \end{array} \quad \begin{array}{l} \text{carries} \\ A_{4...1} \\ B_{4...1} \\ S_{4...1} \end{array}$$




Carry Ripple Adder

 - Simplest design: cascade full adders
 - Critical path goes from C_{in} to C_{out}
 - Design full adder to have fast carry delay



Inversions

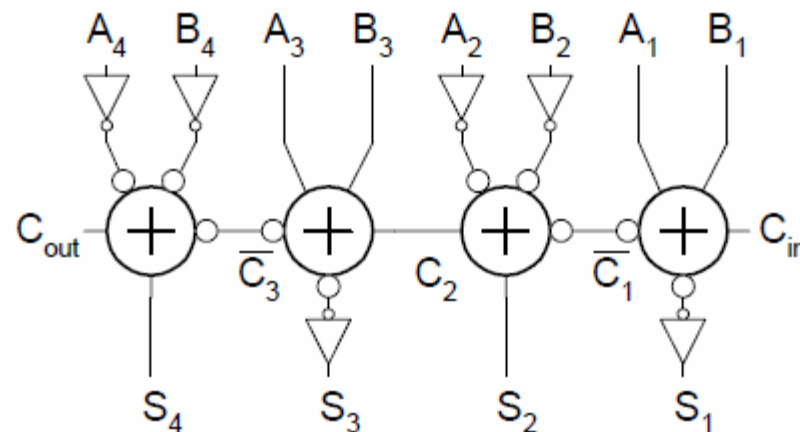- ❑ Critical path passes through majority gate
 - Built from minority + inverter
 - Eliminate inverter and use inverting full adder



Carry propagate, generate and kill

- For a full adder, define what happens to carries
 - Generate: $C_{out} = 1$ independent of C
 - $G =$
 - Propagate: $C_{out} = C$
 - $P =$
 - Kill: $C_{out} = 0$ independent of C
 - $K =$



Generate and Propagate

- Equations often factored into G and P
- Generate and propagate for groups spanning $i:j$

$$G_{i:j} =$$

$$P_{i:j} =$$

- Base case

$$G_{i:i} \equiv G_i =$$

$$P_{i:i} \equiv P_i =$$

$$G_{0:0} \equiv G_0 =$$


$$P_{0:0} \equiv P_0 =$$

- Sum:

$$S_i =$$




Propagate Generate Logic

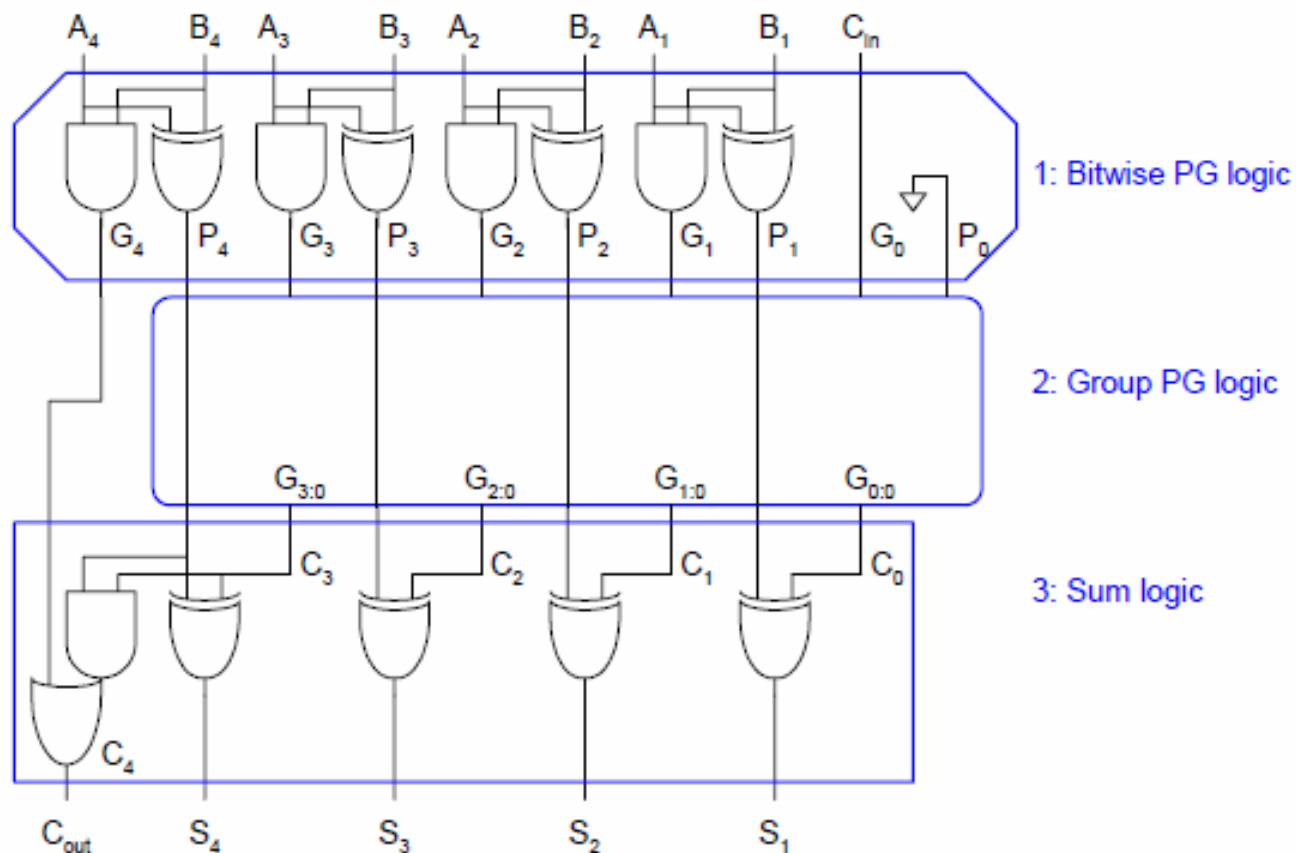


Carry Ripple Revisited

$$G_{i:0} = G_i + P_i \cdot G_{i-1:0}$$

 


Carry ripple PG diagram

$t_{\text{ripple}} =$

 


PG diagram notation

 


Carry Skip Adder

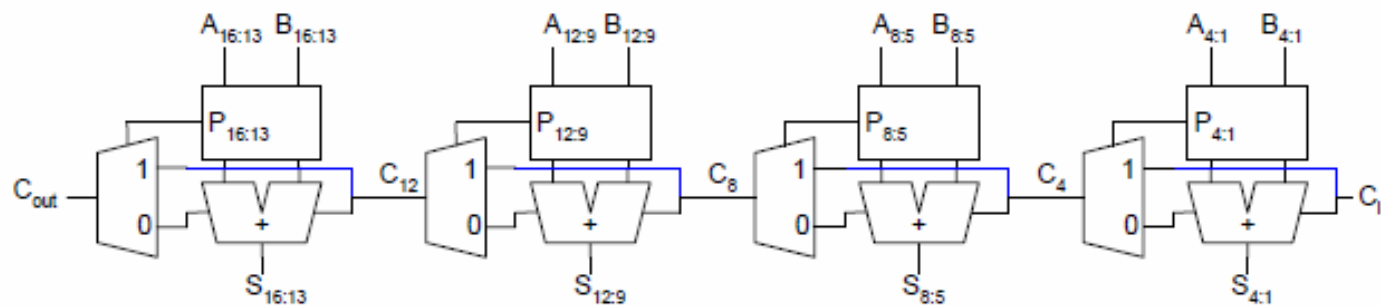- ❑ Carry-ripple is slow through all N stages
- ❑ Carry-skip allows carry to skip over groups of n bits
 - Decision based on n-bit propagate signal



PG diagram of Carry Skip Adder

 


For k n-bit groups ($N = nk$)

$$t_{\text{skip}} =$$




Carry Look Ahead Adder

 - ❑ Carry-lookahead adder computes $G_{i:0}$ for many bits in parallel.
- ❑ Uses higher-valency cells with more than two inputs.




Carry Look Ahead Adder PG diagram

 


Carry Select Adder

 - ❑ Trick for critical paths dependent on late input X
 - Precompute two possible outputs for $X = 0, 1$
 - Select proper output when X arrives
- ❑ Carry-select adder precomputes n-bit sums
 - For both possible carries into n-bit group



Carry Increment Adder

 - Factor initial PG and final XOR out of carry-select



$$t_{\text{increment}} = t_{pg} + \left[(n-1) + (k-1) \right] t_{AO} + t_{\text{xor}}$$




Tree Adders


- ❑ If lookahead is good, lookahead across lookahead!
 - Recursive lookahead gives $O(\log N)$ delay
- ❑ Many variations on tree adders




Brent Kung Adder

 

Sklansky Adder

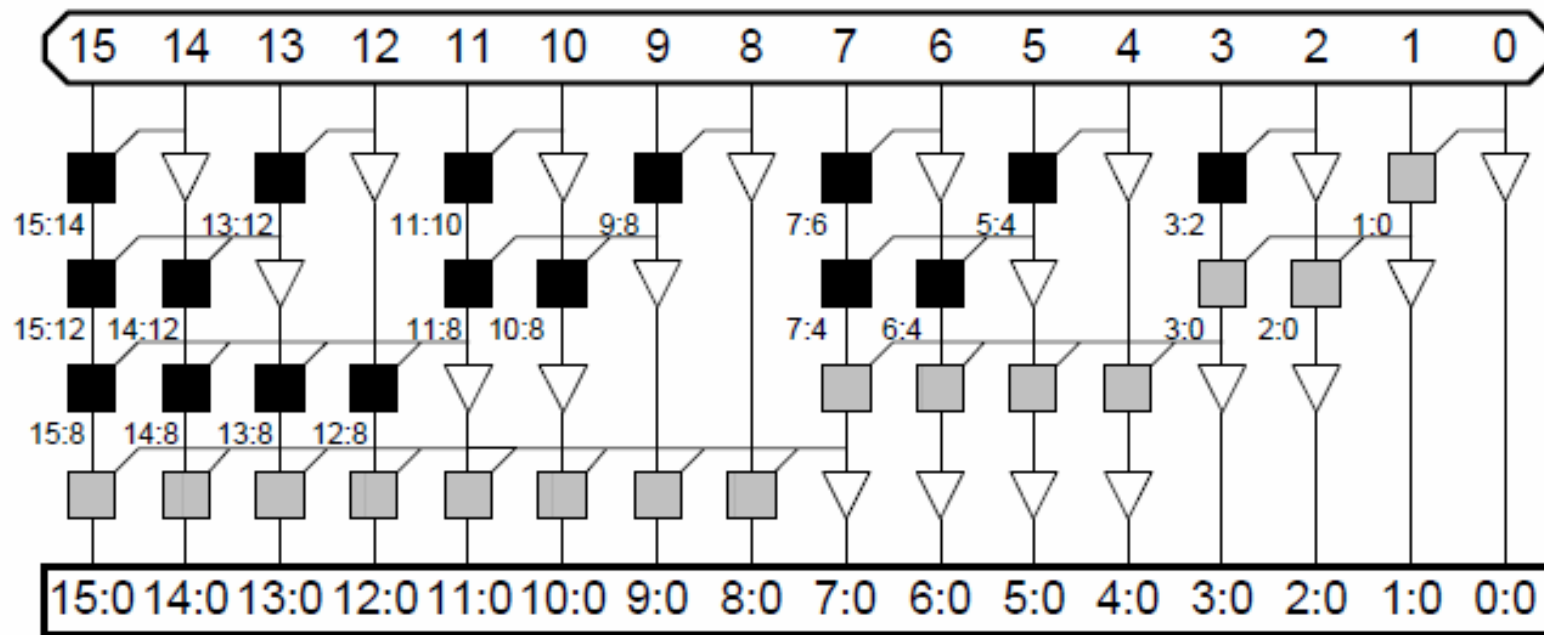

Kogge Stone Adder

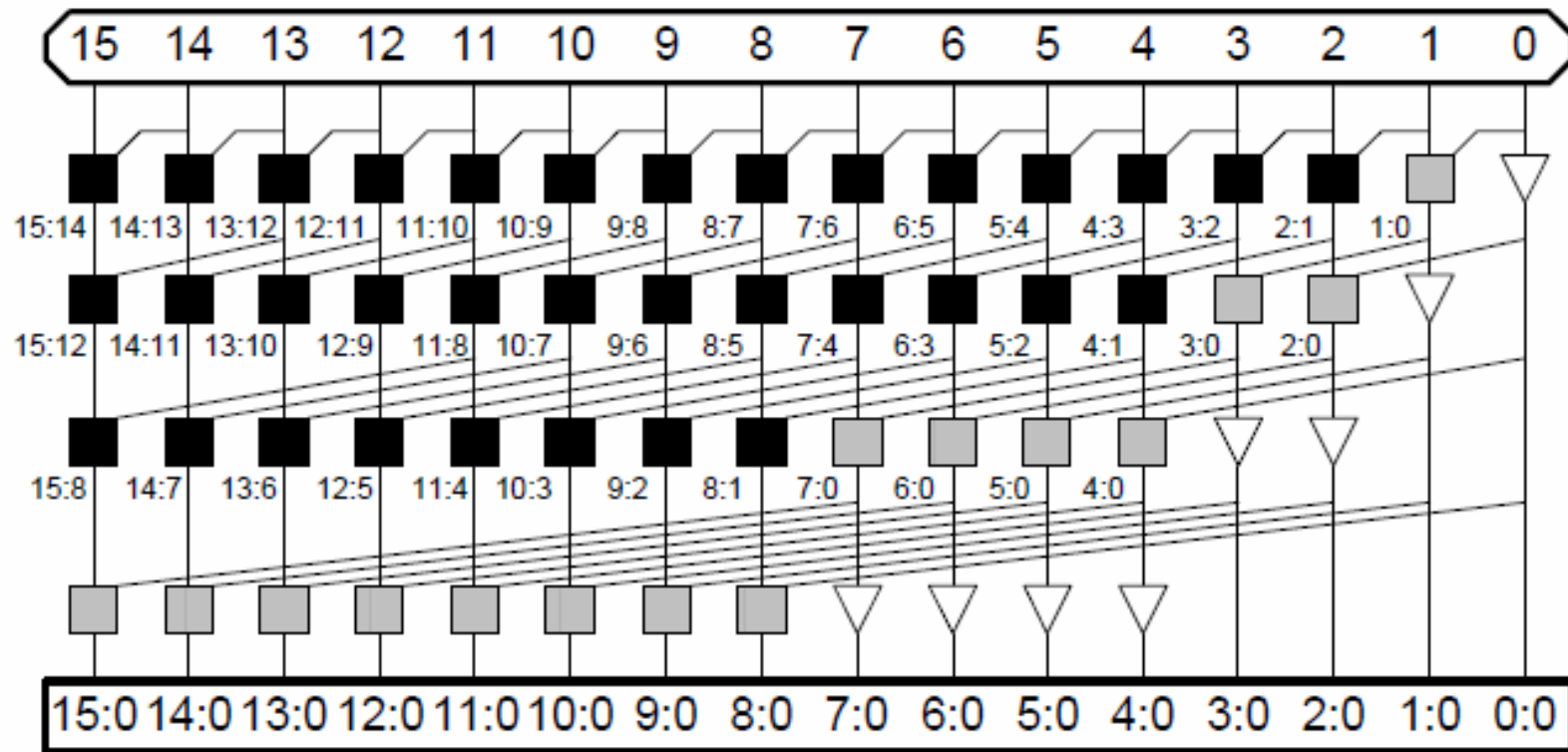

Comparison of the adders

Adder architectures offer area / power / delay tradeoffs.


Choose the best one for your application.

| Architecture | Classification | Logic Levels | Max Fanout | Tracks | Cells |
|------------------|----------------|-----------------|------------|--------|------------------|
| Carry-Ripple | | $N-1$ | 1 | 1 | N |
| Carry-Skip $n=4$ | | $N/4 + 5$ | 2 | 1 | $1.25N$ |
| Carry-Inc. $n=4$ | | $N/4 + 2$ | 4 | 1 | $2N$ |
| Brent-Kung | $(L-1, 0, 0)$ | $2\log_2 N - 1$ | 2 | 1 | $2N$ |
| Sklansky | $(0, L-1, 0)$ | $\log_2 N$ | $N/2 + 1$ | 1 | $0.5 N \log_2 N$ |
| Kogge-Stone | $(0, 0, L-1)$ | $\log_2 N$ | 2 | $N/2$ | $N \log_2 N$ |



Higher Valency Trees

 - ❑ Combine 3 or 4 groups at each level
- ❑ High fan-in gates better suited to domino circuits



Thank You



Dr. Shubhajit Roy Chowdhury

CVEST, IIIT HYDERABAD