

Intro. To VLSI (ECE 361)

Assignment #3

Deadline: 16th Feb


Q1. Draw the schematic of the following using 'BICMOS' logic:



[6 Marks]

- a) 2-input AND gate
- b) 2-input XOR gate
- c) $AB+BC+AC$

Q2. Estimate the area of the following layout designs:

[4 Marks]

 

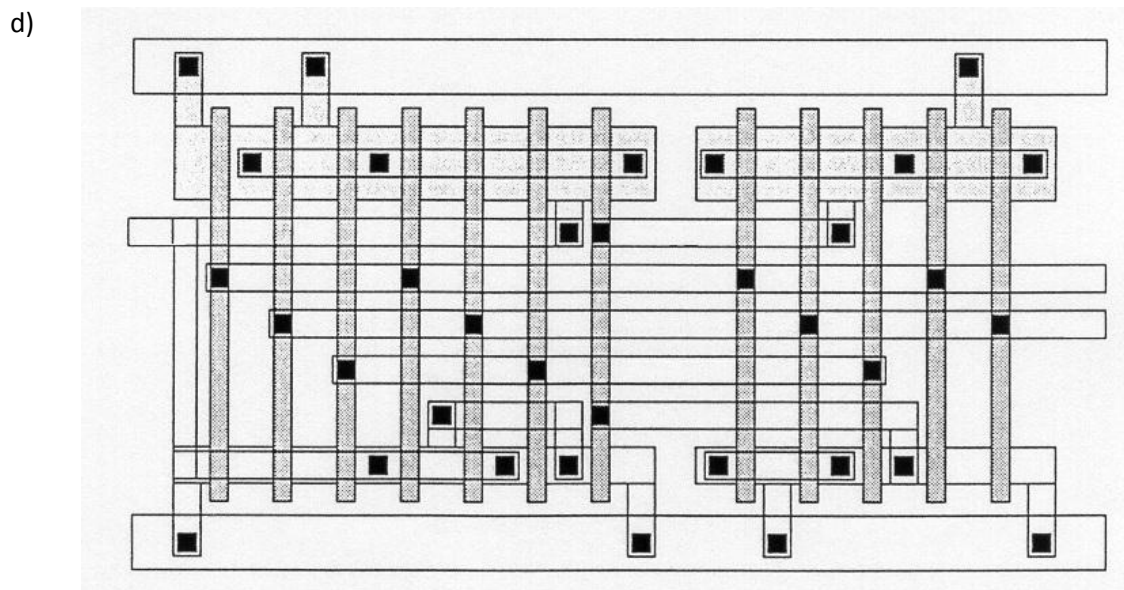 

Q3. Sketch the layout of the following gate and estimate its area in terms of λ^2 .

[5 Marks]

3-input XOR gate ($A \text{ xor } B \text{ xor } C$)

Q4. Write short notes on:

[5 Marks]

- a.) Photolithography
- b.) Ion implantation
- c.) Solid state diffusion

- d.) Etching
- e.) Photoresist

Q5. Describe the fabrication process (including all steps and diagrams) for a NOR gate. [10 Marks]