

Clocking Strategies in VLSI Circuits

Dr. Shubhajit Roy Chowdhury,

Centre for VLSI and Embedded Systems Technology,
IIIT Hyderabad, India

Email: src.vlsi@iiit.ac.in



Dr. Shubhajit Roy Chowdhury

CVES, IIIT HYDERABAD


Clocked Flip-flops

- *Synchronous* design employs clocking signals to coordinate the movement of data through the system
- The data bit D is loaded into the DFF only on a rising clock edge



$$Q(t_0 + t_{ff}) = D(t_0)$$

Where t_0 is the rise edge, and t_{ff} is the time delay when the output has this value

 - In high speed design, the limiting circuit factor is the DFF delay time t_{ff} that is determined by the electronics and the load
 - Decreasing t_{ff} allows for a higher frequency clock
 - The tradeoff of speed and power



Ideal clocking signal

  


Timing in a DFF




Classical State Machines

 - Two models for state machines that use single-clock timing are shown
 - Moore machine and Mealy machine
 - Huffman model: contains both the Moore and Mealy models




(a) Moore machine

 

(b) Mealy machine

Moore and mealy state machines

 

Huffman model of a state machine



Classical State Machines

- FPGA design are also heavily based on classical state machine theory
 - For examples, in combinational logic, Individual gates, PLAs, Programming Logic Device (PLD), and groups of multiplexors
 - Programming is achieved with EPROMs, fuses, SRAM arrays, and some contain lookup tables (LUT, e.g. FPGA) to aid in the design

$$\sum_r m_r$$


(The AND-plane of the PLA can be programmed to produce minterms m_r)

$$T > t_{ff} + t_d + t_{su} + t_h$$

(The clock T must be large enough to allow completion)

Where,

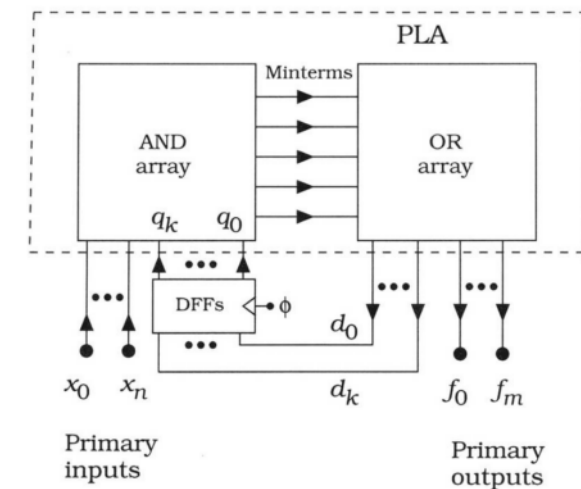- t_{ff} is the delay time from input to output of the flip-flop
- t_d is the logic delay time through the PLA
- t_{su} is the "setup time" of the flip-flop
- t_h is the "hold time" of the flip flop



Huffman state machine using PLA logic




Clocked Logic Cascades


- Ideal waveforms for the complimentary signal

$$\phi \cdot \bar{\phi} = 0$$

$$V_{\max} = V_{DD} - V_{Tn}$$

 


Complementary clocks

 

(a) FETs

(b) Transmission gate

Clock-controlled transistors

 


A clocked cascade




Timing Circles and Clock Skew

 
- *Timing circles*: are simple constructs that can be useful for visualizing data transfer
 - this defines what is known as a 50% duty cycle
- *Clock skew*: the timing of a clock is out of phase with the system reference




Clock generation circuit

 

Clock skew

 

 Timing circle for a single-clock, dual-phase cascade




Timing circle with clock skew




Dual Non-overlapping Clocks

 
- In this technique, two distinct non-overlapping clocks ψ_1 and ψ_2 are used such that
$$\phi_1(t) \cdot \phi_2(t) = 0$$
- Finite-state machines that are based on dual-clock schemes can provide powerful interactive capabilities



Timing circuit for a 2-clock network

 

Dual non-overlapping clocks

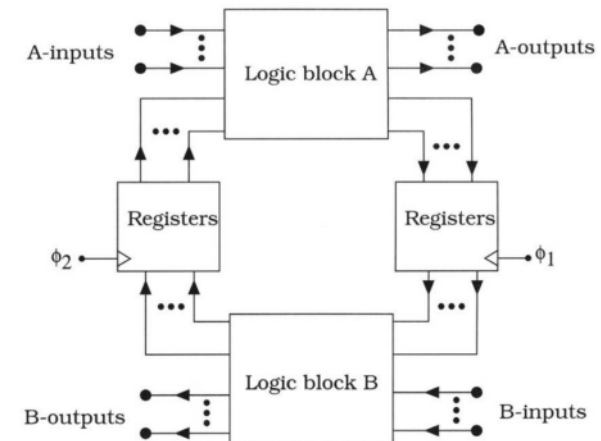


A dual-clock finite-state machine design




Other Multiple-clock Schemes

- It is possible to create different multiple-clock schemes to control clocked logic cascades and state machine
 - For example, a triple, non-overlapping clock set
- However, in modern high-speed VLSI, complicated clocking schemes introduce too many problems
 - Solution: speed gains are accomplished by improved *circuit design, processing, and architectural modifications*
 - The most popular approach is to use a *single-clock, dual-phase system*

 

Triple, non-overlapping clock signals

 


Timing circle for a 3-clock non-overlapping network




Dynamic Logic Cascades

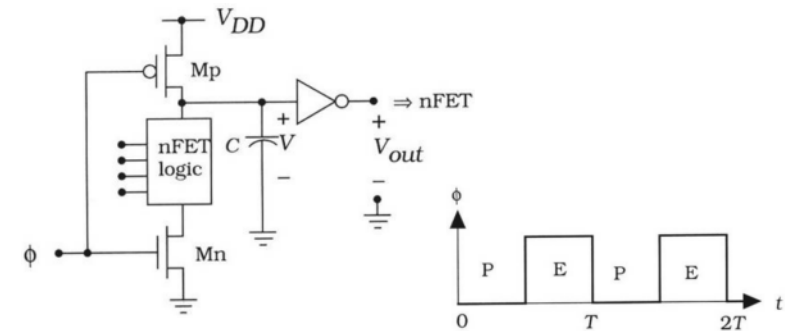- Dynamic logic circuits achieve synchronized data flow by controlling the internal operational states of the logic gate circuits
 - Typical domino logic state:
 - P: pre-charge phase
 - E: Evaluation phase



Operation of a domino logic state

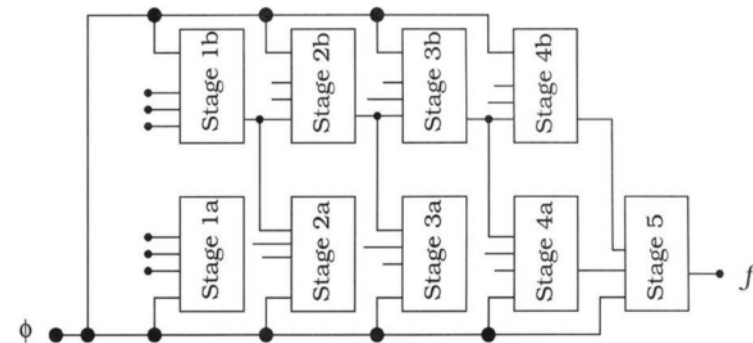


A dynamic logic cascade




Dynamic Logic Cascades

 - The data transfer into and out of a dynamic logic cascade is sequenced with the clock
 - The number of stages that can be included in the chain is determined by the delay for the case where every stage switches
- True Single-Phase Clock (TSPC): use only a single clock ψ throughout



Timing sequence in the domino cascade

 

(a) n-block


(b) p-block

True single-phase clock latches



Basic Concept of Pipelining

 - Pipelining is a tech. that is used to increase the throughput of a sequential set of distinct data inputs through a synchronous logic cascade



Basic pipelined stage for timing analysis

$$T > t_{ff} + t_d + t_{su} + t_s$$


$$t_{hold} < PW$$

(PW: pulse width of the clock)

$$f < \frac{1}{t_{ff} + t_d + t_{su} + t_s}$$

Where,

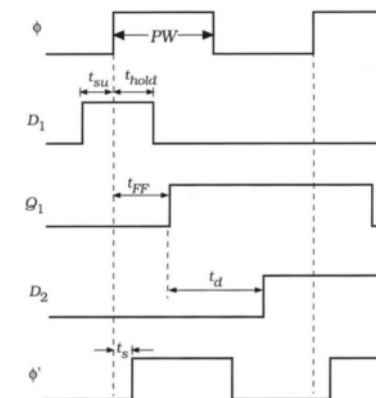- t_{ff} : flip-flop delay time
- t_d : logic delay time
- t_{su} : setup time of the flip-flop
- t_{hold} : hold time of the flip-flop




Waveform quantities for timing analysis




Pipelining

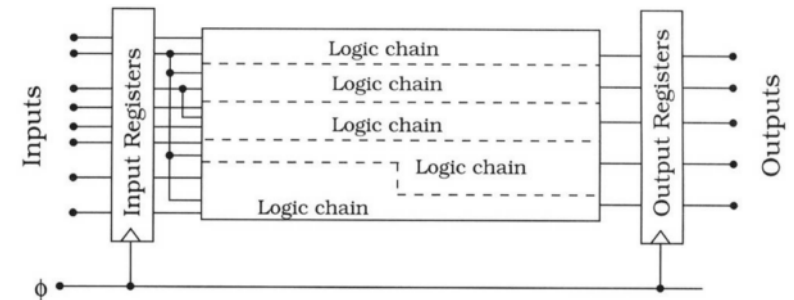- Pipelined systems are designed to increase the overall throughput of a set of sequential input states by dividing the cascade into small visualization of the problem
- Once a circuit completes a calculation and passes the result on to the next stage, it remain idle for the rest of the clock cycle



Logic chains in a clocked system

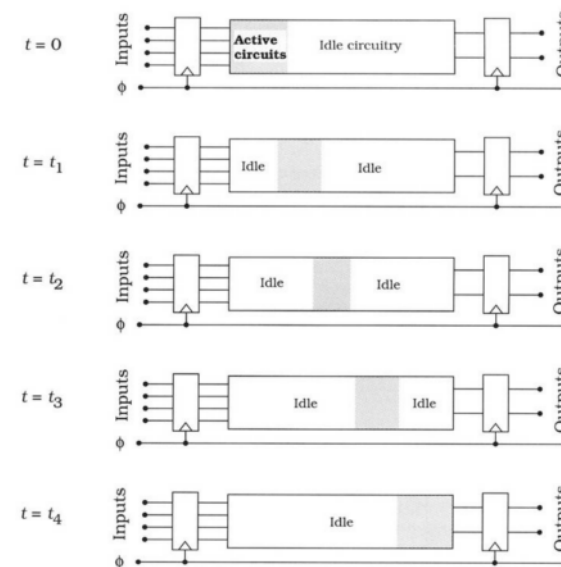


Circuit activity in a logic cascade



Pipelining

 - Since the delay through a logic gate varies its complexity and parasitics, the logic propagation rate will not be uniform




Progression times in the logic cascade


- Dividing the long logic into small groups, add registers between the sections, and use a faster clock, then most of the circuits will be active at any given time

$$T_i > t_{ff} + t_{su} + t_{d,i} + t_{s,i+1}$$

$$T_{pipe} = \max \{T_1, \dots, T_m\}$$

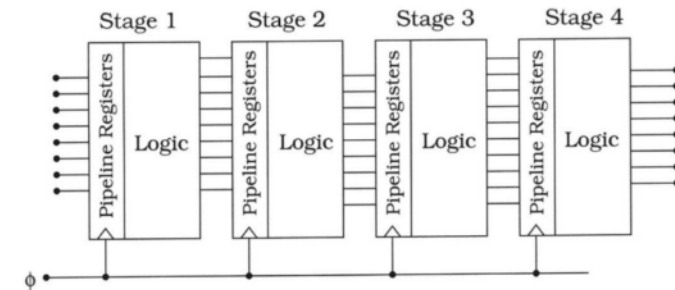

A 4-stage pipeline

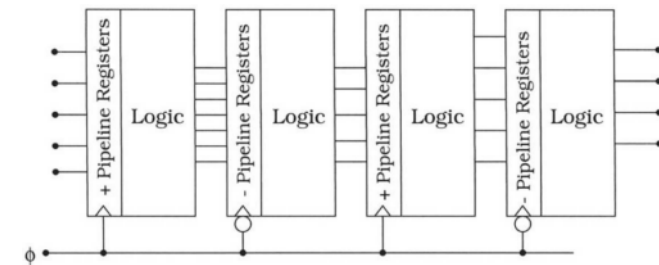

Pipeline with positive edge and negative edge-triggering



Clock Distribution

- When frequencies f reach the 1GHz (10^9 Hz) level corresponding to a clock period of

$$T = \frac{1}{f} = 1 \text{ ns}$$


- However, distribution of the clocking signal to various points of the chip is complicated because the intrinsic RC time delay τ increases as the square of the line length l according to

$$\tau = Bl^2$$


$$\Delta t_1 = B(l_b^2 - l_a^2)$$

$$\Delta t_2 = B(l_c^2 - l_b^2)$$

 - Problems: clock skew and signal distortion will be very difficult to deal with in large chips




A 4-stage pipeline

 


A 4-stage pipeline




Clock Routing and Driver Trees

 

(a) Clocking points

 


(b) First grouping

 


 (c) Interior routing


Simplified view of the clock routing problem




(a) First

 

(b) Second

 

(c) Third

 


(d) Routing


Partitioning steps for defining clocking groups




Driver Tree

 


Geometrical analysis of the letter
"H"

 

Macro-level H-type distribution tree

 


(a) Driver tree

 

(b) Application to H-tree

Driver tree arrangement

 

Driver tree design with interconnect parasitics



Questions?

