

Adder Architectures

Dr. Shubhajit Roy Chowdhury,

Centre for VLSI and Embedded Systems Technology,
IIIT Hyderabad, India

Email: src.vlsi@iiit.ac.in



Dr. Shubhajit Roy Chowdhury

CVES^T, IIIT HYDERABAD

Types of Adders

- Single-bit Addition
- Carry-Ripple Adder
- Carry-Skip Adder
- Carry-Lookahead Adder
- Carry-Select Adder
- Tree Adder
- Higher Valency Trees




Single bit addition

Half Adder

$S =$

$C_{out} =$

 


A	B	C_{out}	S
0	0		
0	1		
1	0		
1	1		

Full Adder

$S =$

$C_{out} =$

 

A	B	C	C_{out}	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		



Propagate, Generate and Kill

- For a full adder, define what happens to carries
 - Generate: $C_{out} = 1$ independent of C
 - $G =$
 - Propagate: $C_{out} = C$
 - $P =$
 - Kill: $C_{out} = 0$ independent of C
 - $K =$




Full Adder Design I (using 32 transistors)

- Brute force implementation from eqns


$$S = A \oplus B \oplus C$$

$$C_{out} = MAJ(A, B, C)$$

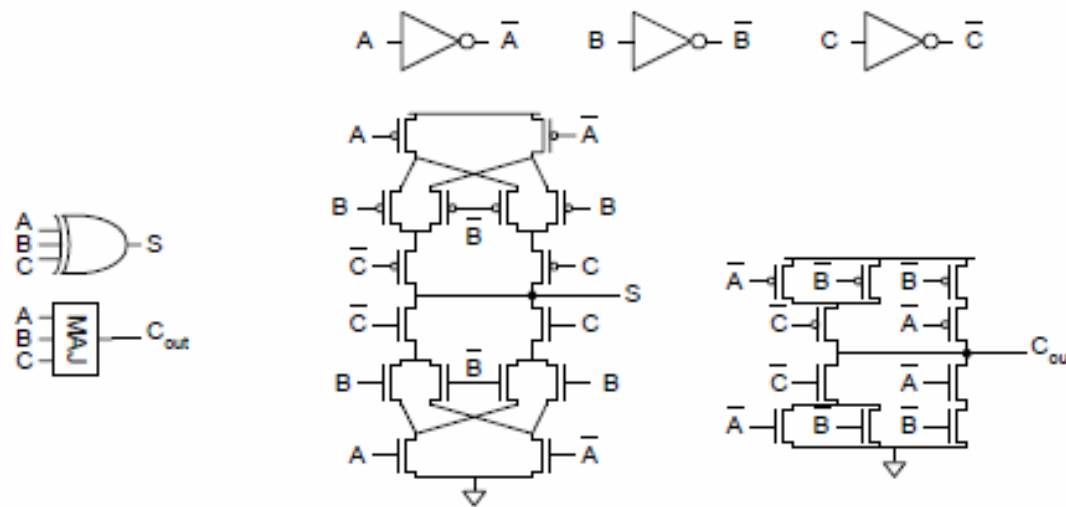


Full Adder Design II (using 28 transistors)

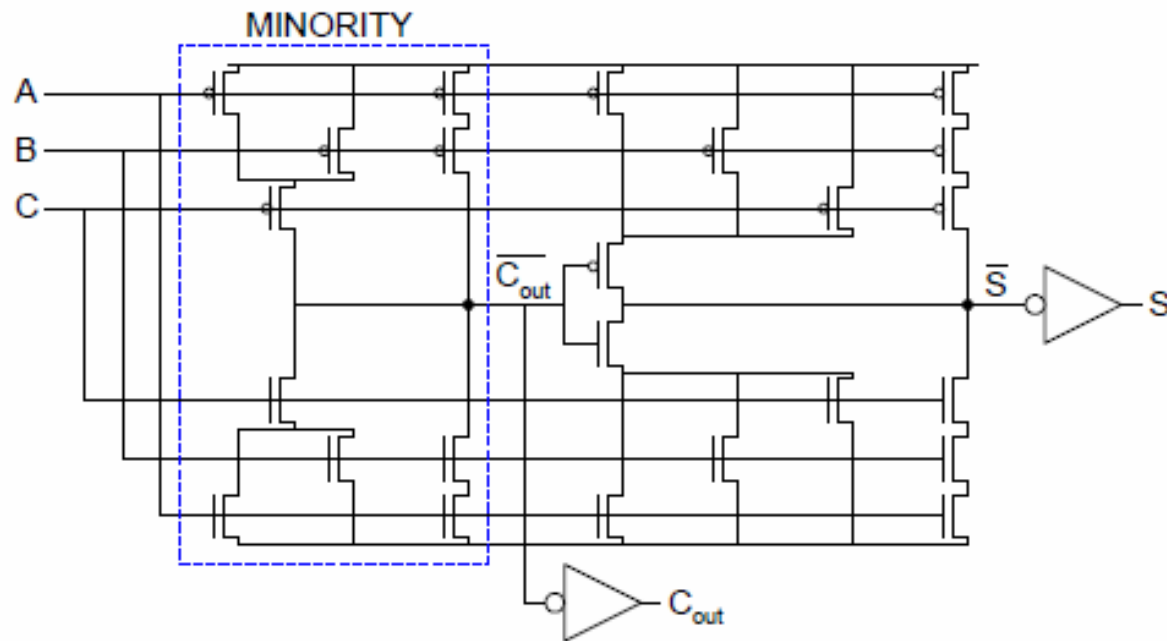- ❑ Factor S in terms of C_{out}
$$S = ABC + (A + B + C)(\sim C_{out})$$
- ❑ Critical path is usually C to C_{out} in ripple adder




Layout of 28 transistor Full Adder

 


Modified Layout of 28T full adder

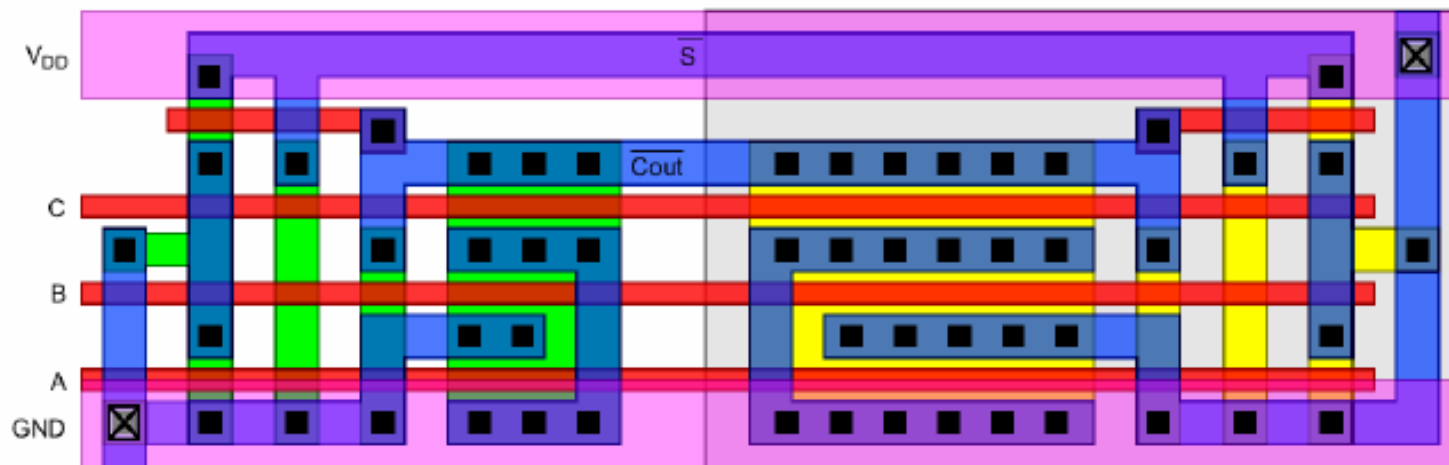- Clever layout circumvents usual line of diffusion
 - Use wide transistors on critical path
 - Eliminate output inverters



Full Adder Design III

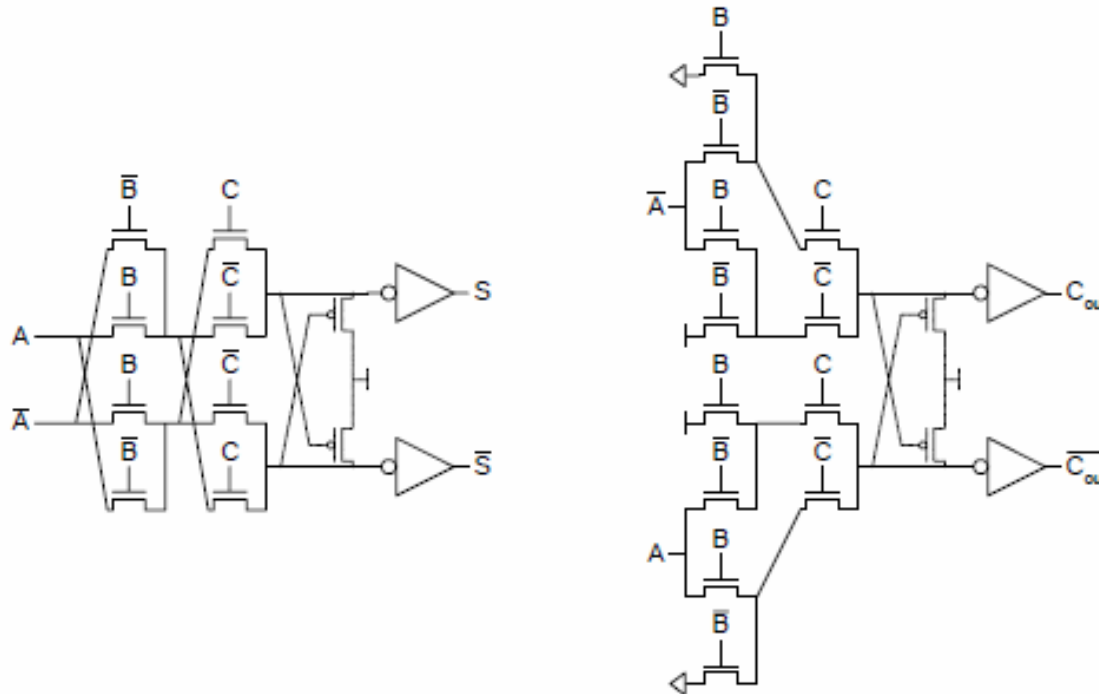
- ❑ Complementary Pass Transistor Logic (CPL)
 - Slightly faster, but more area



Carry Propagate Adder

□ N-bit adder called CPA

 - Each sum bit depends on all previous carries
- How do we compute all these carries quickly?




$$\begin{array}{r} \text{C}_{out} \swarrow \quad \nwarrow \text{C}_{in} \\ \textcircled{00000} \\ 1111 \\ +0000 \\ \hline 1111 \end{array}$$

$$\begin{array}{r} \text{C}_{out} \swarrow \quad \nwarrow \text{C}_{in} \\ \textcircled{11111} \\ 1111 \\ +0000 \\ \hline 0000 \end{array} \quad \begin{array}{l} \text{carries} \\ A_{4...1} \\ B_{4...1} \\ S_{4...1} \end{array}$$




Ripple Carry Adder

 - ❑ Simplest design: cascade full adders
 - Critical path goes from C_{in} to C_{out}
 - Design full adder to have fast carry delay



Inversions

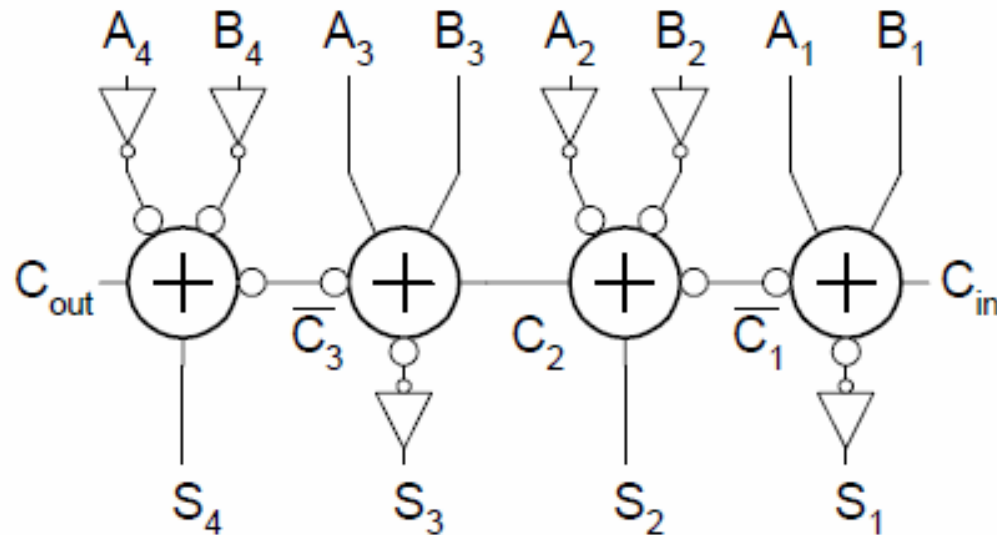- ❑ Critical path passes through majority gate
 - Built from minority + inverter
 - Eliminate inverter and use inverting full adder



Propagate and Generate Logic

- Equations often factored into G and P
- Generate and propagate for groups spanning $i:j$

$$G_{i:j} =$$

$$P_{i:j} =$$

- Base case

$$G_{i:i} \equiv G_i =$$

$$P_{i:i} \equiv P_i =$$

$$G_{0:0} \equiv G_0 =$$


$$P_{0:0} \equiv P_0 =$$

- Sum:

$$S_i =$$




PG Logic

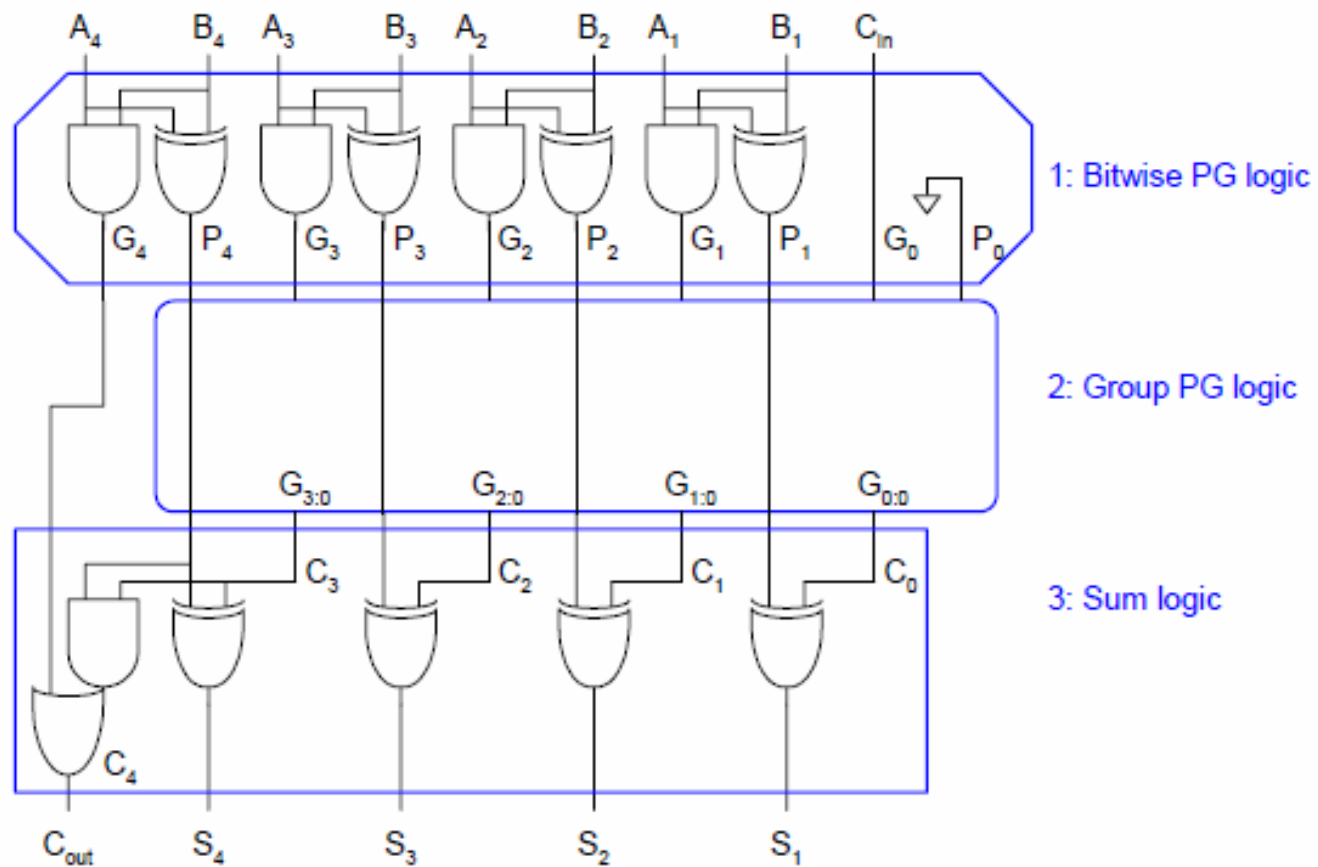


Carry Ripple Revisited

$$G_{i:0} = G_i + P_i \cdot G_{i-1:0}$$

 


Carry Ripple PG Diagram

$t_{\text{ripple}} =$

 


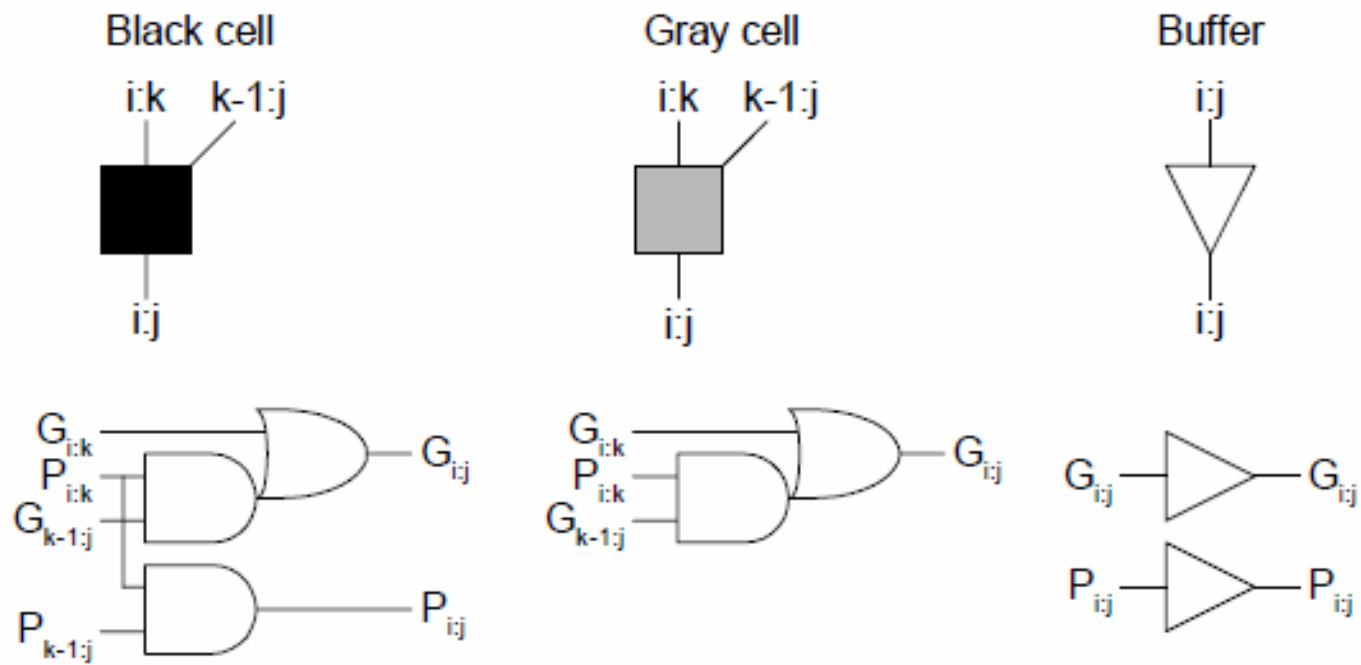Notion of Gray Cell, Black Cell and Buffer




Carry Skip Adder

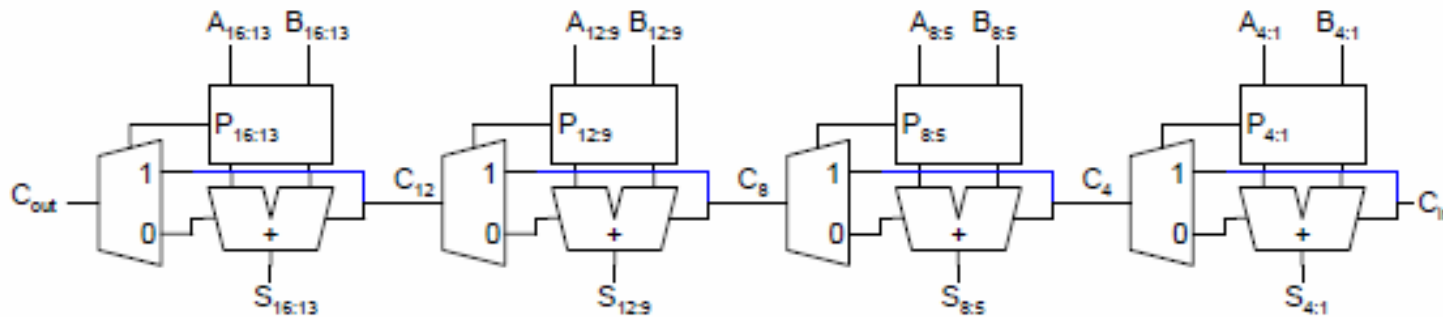- ❑ Carry-ripple is slow through all N stages
- ❑ Carry-skip allows carry to skip over groups of n bits
 - Decision based on n-bit propagate signal



Carry Skip PG Diagram

 


For k n -bit groups ($N = nk$)

$$t_{\text{skip}} =$$




Carry Look Ahead Adder

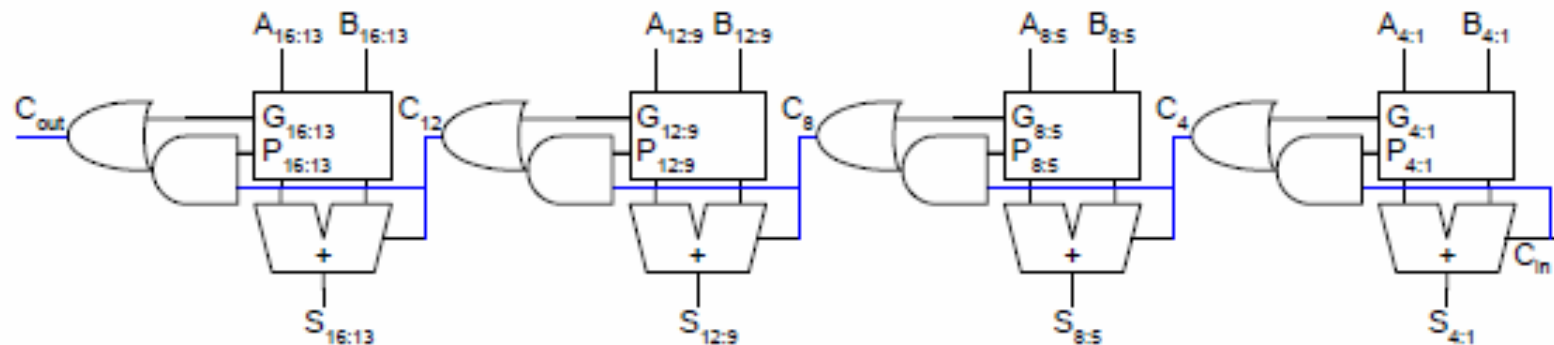
- ❑ Carry-lookahead adder computes $G_{i:0}$ for many bits in parallel.
- ❑ Uses higher-valency cells with more than two inputs.



CLA PG Diagram

 


Higher Valency Cells

 

Carry Select Adder

 - ❑ Trick for critical paths dependent on late input X
 - Precompute two possible outputs for $X = 0, 1$
 - Select proper output when X arrives
- ❑ Carry-select adder precomputes n-bit sums
 - For both possible carries into n-bit group




Tree Adders


- ❑ If lookahead is good, lookahead across lookahead!
 - Recursive lookahead gives $O(\log N)$ delay
- ❑ Many variations on tree adders



Brent Kung Adder

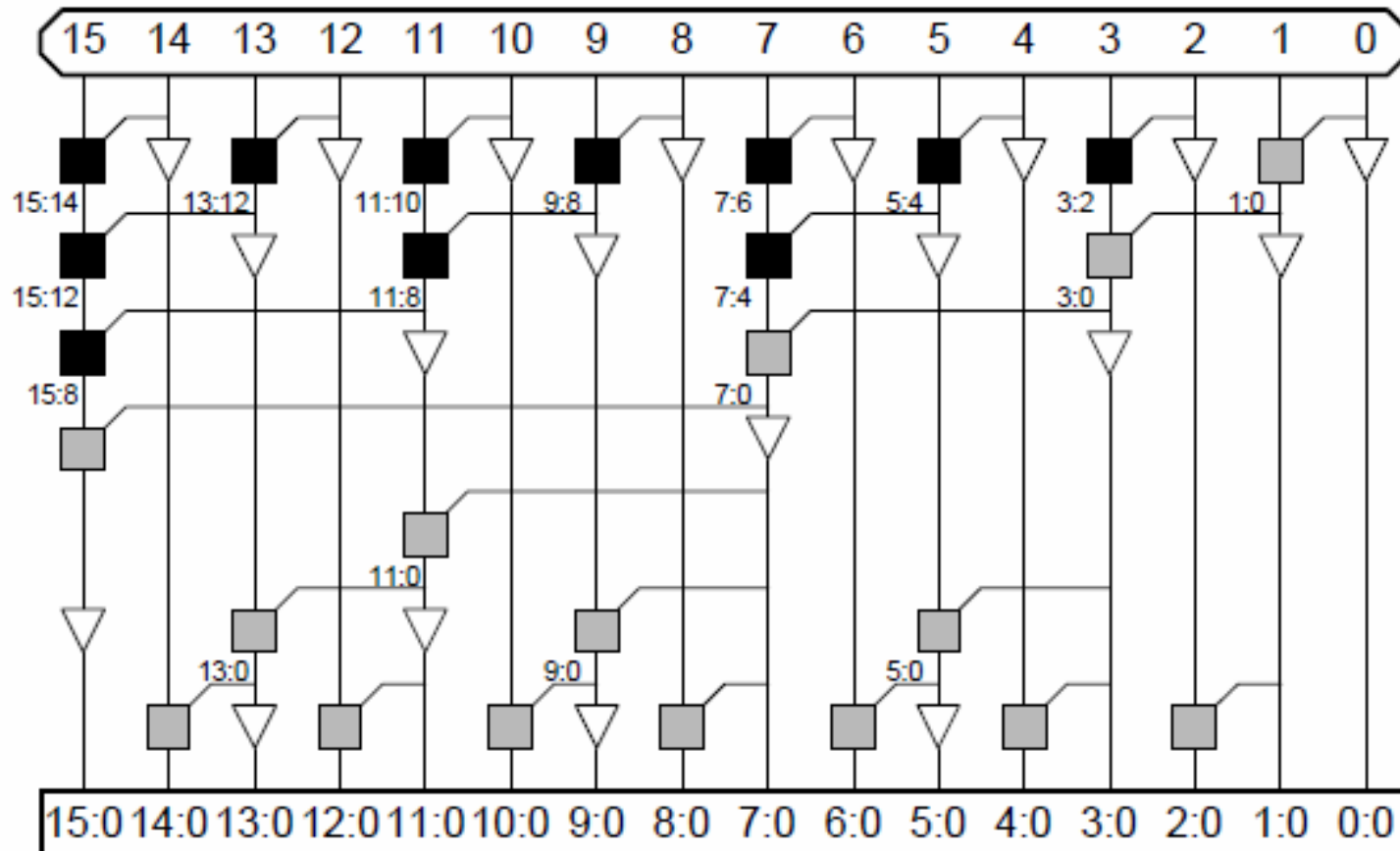

Kogge Stone Adder

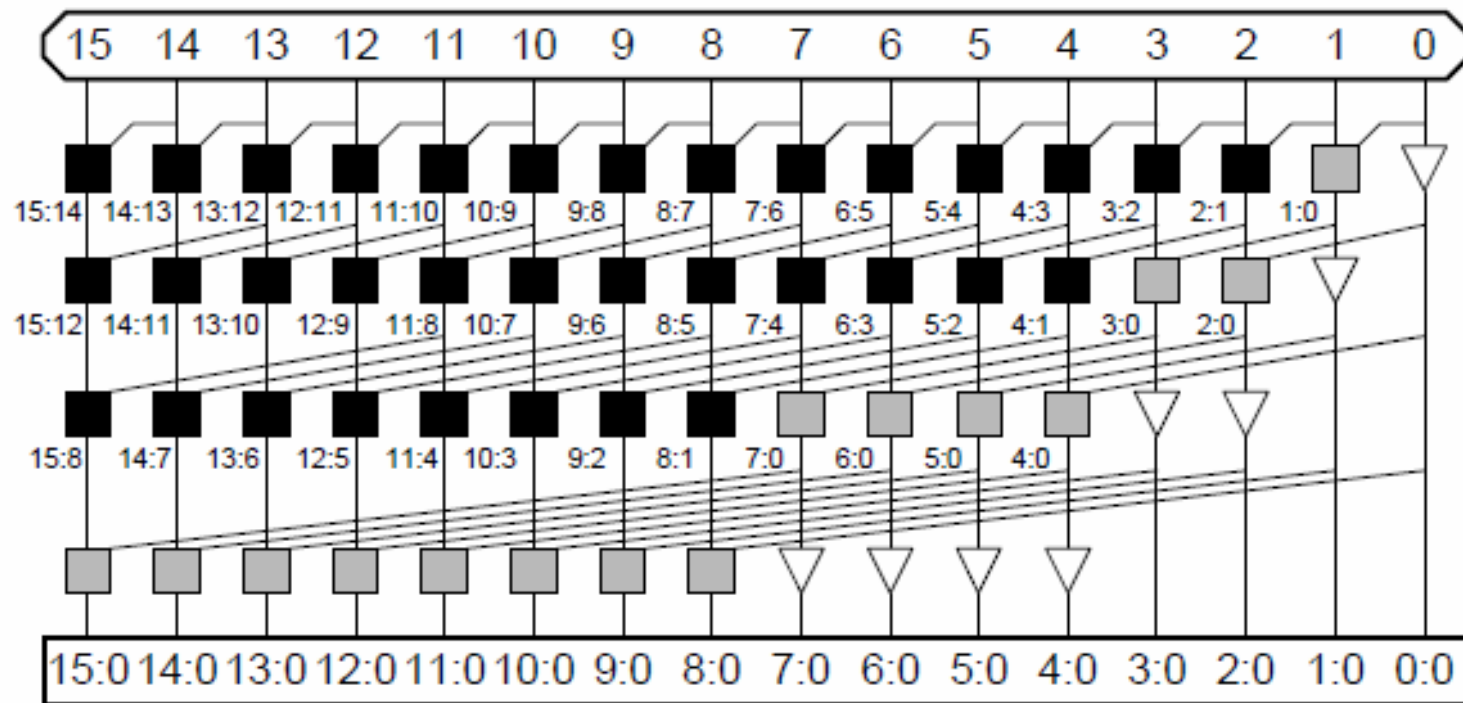


Tree Adder Taxonomy

- ❑ Ideal N-bit tree adder would have
 - $L = \log N$ logic levels
 - Fanout never exceeding 2
 - No more than one wiring track between levels
- ❑ Describe adder with 3-D taxonomy (l, f, t)
 - Logic levels: $L + l$
 - Fanout: $2^f + 1$
 - Wiring tracks: 2^t
- ❑ Known tree adders sit on plane defined by
$$l + f + t = L - 1$$




Tree Adder Taxonomy

 

Higher Valency Trees

 - ❑ Combine 3 or 4 groups at each level
- ❑ High fan-in gates better suited to domino circuits



Thank You



Dr. Shubhajit Roy Chowdhury

CVES*T*, IIIT HYDERABAD