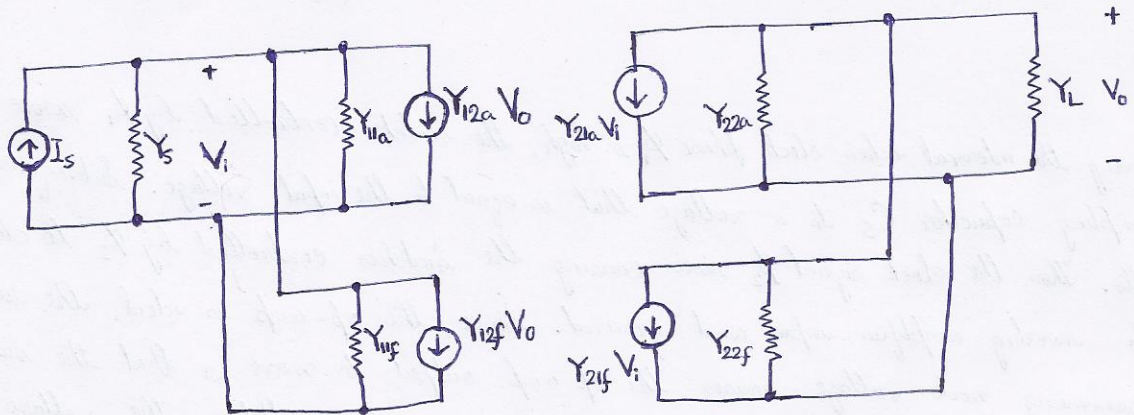


1. The equivalent circuit for the given amplifier configuration is as follows:—



From the  $Y$  parameter representation, we get,

$$I_s = (Y_s + Y_{11a} + Y_{11f}) V_i + (Y_{12a} + Y_{12f}) V_o. \quad (\text{At the input side}) \quad (1)$$

$$0 = (Y_{21a} + Y_{21f}) V_i + (Y_L + Y_{22a} + Y_{22f}) V_o. \quad (\text{At the output side}) \quad (2)$$

$$\text{Let } Y_i = Y_s + Y_{11a} + Y_{11f}.$$


$$Y_o = Y_L + Y_{22a} + Y_{22f}.$$

$$\text{Solving (1) and (2) we get, } \frac{V_o}{I_s} = \frac{-(Y_{21a} + Y_{21f})}{Y_i Y_o - (Y_{21a} + Y_{21f})(Y_{12a} + Y_{12f})}$$

$$\Rightarrow \frac{V_o}{I_s} = \frac{-\frac{(Y_{21a} + Y_{21f})}{Y_i Y_o}}{1 + \frac{-(Y_{21a} + Y_{21f})(Y_{12a} + Y_{12f})}{Y_i Y_o}}$$

$$\Rightarrow \frac{V_o}{I_s} = \frac{-\frac{(Y_{21a} + Y_{21f})}{(Y_s + Y_{11a} + Y_{11f})(Y_L + Y_{22a} + Y_{22f})}}{1 - \frac{(Y_{21a} + Y_{21f})(Y_{12a} + Y_{12f})}{(Y_s + Y_{11a} + Y_{11f})(Y_L + Y_{22a} + Y_{22f})}} \quad (\text{Proved}). \quad (A)$$

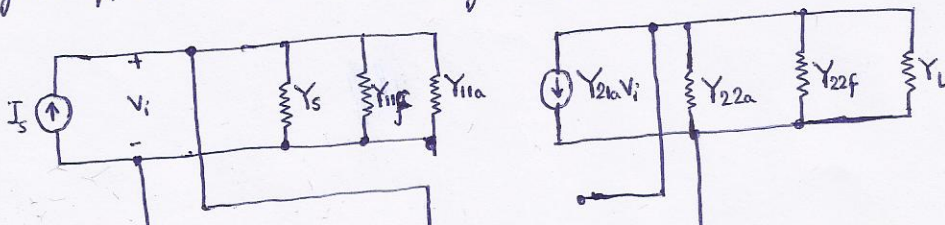With the given approximation the circuit may be redrawn as:





For the given practical approximations, we have,  $|Y_{21a}| \gg |Y_{21f}|$  and  $|Y_{12a}| \ll |Y_{12f}|$ .

Hence from (A), we get, 
$$\frac{V_o}{I_s} \approx - \frac{\frac{Y_{21a}}{(Y_s + Y_{11a} + Y_{11f})(Y_L + Y_{22a} + Y_{22f})}}{1 - \frac{Y_{21a}Y_{12f}}{(Y_s + Y_{11a} + Y_{11f})(Y_L + Y_{22a} + Y_{22f})}} \quad (\text{Proved}).$$

2. During the interval when clock phase  $\phi_1$  is high, the switches controlled by  $\phi_1$  serve to close and charge the sampling capacitor  $C_s$  to a voltage that is equal to the input voltage. Subsequently the clock signal  $\phi_1$  falls. Then the clock signal  $\phi_2$  rises causing the switches controlled by  $\phi_2$  to close and  $C_s$  is connected to inverting amplifier input and ground. Since, the op-amp is ideal, the resulting change in the summing node voltage causes the op-amp output to move so that the summing node voltage is driven back to ground. After the transient has gone to completion, the voltage across  $C_s$  is driven to zero.

Applying the principle of charge conservation, the charge stored at time index  $[n]$  is

$$Q[n] = (0 - V_s[n])C_s + (0 - V_o[n])C_I \quad \dots \quad (1)$$

Charge stored at time  $[n + \frac{1}{2}]$  is:

$$Q[n + \frac{1}{2}] = (0)C_s + (0 - V_o[n + \frac{1}{2}])C_I \quad \dots \quad (2)$$

Since charge is conserved,

$$Q[n] = Q[n + \frac{1}{2}] \quad \dots \quad (3)$$

Also, the charge stored in  $C_I$  is constant during  $\phi_1$ .

$$\text{Hence, } V_o[n+1] = V_o[n + \frac{1}{2}] \quad \dots \quad (4)$$

$$\text{Combining (1), (2), (3), (4), we get, } V_o[n+1] = V_o[n] + \left(\frac{C_s}{C_I}\right)V_s[n] \quad \dots \quad (5)$$


$$\text{From (5), we have, } V_o(j\omega) = V_o(j\omega)e^{-j\omega T} + \left(\frac{C_s}{C_I}\right)V_s(j\omega)e^{-j\omega T}$$

$$\text{Hence, } \frac{V_o(j\omega)}{V_s(j\omega)} = - \frac{C_s}{C_I} \frac{1}{(1 - e^{j\omega T})} = \frac{C_s}{C_I} \cdot \frac{2j}{(e^{j\omega T/2} - e^{-j\omega T/2})} \cdot \frac{e^{-j\omega T/2}}{2j}$$

$$= \frac{C_s}{C_I} \cdot \left(\frac{1}{\sin \frac{\omega T}{2}}\right) \cdot \left(\frac{e^{-j\omega T/2}}{2j}\right) \quad (\text{Proved}).$$



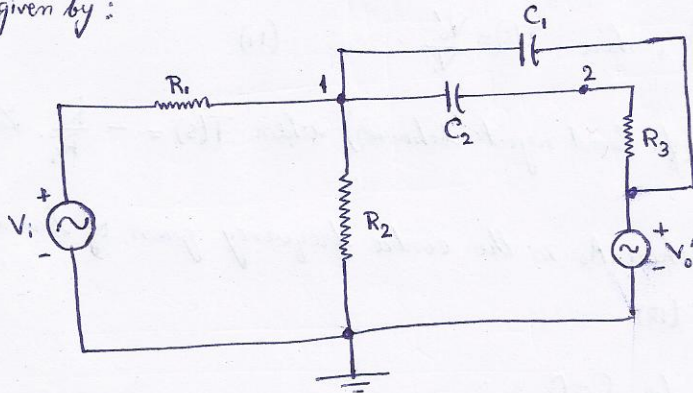3. Let  $V_0'$  be the voltage at the input of resistance  $R_3$ . The equivalent circuit for the subcircuit driving resistance  $R_3$  is given by:



Applying KCL at nodes 1 and 2 we get,

$$\frac{V_1 - V_i}{R_1} + \frac{V_1 - V_0'}{(1/sC_1)} + \frac{V_1 - V_2}{(1/sC_2)} + \frac{V_1}{R_2} = 0 \dots (1)$$

$$\frac{V_2 - V_1}{(1/sC_2)} + \frac{V_2 - V_0'}{R_3} = 0 \dots (2)$$

Rearranging (1) and (2) we get,  $V_1 \left( \frac{1}{R_1} + \frac{1}{R_2} + sC_1 + sC_2 \right) - sC_2 V_2 = \frac{V_i}{R_1} + sC_1 V_0' \dots (3)$

and  $V_1 (-sC_2) + V_2 \left( sC_2 + \frac{1}{R_3} \right) = \frac{V_0'}{R_3} \dots (4)$

Solving (3) and (4) for  $V_2$  and putting  $V_2 = 0$  we get,

$$\begin{vmatrix} \frac{1}{R_1} + \frac{1}{R_2} + sC_1 + sC_2 & \frac{V_i}{R_1} + sC_1 V_0' \\ -sC_2 & \frac{V_0'}{R_3} \end{vmatrix} = 0$$

$$\Rightarrow V_0' \left( \frac{1}{R_1 R_3} + \frac{1}{R_2 R_3} + \frac{sC_1}{R_3} + \frac{sC_2}{R_3} + s^2 C_1 C_2 \right) = -\frac{V_i}{R_1} sC_2$$

$$\Rightarrow \frac{V_0'}{V_i} = - \frac{\frac{sC_2}{R_1}}{\frac{1}{R_1 R_3} + \frac{1}{R_2 R_3} + \frac{sC_1}{R_3} + \frac{sC_2}{R_3} + s^2 C_1 C_2}$$

$$\Rightarrow \frac{V_0'}{V_i} = - \frac{\frac{s}{R_1 C_1}}{s^2 + \left( \frac{C_1 + C_2}{R_3 C_1 C_2} \right) s + \frac{(R_1 + R_2)}{R_3 C_1 C_2 R_1 R_2}} \dots (5)$$

Equation (5) represents the standard form of a series resonant RLC circuit given by,

$$\left| \frac{V_0'}{V_i} \right| = \frac{A_0 s \frac{R}{L}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} \dots (6)$$

Comparing (5) and (6), we get,  $R_1 C_1 = \frac{L}{A_0 R} \dots (7)$  (where  $A_0$  is the centre frequency gain).

$$\frac{R_3 C_1 C_2}{C_1 + C_2} = \frac{L}{R} \dots (8)$$

$$\frac{R_1 R_2 R_3 C_1 C_2}{R_1 + R_2} = LC \dots (9)$$

$$\frac{V_0}{R_6} + \frac{V_i}{R_4} + \frac{V_0'}{R_5} = 0 \dots \dots \dots (10)$$

$$\Rightarrow V_0 = -V_i R_6 \left( \frac{1}{R_4} + \frac{T(s)}{R_5} \right), \text{ where } T(s) = \frac{V_0'}{V_i} \dots \dots \dots (11)$$

The minimum output  $V_0$  occurs (for band reject behavior) when  $T(s) = -\frac{R_5}{R_4}$ . Let the frequency at which  $V_0$  is minimum be  $\omega_0$ .

But at  $\omega_0$ ,  $T(s)$  must be  $-A_0$ , where  $A_0$  is the centre frequency gain of band pass section.

$$\text{Hence, } A_0 = \frac{R_5}{R_4} \dots \dots \dots (12)$$

From (7) and (8), we have for  $C_1 = C_2$ ,

$$A_0 R_1 C_1 = R_3 \frac{C_1}{2}$$

$$\Rightarrow A_0 = \frac{R_3}{2R_1} \dots \dots \dots (13)$$

$$\text{Hence we have, } \frac{R_3}{2R_1} = \frac{R_5}{R_4} \text{ (Proved)}$$

(from (12) and (13))

4. The amplitude of the input sinusoidal signal is  $V_m = \sqrt{2} \times 7.5 \text{ V} = 10.61 \text{ V}$ .

$$\text{With no filter capacitor, } V_{DC} = \frac{2V_m}{\pi} - 2V_Y = 5.358 \text{ V}$$

$$\text{If filtering capacitor is used, ripple voltage } V_R = \frac{V_m - 2V_Y}{2fR_L C} = \frac{(V_m - 2V_Y) I_{Lav}}{2(V_m - 2V_Y - V_R/2) f C}$$

$$\text{Solving for } V_R, \text{ we have } V_R = 1.987 \text{ V.}$$

$$\text{Hence } V_{DC} = V_m - 2V_Y - \frac{V_R}{2} = 8.22 \text{ V.}$$

$$\theta_0 = \sin^{-1} (1 - V_R/V_m) = 0.9488 \text{ rad.}$$

$$\therefore I_{DP} = I_{Lav} + \omega C V_m \cos \theta_0 = 0.12 \text{ A. } A_{200}$$