

VLSI Architectures

Assignment -5

Memory Design

1. Consider a 1KX64 bit SRAM. The memory consist of 1K words, each consisting of 64 bits arranged as a 256X256 array of 6T SRAM cells. A word is selected for reading by the row and column decoders. The row decoder asserts one of the 256 word-lines. Each word-line selects a row of four 64 bit words. Four selected words feed the input of the 4:1 MUX controlled by the outputs of the column decoder. Each access transistor in the memory cell is 4λ in width. Each SRAM cell is $40\lambda \times 40\lambda$. Use TSMC 180nm CMOS process.
 - (a) Estimate the average power being dissipated and the maximum power being dissipated.
 - (b) Estimate the average delay to access a word from the memory..