


Intro. To VLSI (ECE361)

Assignment #2

Q1. Consider the nMOS transistor in a  $0.6\mu\text{m}$  process with gate oxide thickness of  $100\text{\AA}$ . The doping level is  $N_A = 2 \times 10^{17} \text{cm}^{-3}$  and the normal threshold voltage is  $0.7\text{V}$ . The body is tied to ground with a substrate contact. How much does the threshold change at room temperature if the source is at  $4\text{V}$  instead of  $0$ ? [2 Marks]

Q2. Does the body effect of a process limit the no. of transistors that can be placed in series in a CMOS gate at low frequencies? Explain. [2 Marks]

 
Q3. A novel inverter has the transfer characteristics shown below. What are the values of  $V_{IL}$ ,  $V_{IH}$ ,  $V_{OL}$  and  $V_{OH}$  that give best noise margins? What are these high and low noise margins? [4 Marks]



Q4. Draw the schematic of a Half Adder and a Full Adder (Max. 28 transistors) using complementary CMOS Logic. Can you think of a novel design that may reduce no. of transistors used? [8+2 Marks]

Q5. Suppose  $V_{DD} = 1.2\text{ V}$  and  $V_t = 0.4\text{ V}$ . Neglecting body effect, determine  $V_{out}$  in the following circuit for:

 - i.  $V_{in} = 0\text{ V}$
- ii.  $V_{in} = 0.6\text{ V}$
- iii.  $V_{in} = 0.9\text{ V}$
- iv.  $V_{in} = 1.2\text{ V}$



[2 Marks]